

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EVERYDAY

Vol.34 No.6

PRACTICAL ELECTRONICS

CAN \$6.99/US \$4.95

SPECIAL FEATURE

CATCH THE WAVE

A tsunami warning system



PIC ULTRASONIC RADAR

Experimental "vision" system



RADIO CONTROLLED MODEL SWITCHER

Additional
switching for
RC systems

SUPER-EAR AUDIO TELESCOPE

A parabolic microphone & amplifier

BACK TO BASICS - 3

Scarecrow - Digital Lock



www.epemag.co.uk

Copyright © 2005, Wimborne Publishing Ltd
(408 Wimborne Road East, Ferndown, Dorset, BH22 9ND, UK)

and TechBites Interactive Inc.,
(PO Box 857, Madison, Alabama 35758, USA)

All rights reserved.

WARNING!

The materials and works contained within *EPE Online* — which are made available by Wimborne Publishing Ltd and TechBites Interactive Inc — are copyrighted. You are permitted to make a backup copy of the downloaded file and one (1) hard copy of such materials and works for your personal use. International copyright laws, however, prohibit any further copying or reproduction of such materials and works, or any republication of any kind.

TechBites Interactive Inc and Wimborne Publishing Ltd have used their best efforts in preparing these materials and works. However, TechBites Interactive Inc and Wimborne Publishing Ltd make no warranties of any kind, expressed or implied, with regard to the documentation or data contained herein, and specifically disclaim, without limitation, any implied warranties of merchantability and fitness for a particular purpose.

Because of possible variances in the quality and condition of materials and workmanship used by readers, *EPE Online*, its publishers and agents disclaim any responsibility for the safe and proper functioning of reader-constructed projects based on or from information published in these materials and works. In no event shall TechBites Interactive Inc or Wimborne Publishing Ltd be responsible or liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or any other damages in connection with or arising out of furnishing, performance, or use of these materials and works.

ISSN 0262 3617

PROJECTS ... THEORY ... NEWS ...
COMMENTS ... POPULAR FEATURES ...

VOL. 34. No. 6 JUNE 2005




Cover illustration: Mehau Kulyk/Science Photo Library

EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

www.epemag.co.uk

EPE Online: www.epemag.com

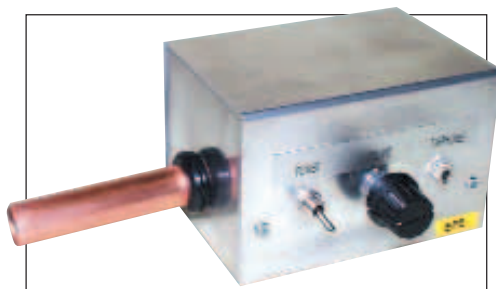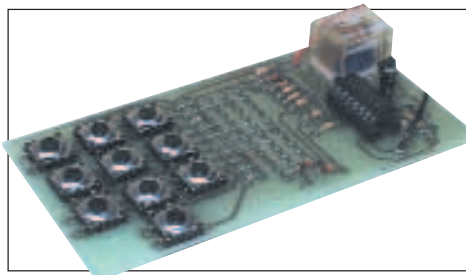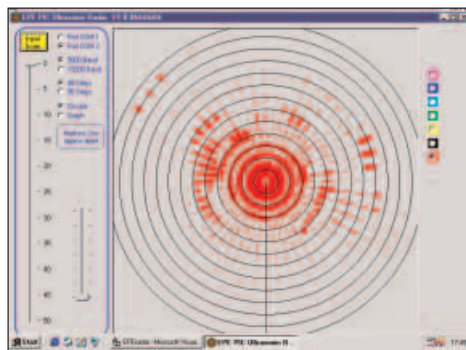

© Wimborne Publishing Ltd 2005. Copyright in all drawings, photographs and articles published in **EVERYDAY PRACTICAL ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our July 2005 issue will be published on Thursday, 9 June 2005. See page 379 for details

Projects and Circuits

- SUPER-EAR AUDIO TELESCOPE** by Tom Merryfield 388
Listen more clearly to those distant sounds
- RADIO CONTROL MODEL SWITCHER** by Ken Ginn 394
A radio controlled power switch for models and other devices
- INGENUITY UNLIMITED – Sharing your ideas with others** 403
GPS/Audio Selector; Virtual Bomb
- PIC ULTRASONIC RADAR** by John Becker 412
Let your mobile robot listen to the landscape with this experimental system
- BACK TO BASICS – 3 Scarecrow and Digital Lock** by Bart Trepak 430
Simple, easy-to-build circuits based on one or two CMOS logic chips

Series and Features


- CIRCUIT SURGERY** by Alan Winstanley and Ian Bell 400
Continuing the CompactFlash primer and outlining how to use the interface
- CATCH THE WAVE** by Mark Williamson 408
Can technology help to reduce tsunami life-loss?
- TECHNO TALK** by Mark Nelson 411
Playing tag – more applications for r.f. ID tags
- DIGITAL TV SWITCHOVER** by Barry Fox 421
Updating us on the plans, and problems, for switching off UK analogue TV
- PROGRAMMING PIC 18F INTERRUPTS** by Malcolm Wiles 422
Clarifying the datasheet for the PIC 18F family
- NET WORK – THE INTERNET PAGE** surfed by Alan Winstanley 435
File download blues; broadband choices; 30Mbps – why are we waiting?
- INTERFACE** by Robert Penfold 438
Computer-controlled PWM power supply

Regulars and Services

- BACK ISSUE CD-ROMS** single-source shopping for issues you've missed 382
- BACK ISSUES** Did you miss these? 383
- EDITORIAL** 387
- NEWS** – Barry Fox highlights technology's leading edge 398
Plus everyday news from the world of electronics
- READOUT** John Becker addresses general points arising 406
- CD-ROMS FOR ELECTRONICS** 426
A wide range of CD-ROMs for hobbyists, students and engineers
- PIC N' MIX** by John Becker 436
Data tables and the DE directive, and a "D"ebatable VB problem
- SHOPTALK** with David Barrington 437
The *essential* guide to component buying for *EPE* projects
- DIRECT BOOK SERVICE** 440
A wide range of technical books available by mail order, plus more CD-ROMs
- ELECTRONICS MANUALS** 443
CD-ROM reference works for hobbyists, students and service engineers
- PIC PROJECTS VOL 1 CD-ROM** 444
A plethora of 20 "hand-PICKed" *EPE* past projects
- PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE** 445
PCBs for *EPE* projects. Plus *EPE* project software
- ADVERTISERS INDEX** 448

Readers Services • Editorial and Advertisement Departments 387

Learn About Microcontrollers

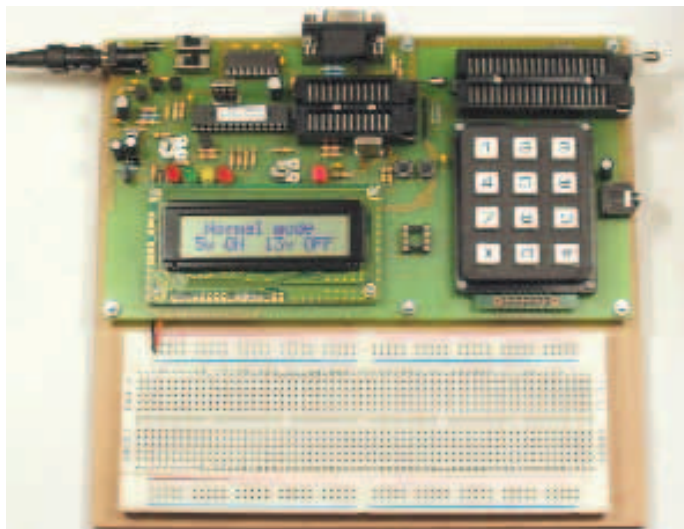

PIC Training & Development System

The best place to start learning about microcontrollers is the PIC16F84. This is easy to understand and very popular with construction projects. Then continue on using the more sophisticated PIC16F877 family.

The heart of our system is two real books which lie open on your desk while you use your computer to type in the programme and control the hardware. Start with four very simple programmes. Run the simulator to see how they work. Test them with real hardware. Follow on with a little theory....

Our complete PIC training and development system consists of our universal mid range PIC programmer, a 306 page book covering the PIC16F84, a 262 page book introducing the PIC16F877 family, and a suite of programmes to run on a PC. The module is an advanced design using a 28 pin PIC16F870 to handle the timing, programming and voltage switching requirements. The module has two ZIF sockets and an 8 pin socket which between them allow most mid range 8, 18, 28 and 40 pin PICs to be programmed. The plugboard is wired with a 5 volt supply. The software is an integrated system comprising a text editor, assembler disassembler, simulator and programming software. The programming is performed at 5 volts, verified with 2 volts or 3 volts applied and verified again with 5.5 volts applied to ensure that the PIC is programmed correctly over its full operating voltage. DC version for UK, battery version for overseas. UK orders include a plugtop power supply.

Universal mid range PIC programmer module
 + Book Experimenting with PIC Microcontrollers
 + Book Experimenting with the PIC16F877 (2nd edition)
 + Universal mid range PIC software suite
 + PIC16F84 and PIC16F870 test PICs. £159.00
 (Postage & insurance UK £10, Europe £15, Rest of world £25)

Experimenting with PIC Microcontrollers

This book introduces the PIC16F84 and PIC16C711, and is the easy way to get started for anyone who is new to PIC programming. We begin with four simple experiments, the first of which is explained over ten and half a pages assuming no starting knowledge except the ability to operate a PC. Then having gained some practical experience we study the basic principles of PIC programming, learn about the 8 bit timer, how to drive the liquid crystal display, create a real time clock, experiment with the watchdog timer, sleep mode, beeps and music, including a rendition of Beethoven's *Für Elise*. Finally there are two projects to work through, using the PIC16F84 to create a sine wave generator and investigating the power taken by domestic appliances. In the space of 24 experiments, two projects and 56 exercises the book works through from absolute beginner to experienced engineer level.

Hardware & Ordering Information

The programmer module for both systems connects to the serial port of your PC (COM1 or COM2). All our software referred to in this advertisement will operate within Windows 98, XP, NT, 2000 etc.

Telephone with Visa, Mastercard or Switch, or send cheque/PO. All prices include VAT if applicable.

Web site:- www.brunningssoftware.co.uk

Mail order address:

Brunning Software 138 The Street, Little Clacton, Clacton-on-sea, Essex, CO16 9LS. Tel 01255 862308

PIC16F88 Project Modules

If you have our PIC Training & Development System or you are thinking of buying it you will find our Project Modules for the PIC16F88 a very useful extension.

The new system consists of five modules, a new book featuring one of the latest PIC microcontrollers, software to run on your PC with ready made library routines, inter-connecting cables and plugtop power supply (UK only). You only need the programmer module if you purchased our PIC training system before January 2004.

Module 1 - Programmer Module
 with PIC programming software. . . £50.00
 Module 2 - Display Driver Module. . . £40.00
 Module 3 - Motor Control Module. . . £20.00
 Module 4 - General I/O Module. . . . £20.00
 Module 5 - RS-232 Module. £10.00
 Book PIC Project Modules. £20.00
 PC programming software. £25.00

Plugtop PSU for UK. £ 4.00
 PC serial lead (9 way D). £ 3.80
 Two 10 way interconnecting leads. . . £ 6.00


Total price for the complete system. . £135.00
 (plus carriage same as PIC training system.)

The Motor Control Module although only 70mm by 42mm has two outputs which can each control a DC motor up to 12 volts at 4 amps continuous (or be used to switch up to 4 amps of DC for any other use such as mains switching relays). The speed of the two motors can be remotely controlled using the onboard serial port to connect directly to the Display Driver Module with its 16 character by 2 line display and keypad, or connected to your PC via the RS-232 module (40mm x 45mm). If you want to remotely control more motors or switch more relays that is no problem - daisy chain modules into the serial link and programme each of them with a unique code. The book explains how to do it.

The General I/O Module also has a serial port for daisy chaining into the same system. It has 3 CMOS or analogue inputs (connecting to the 10 bit analogue to digital converter), and two open drain outputs which can switch up to 2 amps at 100 volts DC for switching relays or motors, or which can be linked to on board inductors for generating step up voltages or TENS or muscle exercise waveforms.

Modules 1, 2 and 3 have a DC input socket and regulator. One input will run the whole chain.

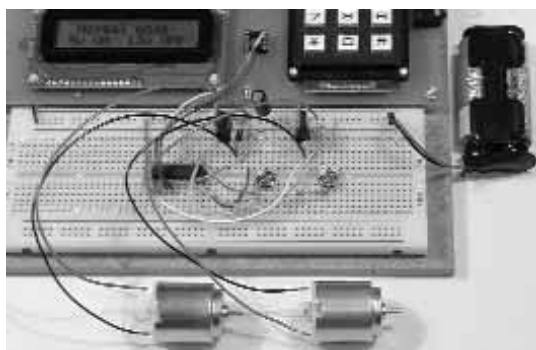For the latest information and pictures see our web site.



Experimenting with the PIC16F877

The second PIC book starts with the simplest of experiments to give us a basic understanding of the PIC16F877 family. Then we look at the 16 bit timer, efficient storage and display of text messages, simple frequency counter, use a keypad for numbers, letters and security codes, and examine the 10 bit A/D converter.

The PIC16F627 is then introduced as a low cost PIC16F84. We use the PIC16F627 as a step up switching regulator, and to control the speed of a DC motor with maximum torque still available. We study how to use a PIC to switch mains power using an optoisolated triac driving a high current triac. Finally we study how to use the PICs USART for serial communication to a PC.

NEXT MONTH

EPE CYBERVOX

So The Doctor's back! Dr Who's exploits are once more being told on BBC TV, during which he is again challenged by the Daleks, whose one aim in all of eternity is to "ExTeRmiNAtE!" everything in sight of their lethal sink plungers!

And what better way to commemorate the return of these Great Sagas than to provide you with the vocal armament to challenge the dastardly Daleks in their own language. Suspend your disbelief – next month we equip you with a Dalek voice emulator on behalf of humanity in these apocalyptic adventures. Here then is the EPE Cybervox, a linguistic cyborg challenger that is tunable to many Dalekesque dialects, all selectable at the twist of a few knobs. To this end, it has been furnished with the essential undulating vocal modulator, and a variable cavernous multi-spacial timeline echo delay such as befits a Time Lord's confrontation with the evil creatures inhabiting the asynchronastic parafundibulum.

LF and VLF CONVERTER

Britain, Ireland, France, Germany and Russia operate high-power broadcast transmitters in what is known as the longwave band covering 150kHz to 350kHz, an amateur band is centred on 136kHz and various other transmissions exist from 150kHz to below 10kHz where submarine communications are located. In the 1kHz to 20kHz region whistlers or howlers can be found – these are a natural electromagnetic phenomena caused by lightning around the world.

This simple converter will allow a high performance receiver to tune in to transmissions from zero to 350kHz. Previously published receivers from the Practical Radio Circuits series in the June '03 to Jan '04 issues are suitable, as are most communications receivers. A suitable aerial system is also detailed.

BACK TO BASICS - 4

• Doorchime • Electronic Dice



MULTI-CLAP SWITCH

Consider that an estimated 5% of all car drivers lock their keys in their cars every year. Add to this the (unknown) number of people who find themselves without their house keys, or various other keys or access codes. Then imagine what a secret knock-knock code switch could achieve.

Tap a code on your car window, and the door locks open – or knock on your front door in a predetermined sequence, and you regain access to your home. All this the Multi-Clap Switch can do, albeit more basically.

In brief, the Multi-Clap Switch may be activated with one to nine claps, as preferred. The same number of claps is required to switch it off again. This it does with more than the usual sensitivity. The precise "speed" of the claps may also be set, so that clapping either too fast or too slow will reset the switch.

NO ONE DOES IT BETTER



**DON'T MISS AN
ISSUE – PLACE YOUR
ORDER NOW!**

see page 434

Or take out a subscription and save money.

See page 448

JULY 2005 ISSUE ON SALE THURSDAY, JUNE 9



Quasar Electronics Limited
 PO Box 6935, Bishops Cleeve, Nottingham
 CM23 4WP
 Tel: 0870 246 1826
 Fax: 0870 460 1045
 E-mail: sales@quasarelectronics.com

Postage & Packing Options (Up to 2kg gross weight): **UK standard 3-7 Day Delivery** – £3.95; **UK Mainland Next Day Delivery** – £8.95; **Europe (EU)** – £6.95; **Rest of World** – £9.95. **Order online for reduced price UK Postage!**
 We accept all major credit/debit cards. Make cheques/POs payable to Quasar Electronics Limited.
 Prices include 17.5% VAT. **MAIL ORDER ONLY.**
 Call now for our **FREE CATALOGUE** with details of over 300 high quality kits, projects, modules and publications.



QUASAR 0871 CREDIT CARD 717 7168 SALES

Helping you make the right connections!

PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £15.00
18VDC Power supply (PSU010) £19.95
Leads: Parallel (LDC136) £4.95 / **Serial (LDC441)** £4.95 / **USB (LDC644)** £2.95

NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows Software. ZIF Socket and USB Plug A-B lead not incl.

Kit Order Code: 3128KT – £34.95

Assembled Order Code: AS3128 – £44.95



Enhanced "PICALL" ISP PIC Programmer

Will program virtually ALL 8 to 40 pin PICs plus certain ATMEL AVR, SCENIX SX and EEPROM 24C devices. Also supports In System Programming (ISP) for PIC and ATMEL AVRs. Free software. Blank chip auto detect for super fast bulk programming. Requires a 40-pin wide ZIF socket (not included)

Assembled Order Code: AS3144 – £54.95

ATMEL 89xxx Programmer

Uses serial port and any standard terminal comms program. 4 LEDs display the status. ZIF sockets not included. Supply: 16VDC.

Kit Order Code: 3123KT – £29.95

Assembled Order Code: AS3123 – £34.95



NEW! USB & Serial Port PIC Programmer

USB/Serial connection. Header cable for ICSP. Free Windows software. See web-site for PICs supported. ZIF Socket and USB Plug A-B lead extra. 18VDC.

Kit Order Code: 3149KT – £34.95

Assembled Order Code: AS3149 – £49.95

Introduction to PIC Programming

Go from a complete PIC beginner to burning your first PIC and writing your own code in no time! Includes a 49-page step-by-step Tutorial Manual, Programming Hardware (with LED bench testing section), Win 3.11-XP Programming Software (will Program, Read, Verify & Erase), and a rewritable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). Connects to PC parallel port.

Kit Order Code: 3081KT – £14.95

Assembled Order Code: AS3081 – £24.95



ABC Maxi AVR Development Board

The ABC Maxi board has an open architecture design based on Atmel's AVR AT90S8535 RISC microcontroller and is ideal for developing new designs.

Features:

- 8Kb of In-System Programmable Flash (1000 write/erase cycles) • 512 bytes internal SRAM • 512 bytes EEPROM
- 8 analogue inputs (range 0-5V)
- 4 Opto-isolated Inputs (I/Os are bi-directional with internal pull-up resistors)
- Output buffers can sink 20mA current (direct i.e.d. drive) • 4 x 12A open drain MOSFET outputs • RS485 network connector • 2-16 LCD Connector
- 3-5mm Speaker Phone Jack
- Supply: 9-12VDC.

The ABC Maxi STARTER PACK includes one assembled Maxi Board, parallel and serial cables, and Windows software CD-ROM featuring an Assembler, BASIC compiler and in-system programmer.

Order Code ABCMAXISP – £99.95

The ABC Maxi boards only can also be purchased separately at £79.95 each.



Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU445 – £8.95

Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security.

4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learned by one Rx (kit includes one Tx but more available separately).

4 indicator LEDs.

Rx: PCB 77x85mm, 12VDC/6mA (standby).

Two & Ten Channel versions also available.

Kit Order Code: 3180KIT – £41.95

Assembled Order Code: AS3180 – £49.95



Computer Temperature Data Logger

Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 38x38mm. Powered

by PC. Includes one DS1820 sensor and four header cables.

Kit Order Code: 3145KT – £19.95

Assembled Order Code: AS3145 – £26.95

Additional DS1820 Sensors – £3.95 each



NEW! DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12VDC.

Kit Order Code: 3140KT – £39.95

Assembled Order Code: AS3140 – £49.95



Serial Port Isolated I/O Module

Computer controlled 8-channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130 x 100 x 30mm. Power: 12VDC/500mA.

Kit Order Code: 3108KT – £54.95

Assembled Order Code: AS3108 – £64.95




Infra-red RC 12-Channel Relay Board

Control 12 on-board relays with included infra-red remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm.

Supply: 12VDC/0-5A.

Kit Order Code: 3142KT – £41.95

Assembled Order Code: AS3142 – £51.95

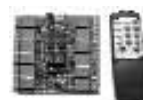

PC Data Acquisition & Control Unit

Monitor and log a mixture of analogue and digital inputs and control external devices via the analogue and digital outputs. Monitor pressure, temperature, light intensity, weight, switch state, movement, relays, etc. with the appropriate sensors (not supplied). Data can be processed, stored and the results used to control devices such as motors, sirens, relays, servo motors (up to 11) and two stepper motors.

Features

- 11 Analogue Inputs – 0-5V, 10 bit (5mV/step)
- 16 Digital Inputs – 20V max. Protection 1K in series, 5-1V Zener
- 1 Analogue Output – 0-2.5V or 0-10V. 8 bit (20mV/step)
- 8 Digital Outputs – Open collector, 500mA, 33V max
- Custom box (140 x 110 x 35mm) with printed front & rear panels
- Windows software utilities (3-1 to XP) and programming examples
- Supply: 12V DC (Order Code PSU203)

Kit Order Code: 3093KT – £69.95

Assembled Order Code: AS3093 – £99.95



Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

Hot New Kits This Summer!

Here are a few of the most recent kits added to our range. See website or join our email Newsletter for all the latest news.

NEW! EPE Ultrasonic Wind Speed Meter



Solid-state design wind speed meter (anemometer) that uses ultrasonic techniques and has no moving parts and does not need

calibrating. It is intended for sports-type activities, such as track events, sailing, hang-gliding, kites and model aircraft flying, to name but a few. It can even be used to monitor conditions in your garden. The probe is pointed in the direction from which the wind is blowing and the speed is displayed on an LCD display.

Specifications

- Units of display: metres per second, feet per second, kilometres per hour and miles per hour
- Resolution: Nearest tenth of a metre
- Range: Zero to 50mph approx.

Based on the project published in Everyday Practical Electronics, Jan 2003. We have made a few minor design changes (see web site for full details). Power: 9VDC (PP3 battery or Order Code PSU345).

Main PCB: 50 x 83mm.

Kit Order Code: 3168KT – **£34.95**

NEW! Audio DTMF Decoder and Display



Detects DTMF tones via an on-board electret microphone or direct from the phone lines through the onboard audio transformer. The

numbers are displayed on a 16-character, single line display as they are received. Up to 32 numbers can be displayed by scrolling the display left and right. There is also a serial output for sending the detected tones to a PC via the serial port. The unit will not detect numbers dialled using pulse dialling. Circuit is microcontroller based.

Supply: 9-12V DC (Order Code PSU345).

Main PCB: 55 x 95mm.

Kit Order Code: 3153KT – **£17.95**

Assembled Order Code: AS3153 – **£29.95**

NEW! EPE PIC Controlled LED Flasher



This versatile PIC-based LED or filament bulb flasher can be used to flash from 1 to 160

LEDs. The user arranges the LEDs in any pattern they wish. The kit comes with 8 superbright red LEDs and 8 green LEDs. Based on the Versatile PIC Flasher by Steve Challinor, *EPE Magazine* Dec '02. See website for full details. Board Supply: 9-12V DC. LED supply: 9-45V DC (depending on number of LED used). PCB: 43 x 54mm. Kit Order Code: 3169KT – **£10.95**

Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix)

FM Bugs & Transmitters

Our extensive range goes from discreet surveillance bugs to powerful FM broadcast transmitters. Here are a few examples. All can be received on a standard FM radio and have adjustable transmitting frequency.

MMTX' Micro-Miniature 9V FM Room Bug



Our best selling bug! Good performance. Just 25 x 15mm. Sold to detective agencies worldwide. Small enough to hide just about anywhere.

Operates at the 'less busy' top end of the commercial FM waveband and also up into the more private Air band. Range: 500m. Supply: PP3 battery. Kit Order Code: 3051KT – **£8.95**
Assembled Order Code: AS3051 – **£14.95**

HPTX' High Power FM Room Bug

Our most powerful room bug.

Very Impressive

performance. Clear and stable output signal thanks to the extra circuitry employed.

Range: 1000m @ 9V. Supply: 6-12V DC (9V PP3 battery clip supplied). 70 x 15mm.

Kit Order Code: 3032KT – **£9.95**

Assembled Order Code: AS3032 – **£17.95**

MTTX' Miniature Telephone Transmitter



Attach anywhere along phone line. Tune a radio into the signal and hear

exactly what both parties are saying. Transmits only when phone is used. Clear, stable signal. Powered from phone line so completely maintenance free once installed. Requires no aerial wire – uses phone line as antenna. Suitable for any phone system worldwide. Range: 300m. 20 x 45mm.

Kit Order Code: 3016KT – **£7.95**

Assembled Order Code: AS3016 – **£13.95**

3 Watt FM Transmitter



Small, powerful FM transmitter. Audio preamp stage and three RF stages deliver 3 watts of RF power. Can be used with the electret

microphone supplied or any line level audio source (e.g. CD or tape OUT, mixer, sound card, etc). Aerial can be an open dipole or Ground Plane. Ideal project for the novice wishing to get started in the fascinating world of FM broadcasting. 45 x 145mm.

Kit Order Code: 1028KT – **£22.95**

Assembled Order Code: AS1028 – **£34.95**

25 Watt FM Transmitter

Four transistor based stages with a Philips BLY89 (or equivalent) in the final stage. Delivers a mighty 25 Watts of RF power. Accepts any line level audio source (input sensitivity is adjustable). Antenna can be an open dipole, ground plane, 5/8, J, or YAGI configuration. Supply 12-14V DC, 5A. Supplied fully assembled and aligned – just connect the aerial, power and audio input. 70 x 220mm.

Order Code: 1031M – **£124.95**



Helping you make the right connections!

**CREDIT
CARD
SALES**
**0871
717
7168**

Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

500-in-1 Electronic Project Lab

This is the top of the range and is a complete electronics course taking you from beginner to 'A' level standard and beyond! It contains all the parts and instructions to assemble 500 projects. You get three comprehensive course books (total 368 pages) – *Hardware Entry Course*, *Hardware Advanced Course* and a micro-computer based *Software Programming Course*. Each book has individual circuit explanations, schematic and assembly diagrams. Suitable for age 12 and above. Order Code EPL500 – **£149.95**

30, 130, 200 and 300-in-1 project labs also available – see website for details.

Number 1 for Kits!

With over 300 projects in our range we are the UK's number 1 electronic kit specialist. Here are a few other kits from our range.

- 1046KT – 25W Stereo Car Booster £29.95
- 3087KT – 1W Stereo Amplifier £4.95
- 3105KT – 18W BTL mono Amplifier £9.95
- 3106KT – 50W Mono Hi-fi Amplifier £19.95
- 3143KT – 10W Stereo Amplifier £10.95
- 1011-12KT – Motorbike Alarm £12.95
- 1019KT – Car Alarm System £11.95
- 1048KT – Electronic Thermostat £9.95
- 1080KT – Liquid Level Sensor £6.95
- 3003KT – LED Dice with Box £7.95
- 3006KT – LED Roulette Wheel £8.95
- 3074KT – 8-Ch PC Relay Board £29.95
- 3082KT – 2-Ch UHF Relay £26.95
- 3126KT – Sound-Activated Relay £7.95
- 3063KT – One Chip AM Radio £10.95
- 3102KT – 4-Ch Servo Motor Driver £15.95
- 3155KT – Stereo Tone Controls £8.95
- 1096KT – 3-30V, 5A Stabilised PSU £32.95
- 3029KT – Combination Lock £6.95
- 3049KT – Ultrasonic Detector £13.95
- 3130KT – Infra-red Security Beam £12.95
- SG01MKT – Train Sounds £6.95
- SG10 MKT – Animal Sounds £5.95
- 1131KT – Robot Voice Effect £9.95
- 3007KT – 3V FM Room Bug £6.95
- 3028KT – Voice-Activated FM Bug £12.95
- 3033KT – Telephone Recording Adpt £9.95
- 3112KT – PC Data Logger/Sampler £18.95
- 3118KT – 12-bit Data Acquisition Unit £52.95
- 3101KT – 20MHz Function Generator £69.95

www.quasarelectronics.com



Secure Online Ordering Facilities ● Full Product Listing, Descriptions & Photos ● Kit Documentation & Software Downloads

STORE YOUR BACK ISSUES ON MINI CD-ROMS



**VOL 11
NOW AVAILABLE**

**ONLY
£14.45 each**
including VAT
and p&p



A great way to buy *EPE* Back Issues – our mini CD-ROMs contain back issues from our *EPE Online* website plus bonus articles, all the relevant PIC software and web links. Note: no free gifts are included. All this for just £14.45 each including postage and packing.

- VOL 1: BACK ISSUES** – January 1999 to June 1999
Plus some bonus material from Nov and Dec 1998
- VOL 2: BACK ISSUES** – July 1999 to December 1999
- VOL 3: BACK ISSUES** – January 2000 to June 2000
- VOL 4: BACK ISSUES** – July 2000 to December 2000
- VOL 5: BACK ISSUES** – January 2001 to June 2001
- VOL 6: BACK ISSUES** – July 2001 to December 2001
- VOL 7: BACK ISSUES** – January 2002 to June 2002
- VOL 8: BACK ISSUES** – July 2002 to December 2002
- VOL 9: BACK ISSUES** – January 2003 to June 2003
- VOL 10: BACK ISSUES** – July 2003 to December 2003
- VOL 11: BACK ISSUES** – January 2004 to June 2004

NOTE: These mini CD-ROMs are suitable for use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – www.adobe.com/acrobat)

WHAT IS INCLUDED

All volumes include the *EPE Online* editorial content of every listed issue, plus all the available **PIC Project Codes** for the PIC projects published in those issues.

Note: Some supplements etc. can be downloaded free from the Library on the *EPE Online* website at www.epemag.com. No advertisements are included in Volumes 1 and 2; from Volume 5 onwards the available relevant software for *Interface* articles is also included.

EXTRA ARTICLES – ON ALL VOLUMES

BASIC SOLDERING GUIDE – Alan Winstanley's internationally acclaimed fully illustrated guide. **UNDERSTANDING PASSIVE COMPONENTS** – Introduction to the basic principles of passive components. **HOW TO USE INTELLIGENT L.C.D.s**, by Julian Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules. **PhyzyyB COMPUTERS BONUS ARTICLE 1** – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown. **PhyzyyB COMPUTERS BONUS ARTICLE 2** – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown. **INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS** – A chapter from Intergraph's book that explains computer graphics technology. **FROM RUSSIA WITH LOVE**, by Barry Fox – Russian rockets launching American Satellites. **PC ENGINES**, by Ernest Flint – The evolution of Intel's microprocessors. **THE END TO ALL DISEASE**, by Aubrey Scoon – The original work of Rife. **COLLECTING AND RESTORING VINTAGE RADIOS**, by Paul Stenning. **THE LIFE & WORKS OF KONRAD ZUSE** – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

Note: Some of the **EXTRA ARTICLES** require WinZip to unzip them.

Order on-line from

www.epemag.wimborne.co.uk/shopdoor.htm
or www.epemag.com (USA \$ prices)
or by phone, Fax, E-mail or Post

BACK ISSUES MINI CD-ROM ORDER FORM

Please send me (quantity) BACK ISSUES CD-ROM **VOL 1**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 2**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 3**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 4**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 5**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 6**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 7**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 8**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 9**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 10**
Please send me (quantity) BACK ISSUES CD-ROM **VOL 11**
Price £14.45 each – includes postage to anywhere in the world.

Name

Address

..... Post Code

☐ I enclose cheque/P.O./bank draft to the value of £

☐ Please charge my Visa/Mastercard/Amex/Diners

Club/Maestro

£

Card No.

Card Security Code (The last 3 digits on or just under the signature strip)

Valid From Expiry Date

Maestro Issue No.

SEND TO: **Everyday Practical Electronics,
Wimborne Publishing Ltd.,**

408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax: 01202 874562.

E-mail: orders@epemag.wimborne.co.uk

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

We can supply back issues of *EPE* by post, most issues from the past three years are available. An *EPE* index for the last five years is also available at www.epemag.wimborne.co.uk or see order form below. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photocopy of any *one article* (or *one part* of a series) can be purchased for the same price. Issues from Nov. 98 are available on CD-ROM – see next page – and issues from the last six months are also available to download from www.epemag.com. Please make sure all components are still available before commencing any project from a back-dated issue.

DID YOU MISS THESE?

FEB '04

PROJECTS • PIC LCF Meter • Sonic Ice Warning • Jazzy Necklace • PIC Tug-of-War.
FEATURES • Surface Mount Devices • Circuit Surgery • Teach-In 2004 – Part 4 • Interface • Ingenuity Unlimited • Techno Talk • Net Work – The Internet Page.

MAR '04

PROJECTS • Bat-Band Converter • Emergency Stand-by Light • MIDI Health Check • PIC Mixer for RC Planes.
FEATURES • Teach-In 2004 – Part 5 • New Scientist CD-Rom Review • Circuit Surgery • Techno Talk • Ingenuity Unlimited • Practically Speaking • Net Work – The Internet Page.

APRIL '04

PROJECTS • EPE Experimental Seismograph Logger 1 • Infra-Guard Monitor • Loft Light Alarm • PIC Moon Clock.
FEATURES • USB To PIC Interface • Ingenuity Unlimited • Teach-In 2004 Part 6 • Interface • Techno Talk • Circuit Surgery • New Technology Update • Net Work – The Internet Page • Pull-Out – Semiconductor Classification Data.



MAY '04

PROJECTS • Beat Balance Metal Detector • In-Car Laptop PSU • Low-Frequency Wien Oscillator • EPE Experimental Seismograph Logger-2.
FEATURES • Coping With Lead-Free Solder • Teach-In 2004 – Part 7 • Ingenuity Unlimited • Techno Talk • Circuit Surgery • Practically Speaking • Pic-N'-Mix • Net Work – The Internet Page.

JUNE '04

PROJECTS • PIC Quickstep • Crafty Cooling • MIDI Synchronome • Body Detector Mk2.
FEATURES • Clinical Electrotherapy • Ingenuity Unlimited • Teach-In 2004 – Part 8 • Interface • Circuit Surgery • Techno Talk • PIC-N'-Mix • Net Work – The Internet Page.

JULY '04

PROJECTS • Portable Mini Alarm • Bongo Box • Hard Drive Warbler • EPE PIC Magnetometry Logger-1.
FEATURES • Making Front Panel Overlays • Practically Speaking • Teach-In 2004 – Part 9 • Ingenuity Unlimited • Circuit Surgery • Techno Talk • PIC-N'-Mix • Net Work – The Internet Page.

AUG '04

PROJECTS • EPE Scorer • Keyring L.E.D. Torch • Simple F.M. Radio • EPE PIC Magnetometry Logger-2.
FEATURES • PIC To PS/2 Mouse and Keyboard Interfacing • Techno Talk • Circuit Surgery • Teach-In 2004 – Part 10 • Interface • Ingenuity Unlimited • PIC-N'-Mix • Net Work – The Internet Page.

SEPT '04

PROJECTS • EPE Wart Zapper • Radio Control Failsafe • Rainbow Lighting Control • Alphamouse Game.
FEATURES • Light Emitting Diodes – Part 1 • High Speed Binary-To-Decimal For PICs • Practically Speaking • Ingenuity Unlimited • Techno Talk • Circuit Surgery • PIC-N'-Mix • Network – The Internet Page.



OCT '04

PROJECTS • EPE Theremin • Smart Karts – Part 1 • Volts Checker • Moon and Tide Clock Calendar.
FEATURES • Light Emitting Diodes – 2 • Circuit Surgery • Interface • Ingenuity Unlimited • Techno Talk • PIC-N'-Mix • Network – The Internet Page • ROBOTS – Special Supplement

NOV '04

PROJECTS • Thunderstorm Monitor • M.W. Amplitude Modulator • Logic Probe • Smart Karts - 2.
FEATURES • Light Emitting Diodes-3 • Floating Point Maths for PICs • Ingenuity Unlimited • PE 40th Anniversary • Circuit Surgery • Techno Talk • PIC-N'-Mix • Net Work – The Internet Page.

DEC '04

Photocopies only

PROJECTS • Super Vibration Switch • Versatile PIC Flasher • Wind Direction Indicator • Smart Karts - 3.
FEATURES • Light Emitting Diodes-4 • Ingenuity Unlimited • Circuit Surgery • Interface • PIC 'N' Mix • Techno Talk • Net Work – The Internet Page • INDEX Vol. 33.

JAN '05

PROJECTS • Speed Camera Watch • Gate Alarm • Light Detector • Smart Karts - 4.
FEATURES • Practically Speaking • 32-Bit Signed Integer Maths for PICs • Ingenuity Unlimited • Circuit Surgery • Techo Talk • PIC 'N' Mix • Picoscope 3205 Review • Net Work – The Internet Page

FEB '05

PROJECTS • PIC Electric MK2 Pt1 • Sneaky • Sound Card Mixer • Smart Karts - 5.
FEATURES • Interface • Circuit Surgery • Ingenuity Unlimited • Techno Talk • PIC 'N' Mix • E-Blocks and Flowcode V2.0 Reviews • Net Work – The Internet Page

MAR '05

PROJECTS • Cat Flap • Stereo Headphone Monitor • PIC Electric Mk2 Pt2 • Smart Karts - 6 • Bingo Box.
FEATURES • TK3 Simulator and PIC18F Upgrade • Circuit Surgery • Ingenuity Unlimited • Techno Talk • PIC 'N' Mix • Practically Speaking • Net Work – The Internet Page



APR '05

PROJECTS • Spontaflex Radio Receiver • Safety Interface • Fridge/Freezer Door Alarm • Smart Karts - 7.

FEATURES • Back To Logic Basics - 1 • Circuit Surgery • Ingenuity Unlimited • Interface • PIC18F Microcontroller Family Introduction • Techno Talk • Net Work – The Internet Page

MAY '05

PROJECTS • Crossword Solver • DAB Radio Aerial • 20W Amplifier Module • Smart Karts - 8 • Water Level Detector • Burglar Alarm

FEATURES • Back To Logic Basics - 2 • Circuit Surgery • Ingenuity Unlimited • Passive Component Testing • Practically Speaking • Techno Talk • Net Work – The Internet Page

BACK ISSUES ONLY £3.50 each inc. UK p&p.

Overseas prices £4 each surface mail, £5.50 each airmail.

We can also supply issues from earlier years: 2000 (except Feb., Mar., July, Oct.), 2001 (except Feb., May, Aug., to Nov.), 2002 (except Feb., June, Aug. to Nov.), 2003 (except June), 2004 (except Dec). Where we do not have an issue a photocopy of any *one article* or *one part* of a series can be provided at the same price.

ORDER FORM – BACK ISSUES – PHOTOCOPIES – INDEXES

- ☐ Send back issues dated
☐ Send photocopies of (article title and issue date)
☐ Send copies of last five years indexes (£3.50 for five inc. p&p – Overseas £4 surface, £5.50 airmail)

Name

Address

Tel:

☐ I enclose cheque/P.O./bank draft to the value of £

☐ Please charge my Visa/Mastercard/Amex/Diners Club/Switch £

Switch Issue No.

Card No.

Valid From Card Expiry Date Card Security Code
 (The last 3 digits on or just under the signature strip)

SEND TO: Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax: 01202 874562.

E-mail: orders@epemag.wimborne.co.uk On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

M06/05

MAIL ORDER ONLY • CALLERS BY APPOINTMENT

EPE PROJECT PICS

Programmed PICs for *EPE Projects
12C508/9 - £3.90; 16F627/8 - £4.90
16C84/16F84/16C71 - £5.90
16F876/877 - £10.00
All inc. VAT and Postage
(*Some projects are copyright)

EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847£63.95

PIC PIPE DESCALER

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave. Kit includes case, P.C.B., coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor.



KIT 868 £22.95 POWER UNIT.....£3.99

MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION



Plug-in power supply £4.99

KIT 867.£19.99

KIT + SLAVE UNIT.£32.50

WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

KIT 856.£28.00

★ TENS UNIT ★

DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

KIT 866. . Full kit including four electrodes £32.90

Set of 4 spare electrodes £6.50

1000V & 500V INSULATION TESTER



Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms.

Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

KIT 848.£32.95

EPE TEACH-IN 2000

Full set of top quality NEW components for this educational series. All parts as specified by EPE. Kit includes breadboard, wire, croc clips, pins and all components for experiments, as listed in introduction to Part 1.

*Batteries and tools not included.

TEACH-IN 2000 -

KIT 879 £44.95
MULTIMETER £14.45

SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

KIT 849£16.99



12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMs at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790£29.90

SUPER BAT DETECTOR

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE 20kHz-140kHz NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full-bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.

KIT 861£34.99

ALSO AVAILABLE Built & Tested. . .£48.99




68000 DEVELOPMENT TRAINING KIT

- NEW PCB DESIGN
- 8MHz 68000 16-BIT BUS
- MANUAL AND SOFTWARE
- 2 SERIAL PORTS
- PIT AND I/O PORT OPTIONS
- 12C PORT OPTIONS

KIT 621

£99.95

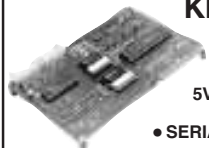- ON BOARD 5V REGULATOR
- PSU £6.99
- SERIAL LEAD £3.99



Stepping Motors

MD100...Std 100 step...£9.99

MD200...200 step...£12.99

MD24...Large 200 step...£22.95



MOSFET MKII VARIABLE BENCH POWER SUPPLY 0-25V 2.5A

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845£64.95

ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS



- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

KIT 812.£15.00

SIMPLE PIC PROGRAMMER

KIT 857... £12.99

Includes PIC16F84 chip disk, lead, plug, p.c.b., all components and instructions

Extra 16F84 chips £3.84
Power Supply £3.99

PIC LCD DISPLAY DRIVER

16 Character x 2 Line display, pcb, programmed PIC16F84, software disk and all components to experiment with standard intelligent alphanumeric displays. Includes full PIC source code which can be changed to match your application.

KIT 860.....£19.99

- Learn how to drive the display and write your own code.
- Ideal development base for meters, calculators, counters, timers --- just waiting for your application!
- **Top quality display** with industry standard driver, data and instructions

PIC STEPPING MOTOR DRIVER

PCB with components and PIC16F84 programmed with demonstration software to drive any 4 phase unipolar motor up to 24 Volts at 1 Amp. **Kit includes 100 Step Hybrid Stepping Motor** Full software source code supplied on disc.

Use this project to develop your own applications. PCB allows simple PIC programmer SEND software to be used to reprogram chip.

KIT 863.....£18.99

8 CHANNEL DATA LOGGER

From Aug/Sept. 99 *EPE*. Featuring 8 analogue inputs and serial data transfer to PC. Magenta redesigned PCB - LCD plugs directly onto board. Use as Data Logger or as a test bed for developing other PIC16F877 projects. Kit includes lcd, prog. chip, PCB, Case, all parts and 8 x 256k EEPROMs

KIT 877.....£49.95

PIC16F84 MAINS POWER CONTROLLER & 4 CHANNEL LIGHT CHASER / DIMMER

- Zero Volt Switching
- Opto-Isolated 5 Amp **HARD FIRED TRIACS**
- 12 Way keypad Control

- With program source code disk.
- Chase Speed and dimming potentiometer controls.
- Reprogram for other applications

KIT 855.....£39.95

PIC TUTOR 1 *EPE MARCH APRIL MAY 98* PIC16F84 STARTER SERIES

The original PIC16F84 series by John Becker. Magenta s Tutor board has individual switches and leds on all portA and PortB lines, plus connectors for optional 4 digit seven segment led display, and 16 x 2 intelligent lcd. Written for newcomers to PICs this series. Disk has over 20 tutorial programs. Connect to a PC parallel port, send, run, and experiment by modifying test programs - Then Write and Program your Own

KIT 870... £27.95, Built...£42.95


16x2 LCD..£7.99. LED display..£6.99. 12VPSU..£3.99

SUPER PIC PROGRAMMER

Magenta s original parallel port programmer. Runs with downloaded WINDOWS 95 - XP software. Use standard Microchip .HEX files. Read/Prog/Verify wide range of 18,28, and 40 pin PICs. Including 16F84/876/877, 627/8, (Inc. A versions) + 16xx OTPs.

KIT 862... £29.99 Power Supply £3.99

ICEBREAKER

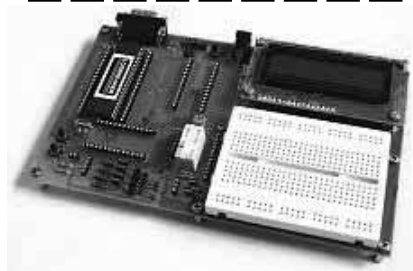

PIC Real Time In-Circuit Emulator

- ICEbreaker uses PIC16F877 in-circuit debugger.
- Links to standard PC Serial port (lead supplied).
- Windows (95 to XP) Software included
- Works with MPASM assembler
- 16 x 2 LCD display, Breadboard, Relay, I/O devices and patch leads.

Featured in *EPE Mar 00* Ideal for beginners & experienced users.

Programs can be written, downloaded, and then tested by single-stepping, running to breakpoints, or free run at up to 20Mhz.

Full emulation means that all ports respond immediately - reading and driving external hardware. Features include: Run; set Breakpoint; View & change registers, EEPROM, and program memory; load program; watch window registers.

KIT 900...£34.99 With serial lead & software disk, PCB, Breadboard, PIC16F877, LCD, all components and patch leads.
POWER SUPPLY - £3.99 STEPPING MOTOR 100 Step £9.99

20W Amp. Module

EPE April 05 -- Superb Magenta Stereo/Mono Module


Wide bandwidth Low distortion 11W/channel Stereo 20W Mono True (rms) Real Power

8 to 18V supply. Short Circuit & Overheat Protected.

Stable Reliable design


Latest Technology IC with local feedback gives very high performance.

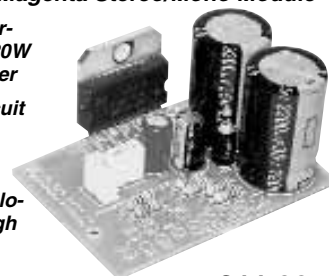KIT 914 (all parts & heatsink for stereo or mono) **£11.90**



Magenta BrainiBorg

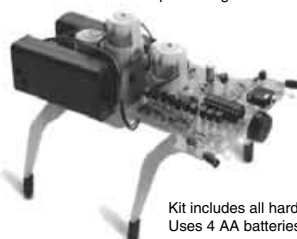A super walking programmable robot with eyes that sense obstacles and daylight: **BrainiBorg** comes with superb PC software CD (*WIN95+ & XP*) and can be programmed to walk and respond to light and obstacles on any smooth surface.



CD contains illustrated constructional details, operating principles, circuits and a superb **Educational Programming Tutorial**.

Test routines give real-time scope traces of sensor and motor signals. Connects to PC via **SERIAL** port with the lead supplied.

Kit includes all hardware, components, 3 motor/gearboxes. Uses 4 AA batteries (not supplied). *An Ideal Present!*

KIT 912 Complete Kit with CD rom & serial lead **£49.99**

KIT 913 As 912 but built & tested circuit board **£58.95**

EPE PIC Tutorial

EPE Apr/May/Jun 03 and PIC Resources CD

- Follow John Becker s excellent PIC toolkit 3 series.
- Magenta Designed Toolkit 3 board with printed component layout, green solder mask, places for 8,18, 28 (wide and slim), and 40 pin PICs. and Magenta extras.
- 16 x 2 LCD, PIC chip all components and sockets included.

KIT 880 (with 16F84) **£34.99**, built & tested **£49.99**

KIT 880 (with 16F877) **£39.99**, built & tested **£55.99**

EPE TEACH-IN 2004

THE LATEST NOV 03 SERIES

All parts to follow this new Educational Electronics Course.

Inc. Breadboard, and wire, as listed on p752 Nov. Issue.

KIT 920.....£29.99

Additional Parts as listed in misc. Section (less RF modules, Lock, and Motor/g.box)

Reprints: £1.00 per part.

KIT921.....£12.99

MAGENTA BRAINIBOT I & II

- Full kit with ALL hardware and electronics.
- As featured in *EPE Feb 03* (KIT 910)
- Seeks light, beeps, and avoids obstacles
- Spins and reverses when cornered
- Uses 8 pin PIC chip
- ALSO KIT 911 - As 910 *PLUS* programmable from PC serial port leads and software CD included.

KIT 910....£16.99 **KIT 911....£24.99**



MAGENTA

All prices include VAT. Add £3.00 p&p. Next day £6.99

042005



Station Road, Cullercoats,
Tyne & Wear, NE30 4PQ

Prices Exclude Vat @17.5%
UK Carriage £2.50 (less than 1kg)
£5.50 greater than 1kg
Cheques / Postal orders payable to
ESR Electronic Components.

PLEASE ADD CARRIAGE & VAT TO ALL ORDERS



See Next / Last Months Ad. for
COMPONENT ACCESSORIES

4000 Series

4000B	0.27	74HC73	0.19	74LS122
4001B	0.27	74HC74	0.31	74LS123
4002B	0.19	74HC76	0.20	74LS126
4008B	0.23	74HC85	0.23	74LS132
4009UB	0.23	74HC86	0.22	74LS133
4010B	0.23	74HC107	0.40	74LS136
4011B	0.16	74HC123	0.33	74LS138
4012B	0.16	74HC125	0.26	74LS139
4013B	0.18	74HC126	0.26	74LS145
4014B	0.30	74HC132	0.26	74LS148
4015B	0.27	74HC133	0.34	74LS151
4016B	0.20	74HC137	0.30	74LS153
4017B	0.18	74HC138	0.26	74LS156
4018B	0.25	74HC139	0.31	74LS158
4019B	0.25	74HC151	0.31	74LS158
4020B	0.25	74HC153	0.30	74LS160
4021B	0.31	74HC154	0.85	74LS161
4022B	0.32	74HC157	0.40	74LS162
4023B	0.23	74HC158	0.23	74LS163
4024B	0.20	74HC160	0.24	74LS164
4025B	0.20	74HC161	0.28	74LS165
4026B	0.22	74HC162	0.28	74LS173
4027B	0.22	74HC163	0.26	74LS174
4028B	0.21	74HC164	0.23	74LS175
4029B	0.38	74HC165	0.35	74LS190
4030B	0.17	74HC173	0.38	74LS192
4035B	0.23	74HC174	0.28	74LS193
4040B	0.23	74HC175	0.35	74LS195
4041B	0.31	74HC193	0.40	74LS221
4042B	0.22	74HC193	0.40	74LS221
4043B	0.35	74HC240	0.32	74LS240
4044B	0.35	74HC241	0.37	74LS243
4045B	0.35	74HC244	0.40	74LS244
4046B	0.34	74HC245	0.34	74LS245
4047B	0.29	74HC251	0.30	74LS247
4048B	0.29	74HC253	0.25	74LS251
4049UB	0.20	74HC257	0.29	74LS257
4050B	0.20	74HC259	0.29	74LS259
4051B	0.22	74HC259	0.29	74LS259
4052B	0.22	74HC273	0.32	74LS266
4053B	0.22	74HC299	0.61	74LS273
4054B	0.56	74HC365	0.28	74LS279
4055B	0.34	74HC367	0.38	74LS283
4060B	0.22	74HC368	0.29	74LS365
4063B	0.41	74HC373	0.35	74LS367
4067B	0.27	74HC374	0.34	74LS368
4068B	0.20	74HC390	0.52	74LS373
4069UB	0.16	74HC393	0.36	74LS374
4070B	0.16	74HC393	0.36	74LS374
4071B	0.20	74HC393	0.36	74LS390
4072B	0.18	74HC393	0.36	74LS390
4073B	0.17	74HC393	0.36	74LS393
4074B	0.17	74HC393	0.36	74LS393
4075B	0.17	74HC393	0.36	74LS393
4076B	0.30	74HC4002	0.36	74LS4002
4077B	0.28	74HC4017	0.31	74LS4017
4078B	0.30	74HC4020	0.36	74LS4020
4081B	0.16	74HC4040	0.29	74LS4040
4082B	0.21	74HC4049	0.31	74LS4049
4085B	0.28	74HC4051	0.30	74LS4051
4086B	0.33	74HC4052	0.43	74LS4052
4093B	0.16	74HC4053	0.38	74LS4053
4094B	0.29	74HC4060	0.23	74LS4060
4098B	0.22	74HC4075	0.32	74LS4075
4099B	0.22	74HC4078	0.32	74LS4078
4502B	0.32	74HC4511	0.64	74LS4511
4503B	0.40	74HC4514	0.84	74LS4514
4508B	0.16	74HC4588	0.31	74LS4588
4510B	0.45	74HC4543	0.90	74LS4543

74 Series

7407

Linear ICs

AD524AD

AD548JN

AD590JH

AD592AN

AD595AC

AD620AN

AD625JN

AD633JN

AD648JN

AD645JN

AD711JN

AD712JN

AD736JN

AD797AN

AD811JN

AD817AN

AD820AN

AD822AN

AD829JN

AD830AN

AD847JN

AD969KCN

ADEL2020A

ADM222AN

ADM232AA

ADM485JN

ADM666AN

ADM690AN

ADM691AN

ADM695AN

ADM699AN

CA3046

CA3080E

ICL701CP

ICL702CP

ICL709CP

DG211CJ

DG141DPJ

ICL706CP

ICL709CP

ICL710CP

ICL711CP

ICL760SC

ICM7555

ICM7555

ICM7555

74 Series

7407

Linear ICs

AD524AD

AD548JN

AD590JH

AD592AN

AD595AC

AD620AN

AD625JN

AD633JN

AD648JN

AD645JN

AD711JN

AD712JN

AD736JN

AD797AN

AD811JN

AD817AN

AD820AN

AD822AN

AD829JN

AD830AN

AD847JN

AD969KCN

ADEL2020A

ADM222AN

ADM232AA

ADM485JN

ADM666AN

ADM690AN

ADM691AN

ADM695AN

ADM699AN

CA3046

CA3080E

ICL701CP

ICL702CP

ICL709CP

DG211CJ

DG141DPJ

ICL706CP

ICL709CP

ICL710CP

ICL711CP

ICL760SC

ICM7555

ICM7555

ICM7555

ICM7555

74 Series

7407

Linear ICs

AD524AD

AD548JN

AD590JH

AD592AN

AD595AC

AD620AN

AD625JN

AD633JN

AD648JN

AD645JN

AD711JN

AD712JN

AD736JN

AD797AN

AD811JN

AD817AN

AD820AN

AD822AN

AD829JN

AD830AN

AD847JN

AD969KCN

ADEL2020A

ADM222AN

ADM232AA

ADM485JN

ADM666AN

ADM690AN

ADM691AN

ADM695AN

ADM699AN

CA3046

CA3080E

ICL701CP

ICL702CP

ICL709CP

DG211CJ

DG141DPJ

ICL706CP

ICL709CP

ICL710CP

ICL711CP

ICL760SC

ICM7555

ICM7555

ICM7555

ICM7555

Editorial Offices:
EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
WIMBORNE PUBLISHING LTD, 408 WIMBORNE ROAD EAST,
FERNDOWN, DORSET BH22 9ND
Phone: (01202) 873872. Fax: (01202) 874562.

Email: enquiries@epemag.wimborne.co.uk
Web Site: www.epemag.co.uk
EPE Online (downloadable version of EPE): www.epemag.com
EPE Online Shop: www.epemag.wimborne.co.uk/shopdoor.htm
See notes on **Readers' Technical Enquiries** below – we regret lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:
408 Wimborne Road East, Ferndown, Dorset BH22 9ND
Phone: 01202 873872
Fax: 01202 874562
Email: epeads@wimborne.co.uk

Technology to The Rescue

The dreadful news late last year of the Asian tsunami and the devastation caused made the world realize just how vulnerable we are to natural disasters. Millions are spent, quite rightly, protecting us from terrorists and other extremists but it appears that, up till now, little has been done to warn of disasters of this type.

Following the Asian tsunami we heard news of a warning system in the Pacific ocean but, as the article by Mark Williamson in this issue shows, this system is far from comprehensive at present with over 30 sensor buoys still to be commissioned. The good news is that the United Nations have agreed to develop an early warning system for the Indian Ocean which could be ready within 18 months.

The loss of life warrants whatever the cost might be, with the lives of more than 250,000 people lost. How many lives could have been saved by an early warning is impossible to tell, but with two hours elapsing from the earthquake until the wave hit the coasts of India and Sri Lanka the number of lives saved would surely have been substantial. On an economic front the cost of rebuilding the infrastructure, of feeding, housing and caring for the injured etc., far outweighs the cost of implementing a warning system, which could be in the region of \$50m.

In the last 50 years there have been three major tsunamis. With the highly developed satellite systems now available, plus the terrestrial communications systems in place to warn of hurricanes etc., we do have the ability to use technology to potentially save hundreds of thousands of lives, and thankfully that should now be implemented in the devastated area.

Out of This World

On a lighter note this issue contains a very wide range of projects and features and we have similar plans for next month when you will find a Dalek "voice box" – PIC-based of course; no self-respecting alien would be complete without the odd microcontroller! We will also feature a very low frequency radio converter which will enable anyone to listen in on various long-wave transmissions, plus the whistlers or howlers generated by lightning around the world.

Don't miss out, place an order with your newsagent now (see page 434) or take out a subscription (see page 448) to make sure of getting your copy each month.



AVAILABILITY

Copies of EPE are available on subscription anywhere in the world (see opposite), from all UK newsagents (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yebo Electronics (S. Africa). EPE can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$14.99US (approx £8) per year available from www.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £16.50, 12 months £31, two years £57; Overseas: 6 months £19.50 standard air service or £28.50 express airmail, 12 months £37 standard air service or £55 express airmail, 24 months £69 standard air service or £105 express airmail. To subscribe from the USA or Canada see the last magazine page. Online subscriptions, for downloading the magazine via the Internet, \$14.99US (approx £8) for one year available from www.epemag.com. Cheques or bank drafts (in £ sterling only) payable to Everyday Practical Electronics and sent to EPE Subs. Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Maestro or Visa. (For past issues see the Back Issues page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £6.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Maestro and MasterCard accepted. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editor: MIKE KENWARD

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Administration: FAY KENWARD

Editorial/Admin: (01202) 873872

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) **Editors:**
CLIVE (MAX) MAXFIELD and ALVIN BROWN

READERS' TECHNICAL ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in EPE employ voltages that can be lethal. **You should not build, test, modify or renovate any item of mains powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.**

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see Shoptalk). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



Editorial Offices:
EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
WIMBORNE PUBLISHING LTD, 408 WIMBORNE ROAD EAST,
FERNDOWN, DORSET BH22 9ND
Phone: (01202) 873872. Fax: (01202) 874562.

Email: enquiries@epemag.wimborne.co.uk
Web Site: www.epemag.co.uk
EPE Online (downloadable version of EPE): www.epemag.com
EPE Online Shop: www.epemag.wimborne.co.uk/shopdoor.htm
See notes on **Readers' Technical Enquiries** below – we regret lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:
408 Wimborne Road East, Ferndown, Dorset BH22 9ND
Phone: 01202 873872
Fax: 01202 874562
Email: epeads@wimborne.co.uk

Technology to The Rescue

The dreadful news late last year of the Asian tsunami and the devastation caused made the world realize just how vulnerable we are to natural disasters. Millions are spent, quite rightly, protecting us from terrorists and other extremists but it appears that, up till now, little has been done to warn of disasters of this type.

Following the Asian tsunami we heard news of a warning system in the Pacific ocean but, as the article by Mark Williamson in this issue shows, this system is far from comprehensive at present with over 30 sensor buoys still to be commissioned. The good news is that the United Nations have agreed to develop an early warning system for the Indian Ocean which could be ready within 18 months.

The loss of life warrants whatever the cost might be, with the lives of more than 250,000 people lost. How many lives could have been saved by an early warning is impossible to tell, but with two hours elapsing from the earthquake until the wave hit the coasts of India and Sri Lanka the number of lives saved would surely have been substantial. On an economic front the cost of rebuilding the infrastructure, of feeding, housing and caring for the injured etc., far outweighs the cost of implementing a warning system, which could be in the region of \$50m.

In the last 50 years there have been three major tsunamis. With the highly developed satellite systems now available, plus the terrestrial communications systems in place to warn of hurricanes etc., we do have the ability to use technology to potentially save hundreds of thousands of lives, and thankfully that should now be implemented in the devastated area.

Out of This World

On a lighter note this issue contains a very wide range of projects and features and we have similar plans for next month when you will find a Dalek "voice box" – PIC-based of course; no self-respecting alien would be complete without the odd microcontroller! We will also feature a very low frequency radio converter which will enable anyone to listen in on various long-wave transmissions, plus the whistlers or howlers generated by lightning around the world.

Don't miss out, place an order with your newsagent now (see page 434) or take out a subscription (see page 448) to make sure of getting your copy each month.



AVAILABILITY

Copies of EPE are available on subscription anywhere in the world (see opposite), from all UK newsagents (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yebo Electronics (S. Africa). EPE can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$14.99US (approx £8) per year available from www.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £16.50, 12 months £31, two years £57; Overseas: 6 months £19.50 standard air service or £28.50 express airmail, 12 months £37 standard air service or £55 express airmail, 24 months £69 standard air service or £105 express airmail. To subscribe from the USA or Canada see the last magazine page. Online subscriptions, for downloading the magazine via the Internet, \$14.99US (approx £8) for one year available from www.epemag.com. Cheques or bank drafts (in £ sterling only) payable to Everyday Practical Electronics and sent to EPE Subs. Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Maestro or Visa. (For past issues see the Back Issues page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £6.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Maestro and MasterCard accepted. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editor: MIKE KENWARD

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Administration: FAY KENWARD

Editorial/Admin: (01202) 873872

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) **Editors:**
CLIVE (MAX) MAXFIELD and ALVIN BROWN

READERS' TECHNICAL ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in EPE employ voltages that can be lethal. **You should not build, test, modify or renovate any item of mains powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.**

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see Shoptalk). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



Super-Ear Audio Telescope

Tom Merryfield

Listen more clearly to those distant sounds



SUPER-EAR has been designed to incorporate a home-constructed parabolic element which boosts the sensitivity of an electret microphone for picking up sound at a distance. For example, as utilised in wildlife studies and, dare it be said, for eavesdropping on conversations from afar!

Because the microphone is securely held in copper tubing, impact and vibrational sounds through a barrier can also be detected to a certain extent. It was found with the prototype, that so long as a few precautions are followed, the results are comparable to those from a commercially produced device.

Parabolic Theory

Most readers will be familiar with satellite dish antennas in the shape of a parabola. Whereas a true parabola has a precise mathematical definition, most items approximating to this shape and with a reflective surface can be used to "catch" sound.

As shown in Fig.1, sound waves travelling more or less parallel from a distant source strike or "illuminate" the parabolic element. These in turn are re-directed to a focal point, X, at which the microphone is placed. In effect, this captures the targeted audio.

Although the focal point varies with different parabolas, the pick-up power of the microphone is considerably boosted since more sound waves are available from a particular source. The received input signal is then amplified as smoothly as possible by a sensitive circuit.

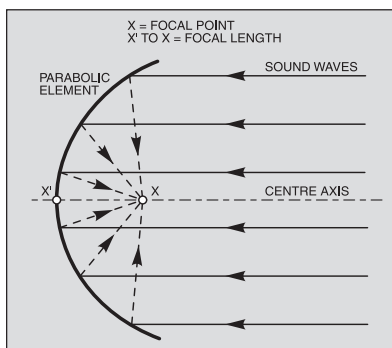


Fig.1. Properties of a true parabola

Circuit Description

In order to adequately amplify the input signal, the circuit consists of both pre-amplifier and audio amplifier stages. Referring to the full circuit diagram for the Super-Ear Audio Telescope in Fig.2, the electret microphone, MIC1, is powered

via resistor R1, which behaves as its load. The signal produced by MIC1 is a.c. coupled via capacitor C1 to the base of *npn* transistor TR1.

The network around TR1 forms the pre-amplifier stage. Resistors R2 to R5 bias it for linear amplification. The BC109C chosen is ideal for low noise audio applications such as this, offering more than adequate gain, although other general purpose high gain *npn* transistors will work in this design.

Any instability at this stage could distort signal processing throughout, hence the inclusion of capacitors C2 and C4. Capacitor C6 provides thermal compensation in the emitter circuit. Capacitor C3 and resistor R6 decouple the stage from disruptive power supply variations.

Audio Amplifier

Capacitor C5 couples the preamplified signal to level (Volume) control VR1, from where it is fed via C7 to IC1 input pin 3. The circuit around IC1 forms the audio amplifier stage. Capacitor C8 acts as an audio filter and the value quoted can be varied up to several nanofarads.

The LM386N audio amplifier i.c. has been chosen for IC1 because it is relatively easy to use and provides a smooth gain of over 200 (set by capacitor C9).

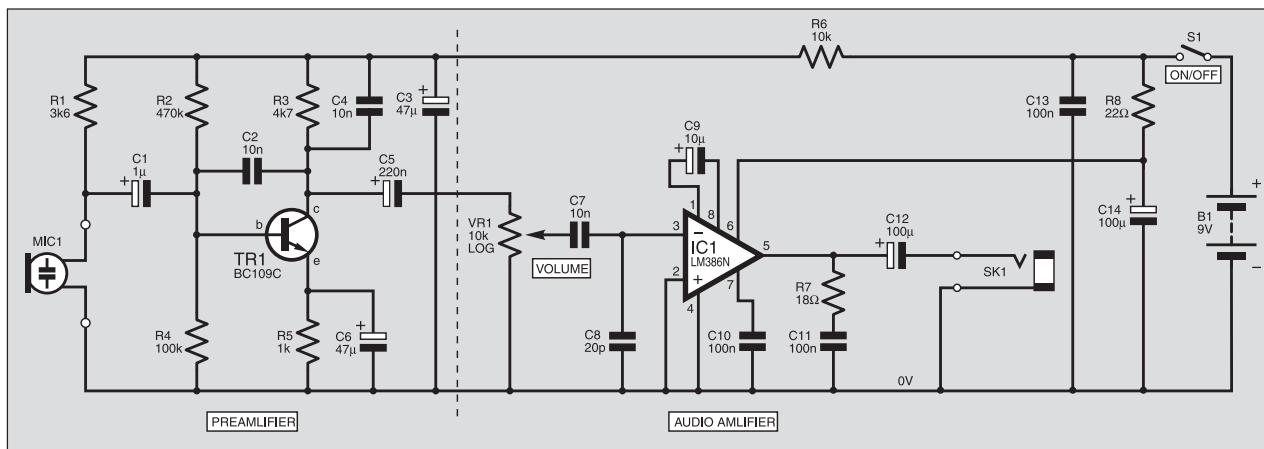




Fig.2. Complete circuit diagram for the Super-Ear Audio Telescope. This circuit is built on two circuit boards; preamplifier and audio amplifier

Table 1: Perception of Sound Intensity

Source	Decibels*	Perception
—	0	Silence
Rustling Leaves	10	Barely Audible
Soft Whisper	20	Quiet
Conversation	60	Audible
Factory	80	Fairly Loud
Construction Noise	110	Very Loud
Rock Concert	120	Pain Threshold

* Decibels, perceived level varies with frequency

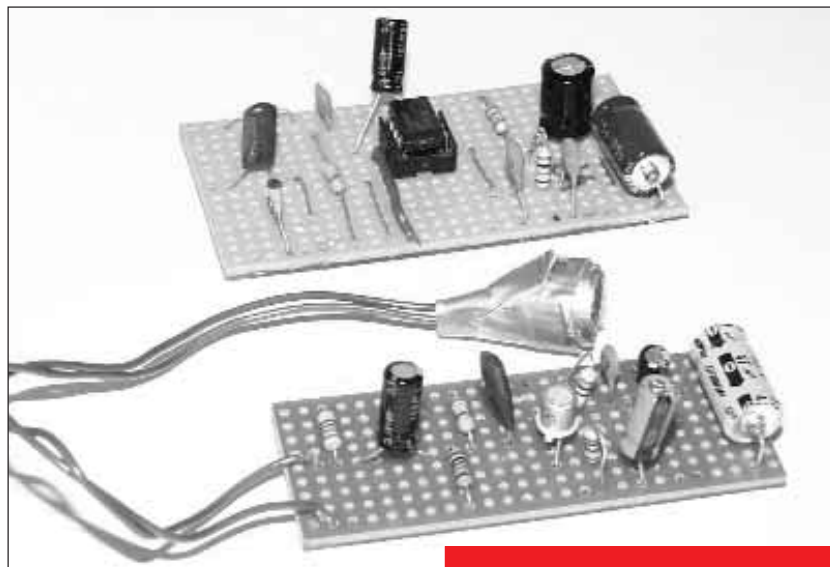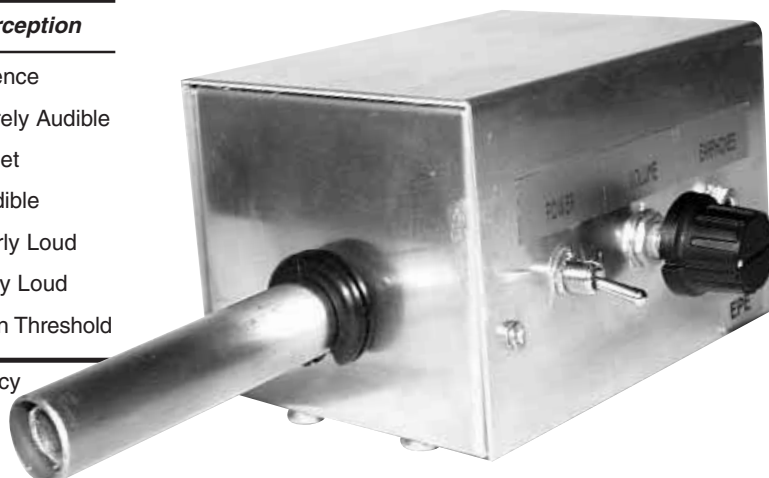Note that the human ear tends to perceive higher frequencies more easily



The two prototype circuit boards, with the tape-insulated Mic. between them. Differs slightly from the final unit

Most of the external components for IC1 are needed for stability. Capacitor C13 caters for variations in the supply voltage and is used on the main amplifier board, as opposed to the preamplifier board.

With IC1's output impedance being 64 ohms, Walkman-type headphones are preferable to speakers. This also avoids the problem of "telephony" which can hamper performance.

Construction

The prototype was built on two separate stripboards for several reasons. Firstly, both stages are isolated, which helps minimise problems with spurious feedback, whilst making fault-finding easier. Secondly, because the project is handheld, compactness is an issue. Two smaller circuit boards can be used to make the most of the available space.

The component layouts and track cutting details for the two stripboard assemblies are shown in Fig.3. Assemble the boards in the usual order of ascending component size, having first correctly cut the tracks where required.

Ensure that the electrolytic capacitors and the semiconductors are inserted the correct way round as shown. Use a socket for IC1, but do not insert the i.c. until the assembly has been completed and checked for accuracy.

Note that the electret microphone insert is also a polarised device. Its case is internally connected to one of its pins, to which the 0V connection should be made. The wiring to the microphone should not exceed about 140mm in length.

Testing

The circuit should be fully tested before housing it in a metal case. It is suggested that the main amplifier is tested first, without it being connected to the preamplifier.

When the amplifier is powered, touching the middle lug (wiper) of VR1 (or pin 3 of IC1) should produce a coarse buzz at

COMPONENTS

Resistors

R1	3k6
R2	470k
R3	4k7
R4	100k
R5	1k
R6	10k
R7	18Ω
R8	22Ω

All 0.25W 5% carbon film or better.

Potentiometer

VR1	10k rotary carbon, log
-----	------------------------

Capacitors

C1	1μ radial elect. 25V
C2, C7	10n polyester (2 off)
C3	47μ axial elect. 25V
C4	10n ceramic disc
C5	220n radial elect. 25V
C6	47μ radial elect. 25V
C8	20p ceramic disc
C9	10μ radial elect. 25V
C10, C11, C13	100n ceramic disc (3 off)

See
SHOP
TALK
page

C12	100μ radial elect. 25V
C14	100μ axial elect. 25V

Semiconductors

TR1	BC109C npn transistor
IC1	LM386N audio amplifier i.c.

Miscellaneous

MIC1	electret microphone insert
S1	min s.p.s.t. toggle switch
SK1	3.5mm jack socket
B1	9V battery (PP3 type), with clips

Stripboard 25 holes × 9 strips; stripboard 30 holes × 14 strips; control knob; parabolic dish (see text); metal case (110mm × 75mm × 60mm); copper tubing, standard type, approx. 15mm diameter × 100mm; mounting clip for tubing (see text); nuts and bolts as required; connecting wire; solder pins, solder, etc.

Approx. Cost
Guidance Only

£10
excl batt &
hardware

the output. There should also be a low level hum at the output, confirming that the amplifier is working. Once the amplifier has been proved, the preamplifier can be connected to it.

Key test voltages are shown in Table 2 and can be measured with a multimeter. Initially check if the microphone is picking anything up by gently tapping it and hearing the output. The prototype easily picked up ambient sound with VR1 set to less than a quarter of a turn.

Casing It

One problem encountered with circuits such as this is that they can easily pick up electrical interference, including odd (but strangely untraceable!) vibrations.

This was remedied by housing the circuit in a metal case, with the microphone situated in a copper tube (see later). Alternatively, plastic tubing with metal tape wrapped around it will suffice.

Before mounting the boards in the case, first drill the necessary holes in it and secure the copper tubing. As Fig.5 shows, the latter can be attached fairly robustly to the case with the help of a mounting clip as used in plumbing installations.

Table 2. Key Test Voltages

Pre-amp supply line	3-8V
Voltage across microphone	3-1V
TR1 base	0-2V
TR1 collector	3-1V
IC1 pin 5	4-5V

Assuming a 9V supply (error ±0.1V)

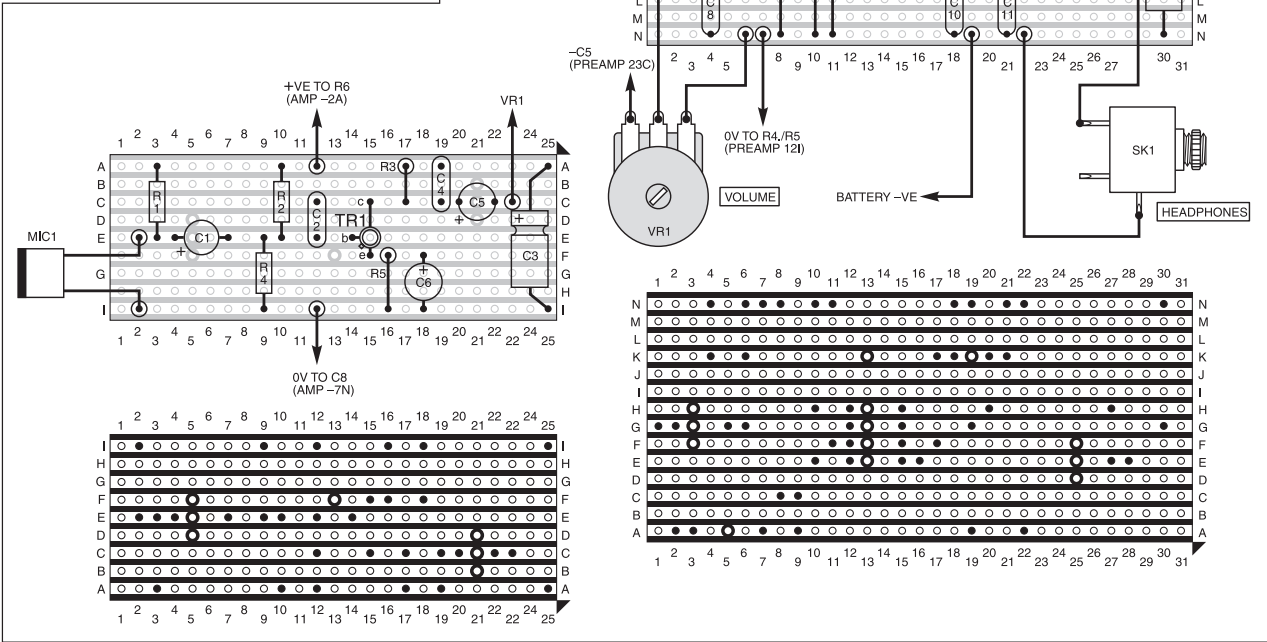


Fig.3. Super-Ear Audio Telescope stripboard component layouts, interwiring and details of breaks required in the copper tracks of the preamplifier and amplifier boards. The wiring and positioning of the two boards within the two-piece aluminium case is shown in the above photograph

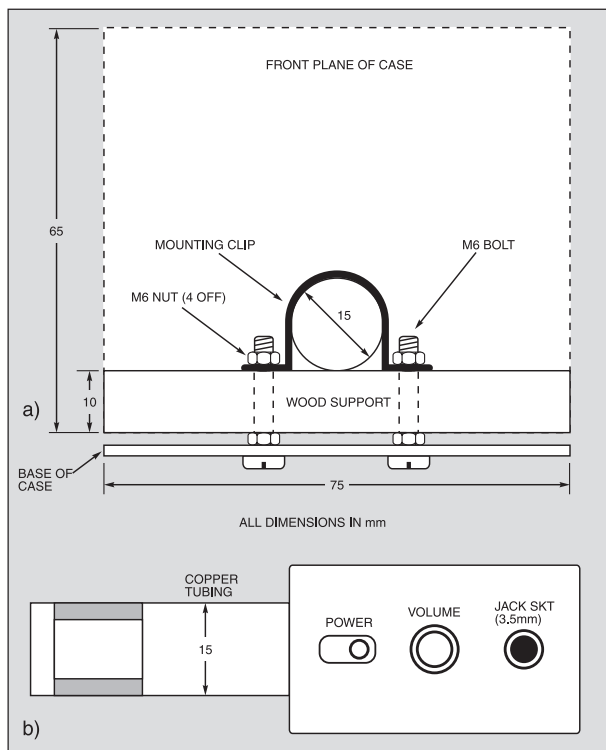


Fig.4. Securing the copper tubing, housing the mic. insert, inside the metal case (a) and (b) position of off-board components on one side panel

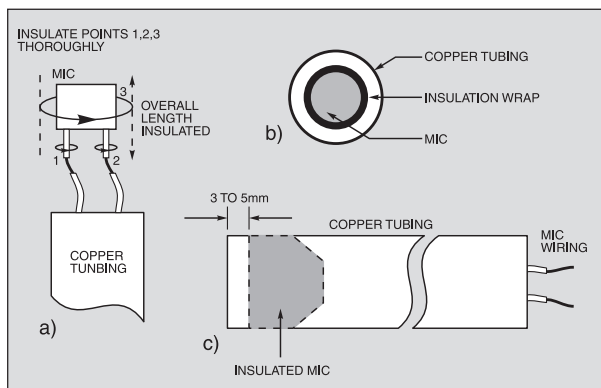


Fig.5. Insulating and wiring the microphone insert (a), end view showing insert "plugged" into the copper pipe (b) and the Mic. insert recessed in the copper tubing (c)



Electret Mounting

Because the circuit is extremely sensitive, anything picked up by the microphone can result in an ear-splitting whine dominating the output. This can be resolved by thoroughly insulating the microphone's bare metal surface using insulating tape. Handle the microphone

carefully to avoid damaging its pins. Solder the connecting cable to the pins and, as shown in Fig.5, wrap tape around each of them.

Push the cable through the copper tubing until it emerges from the other end. Now apply further rounds of tape over the microphone's case, leaving the pick-up

surface free. The microphone can then be eased into the tubing to around 3mm to 5mm short of the rim. For a snug fit and to prevent loosening, apply further rounds of tape.

Parabolic Matters

As mentioned earlier, almost anything concave and reflective to sound will boost the pick-up power of the microphone, it does not have to be a true parabola. The shape includes items such as aluminium bowls, old style car hub caps, and disused satellite dishes.

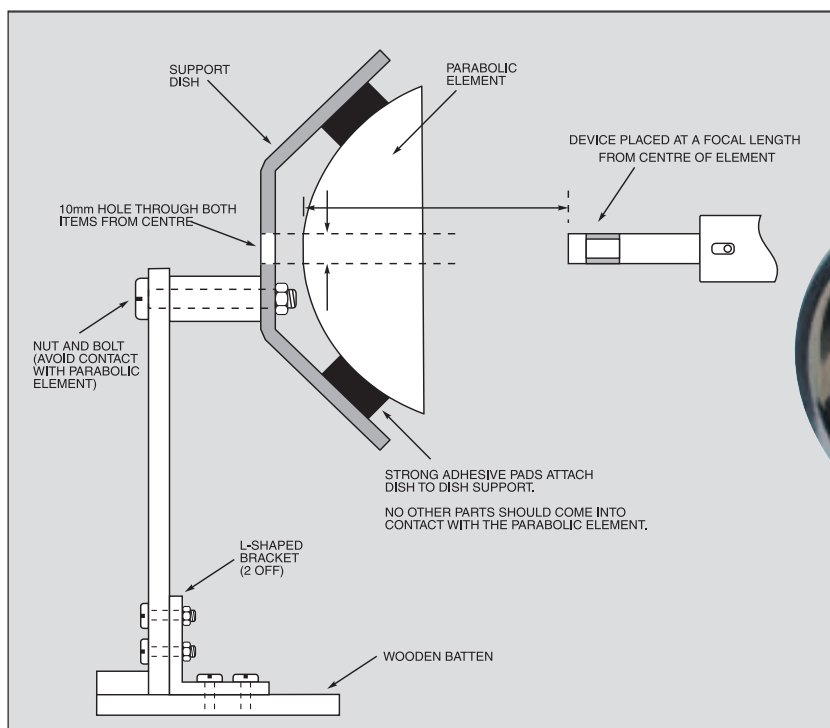


Fig.6. Suggested method for constructing a cradle/support for mounting a bigger more robust parabolic element (dish)



In Use

In use, some degree of experimenting is required providing ambient noise does not block out the targeted audio.

Point the reflector dish in the general direction of interest. As shown in Fig.6, hold the Super-Ear unit in front of the reflector. For optimum pick-up determine the focal length for the chosen "dish", i.e. the distance at which the microphone is held from the centre of the reflector.

A trial and error method sufficed for the prototype, with interesting results. Using this method, low level sounds (only just audible but unintelligible) were amplified using

Ideally Super-Ear should be suspended within a framework of struts to align with the centre and focal point of the dish for optimum audio pick-up

an aluminium bowl of diameter 200mm as the parabolic element, and having a focal point of 90mm.

Of course, the larger the dish diameter (typically up to 800mm) and the more parabolic the shape, the stronger the illumination. The gain of a

satellite dish antenna, for example, increases six decibels simply by doubling its size.

Because holding the parabolic element can muffle sound pick-up, it is worthwhile mounting it on a simple support via strong adhesive pads or glue such as Araldite.

Avoid using fixtures which involve drilling holes, except for the 10mm centre hole mentioned earlier. For bigger and heavier parabolic elements, the suggested method of home assembly as shown in Fig.6 can be used rather effectively.

Acknowledgements

The author offers many thanks to Ralph Turner and Dave Moran at Bradford College, for kindly assisting with this project. □

Drill a hole at the centre of the element equivalent to the diameter of the microphone, in this case 10mm. In terms of picking up sound this helps redirect the sound "illumination" relative to the size of microphone.

PLEASE ENSURE YOU TELEPHONE TO CHECK AVAILABILITY OF EQUIPMENT BEFORE ORDERING OR CALLING.

MISCELLANEOUS CLEARANCE STOCK

OSCILLOSCOPES	
TEKTRONIX 465B Dual Trace 100 MHz Delay fitted into 19in. rack frame	£125
HP 1740A Dual Trace 100 MHz delay (no lock)	£40
HP 1740A Dual Trace 100 MHz Delay	£60
HP 1740A Dual Trace 100 MHz Analogue Storage	£60
HP 1744A Dual Trace 100 MHz Analogue Storage	£60
PHILIPS PM3244 4 Ch. 100 MHz	£125
GOULD OS3000A Dual Trace 40 MHz	£40
TRIO CS1040 Dual Trace 40 MHz	£50
GOLDSTAR SS9202P Dual Trace 20 MHz	£50
WATSDU SS5702 Dual Trace 20 MHz	£40
KIKUSUI COS5020 Dual Trace 20 MHz	£40
POWER SUPPLIES	
FARNELL L308T 0-30V 0-1A Twice	£40
FARNELL L30AT 0-50V 0-500MA Twice	£30
FARNELL L130-1 0-30V 0-1A Twice Scuffy	£40
FARNELL L30-0 0-30V 0-2A Scuffy	£30
FARNELL L30-1 0-30V 0-1A Scuffy	£20
FARNELL L30B 0-30V 0-1A	£25
FARNELL L30AT 0-50V 0-500MA	£20
FARNELL C1 0-50V 0-1A - 2 Meters	£30
Farnell TP51 5V 1A ±15V 200MA	£35
COUTANT LB500 2 0-30V 0-5A - 2 Meters	£45
COUTANT LA200 2 0-30V 0-2A - 2 Meters	£35
COUTANT LQ700 0-15V 0-2A - Twice	£30
COUTANT LQ100 0-30V 0-1A Twice	£40
COUTANT LQ500 0-50V 0-500MA	£30
WEIR 781 0-30V 2A or 0-15V 4A	£30
WEIR 782 0-30V 2A or 0-15V 4A	£30
WEIR 4310 0-30V 1A - 5V 4A	£20
WEIR 400 0-0V 0.3A - 10V 1A	£20
WEIR 460 0-60V 0.3A - 20V 1A	£20
HP 6268B 0-40V 0-5A 2 Meters	£30
HP 6268B 0-10V 0-20A 2 Meters	£35
HP 6111A 0-20V 0-1A	£30
HP 6235A -6V 1A ±15V 200MA	£25
KINGSNILL 36V2C 0-36V 0-2A	£30
MARCONI T215B 0-30V 0-2A Twice	£30
LAMBDA 422FM 0-40V 0-1A Twice 4 Meters	£75
LAMBDA LK345A FM 0-60V 0-10A 2 Meters	£75
SYSTRON DONNER SHR40 2-0-40V 0-2A - 2 Meters	£25
SONENSON SRL60 4 0-60V 0-4A	£60
GRENSON BP14 0-5V 2.5A & ±15V 0.5A	£25
RS 813-991 2 x 5V 2.5A or 2 x 12V 1.5A or 2 x 5V 1A	£40
RS 208-197 Line Voltage Conditioner - Output 240V 0.65A	£40
POWER CONVERSION PLC1000 Line Cond. 1000VA	£50
HARLEY AUTOMATION IPPS5200 System Power Supply	£60
POWERLINE LAB007 0-30V AC 0.75A	£40

POWER SUPPLY Model 12030 0-20V 0-30A - On Wheels	£95
HARMER SIMMONS 50/25/110 Input 240V 10A Output 50V 25A	£100
CENTRONIC M100 Reguokit Input 240V 250 VA Output 240V 1000VA	£50
DRANETZ 606 Line Distribution Analyser	£35
WAYNE KERR B601 Radio Frequency Bridge	£25
FEEDBACK TFA607 Transfer Function Analyser	£25
WAYTEK 52 Data Multimeter	£60
GOULD SG200 RF Signal Generator	£20
CHATILLON Force Meter	£15
ALFRED E105 Variable Attenuator 4-9GHz	£10
CAMMETRIC 6 Decade Resistance Box	£15
SULLIVAN C8710 Precision 5 Decade Capacitor Box	£20
MARCONI 6033/3 Waveguide	£20
MARCONI 2169 Pulse Modulator	£20
MARCONI 2430A Frequency Meter 80MHz	£30
MARCONI 6950 RF Power Meter - No head	£35
MARCONI 6960 RF Power Meter - No head - Digital	£50
HP X382A Variable Attenuator Waveguide	£20
HP S316A Counter	£50
HP 5750A Storage Normalizer	£20
HP 907A Co-axial Sliding Load	£20
PROGRAMMA TM2 Timer	£20
RACAL 9009 Modulation Meter	£40
RACAL 9009A Modulation Meter	£50
TEXCAN SA50 100dB in 1dB steps	£15
BIRD Attenuator etc in box 30dB	£20
BIRD 8341-200 Coaxial Attenuator 20dB 40W 50ohm	£25
BIRD 61 Wattmeter 6 & 30W 50ohm 30-50MHz	£40
TELEONIC TTF95-5EE Tunable Band Pass Filter	£20
TELEONIC 190-3EE Tunable Band Reject Filter 125-250	£15
TELEONIC 35-3EE Tunable Band Reject Filter 60-126	£15
HELPER INST CML1 Snadder	£30
HELPER INST S103 Snadder 3	£30
SIXT100 Parallel to Serial Converter	£10
MICROMASTER LV	£40
DATAMAN S3 Programmer	£50
RS 424-103 Logic Pulser	£5
GLOBAL S01 Shortcircuit	£20
RS 180-7127 Conductivity Meter	£35
EAGLE DC30 Probe 30KΩ DC	£5
AVO 100AMP Shunt for AVO 8	£5
SOUTHERN CALIFORNIA BTRXMS-10 2000.0 MHz	£50
MOTOROLA R2001D Communication System Analyser	£250
WESTON 1149 Standard Cell 1.01859 ABS Volts at 20C	£10
MURHEAD A-6-B Resistance Box	£10
RACAL 9917A UHF Frequency Meter 10Hz-560 MHz	£45
RACAL 9917 UHF Frequency Meter 10Hz-560 MHz	£45
RACAL 9915M UHF Frequency Meter 10Hz-520 MHz	£30

RACAL 9901 Universal Counter Timer DC-50 MHz	£15
RACAL 9900 Universal Counter Timer 30 MHz DC-30 MHz	£15
WATTEK 106 VCO/VCO Generator	£20
HP 455A Power Meter - No lead no head	£15
HP 8015A Pulse Generator	£30
HP 403B AC Voltmeter	£15
DILOG PH415 Phase Rotation Indicator	£10
MAYWOOD D2000 Digital Indicator	£10
HP 3720A HPB Extender	£10
HATFIELD 2115 Attenuator 75ohm 100dB	£10
HATFIELD 2115R Attenuator 75ohm 100dB	£10
HATFIELD 2135 Attenuator 60ohm 100dB	£20
TEKTRONIX 1103 Tekprobe Power Supply	£10
SYSTRON DONNER 6243A Freq Counter 20Hz-1250 MHz	£35
LEVELL TG301 Function Generator 1 MHz Sine/Sq/Tri	£30
SOLARTON 7045 Digital Multimeter	£30
HP 3455A Levelling Amplifier	£15
HP 3455A Digital Voltmeter	£50
FEEDBACK FM610 Digital Frequency Meter	£25
FARNELL TM8 True RMS RF Millivoltmeter	£40
THURLBY 1503 Digital Multimeter	£15
SULLIVAN 6666 Milliohmeter	£15
K&L Tunable Bank Reject Filter	£15
BARR & STROUD EF4-01 Bank Pass Filter 1Hz-100KHz	£15
BARR & STROUD EF4-02 LPHF Filter 1Hz-100KHz	£15
FLUKE 8801A Digital Multimeter	£15
FLUKE 8802A Digital Multimeter	£25
ELECTRONIC VISUAL EV4000 TV Waveform Monitor	£20
TRACER NORTHERN TN1750	£30
RS 555-279 UV Exposure Unit	£15
MICRODYNE CORP. Receiver	£60
VARIAN V2L-6941F1 Travelling Wave Tube Amplifier	£50
MOORE READ SFC500/1 AUXR Static Frequency Converter	£20
120 Volts 400 Hz	£50
DRAGER 2101 Multi Gas Detector	£10
PHILIPS PM8237B Multipoint Data Recorder	£20
ENDECO 4417 Signal Conditioner X 2	£10
PULSETEK 132 DC Current Calibrator	£30
NI1038-014 Display with 1038-N10 Network Analyser	£50
MEGGER MJ4M2 Wind Up 1000V MΩhm	£30
METROHM 250V Pat Tester	£15
SULLIVAN AC1012 4 Decade Resistance Box 0.05%	£10
BRANDENBURGH Q20 Static Freq. Converter 110/240V input 50/60Hz Output 115V 400Hz 20VA	£40
NARDA 706 Attenuator	£10
ANALOGUE ASSOCIATES X800 Audio Amplifier 800watt (400w per Channel no DC Protection)	£80
WAG PC22 PCM Channel Generator	£30
SIVERS LAB 12400 - 18000 MHz	£10
SIVERS LAB 5212 2500 - 4000 MHz C264	£10
CHOPICO VS10 DC Standard 10V	£30

EXTRA SPECIAL OFFERS

H.G.P. 8560A Spectrum Analyser, 50Hz-2.9GHz	£3,250
H.P. 8569B Spectrum Analyser, 10MHz-22GHz	£1,500
MARCONI 2382 Spectrum Analyser, 200Hz-400MHz	£1,500
TEKTRONIX 2465A Oscilloscope, 4-ch, 350MHz	£750
TEKTRONIX 2246 Oscilloscope, 4-ch, 100MHz	£375
H.P. 8640A AM/FM Signal Gen, 500kHz-512MHz	£175

SPECIAL OFFERS

OSCILLOSCOPES	
LECROY 9400A dual trace, 170MHz, 5G/S	£500
LECROY 9400 dual trace, 125MHz	£400
TEKTRONIX 468 dual trace, 100MHz, digital storage	£300
TEKTRONIX 475 dual trace, 200MHz, delay sweep	£250
TEKTRONIX 465B dual trace, 100MHz, delay sweep	£250
TEKTRONIX 465 dual trace, 100MHz, delay sweep	£175
PHILIPS PM3217 dual trace, 50MHz, delay sweep	£150
THURLBY PL320QMD 0-30V 0-2A twice digital PSU	£160
H.P. 86312A 0-20V 0-2A Communications PSU	£200
H.P. 6626A Precision High Resolution PSU, 4 outputs, 0-7V 0-15A or 0-50V 0-0.5A twice; 0-16V 0-0.2A or 0-50V 0-2A twice	£500
CIRRUS CRL254 Sound Level Meter with calibrator 80-120dB LED	£95
WAYNE KERR B424 Component Bridge	£50
RACAL 9300 True RMS Voltmeter, 5Hz-20MHz usable to 60MHz, 10V-316V	£50
RACAL 9300B True RMS Voltmeter, 5Hz-20MHz usable to 60MHz, 10V-316V	£75
AVO DA116 Digital Avometer with battery and leads	£20
FARNELL LF4M Sine/Sq Oscillator, 10Hz-1MHz, low distortion TTL output amplitude meter	£75
FARNELL J3B Sine/Sq Oscillator, 10Hz-100kHz, low dist	£50
HEME 1000 LCD Clamp Meter, 0-1000A, in carrying case	£35
FLUKE 77 Multimeter 3 1/2 digit handheld with battery & leads	£45
KENWOOD VT776 2-Channel Multivoltmeter	£50
KENWOOD FL140 Wow and Flutter Meter	£50
KENWOOD FL180A Wow and Flutter Meter	£75
KENWOOD FL180M Wow and Flutter Meter, unused	£125
MARCONI 6960B Power Meter with 6920 head, 10MHz-20GHz	£450
SOLARTON 7150 DIMM 6 1/2-digit True RMS IEEE	£75
SOLARTON 7150 Plus As 7150 + temp. measurement	£100
IEEE Cables	£5
H.P. 3312A Function Gen, 0-1Hz-13MHz, AM/FM Sweep/Sq/Tri/Burst etc.	£200
H.P. 3310A Function Gen, 0.005Hz-6MHz, Sine/Sq/Tri Ramp/Pulse	£80
RACAL 9008 Automatic Modulation Meter, 1.5MHz-2GHz	£80
ISOLATING Transformer, input 250V, output 500VA, unused	£10
RACAL 1792 Receiver	£525

STEWART of READING

17A King Street, Mortimer, Near Reading RG7 3RS
Telephone: (0118) 933 1111. Fax: (0118) 933 2375
www.stewart-of-reading.co.uk

Open 9am-5.00pm Monday to Friday (other times by arrangement)



Used Equipment - GUARANTEED. Manuals supplied

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists.

Please check availability before ordering.

CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage

Very Interesting!

**The entire range of the 2005 Skytronic catalogue
available from Cricklewood Electronics**

This, Dutch Wholesaler's Catalogue, is now available to UK retail customers via Cricklewood Electronics and includes thousands of electronic items and components at bargain prices. The 432 page catalogue includes:
Plugs, Sockets, Cables, Switches, Speakers, Microphones, Components, Car Audio, Disco & PA & HiFi Equipment, CCTV Cameras & Recorders, Tools, Test Equipment, Inverters, Power Supplies, Electrical, Multimedia, Computer accessories, etc etc

Plugs, Sockets, Cables, Switches, Speakers, Microphones, Components, Car Audio, Disco & PA & HiFi Equipment, CCTV Cameras & Recorders, Tools, Test Equipment, Inverters, Power Supplies, Electrical, Multimedia, Computer accessories, etc etc



Catalogue & Price List free to shop-callers. To have it posted - please send £2.00 towards postage costs. (UK only).

Cricklewood Electronics Ltd

40-42 Cricklewood Broadway, London NW2 3ET. Tel: 020 8452 0161 Fax: 020 8208 1441

email: sales@cricklewoodelectronics.com

Visit our website @ www.cricklewoodelectronics.com

Radio Control Model Switcher

Ken Ginn

A radio controlled power switch for models and other devices



THIS radio controlled (RC) switcher has been designed for use on a spare RC transceiver channel to effect on/off power switching to an RC model or other device. The maximum switching current is set to about 1.0A, at a safe maximum supply voltage of 24V d.c. A larger current could be controlled with the additional use of a relay.

The point at which the unit's output switches state is known as the trigger point. Once the incoming pulse width exceeds a preset value, the switcher's output is switched on. If the pulse width is below this threshold, the output is switched off.

The author's previous designs for RC switchers included a number of monostables to control the circuit trigger timing. These circuits had no hysteresis and were prone to jitter at the trigger point.

The circuit presented here is PIC controlled and has been designed to avoid this problem, and to generally improve performance and reliability.

Circuit Description


The complete circuit diagram for the RC Switcher is shown in Fig.1. A PIC16F84A,

IC1, is the workhorse of the circuit, basically replacing the monostables used in previous designs.

The circuit's input, at PIC pin RB3, is normally biased low by resistor R1 and connected to the output of an existing RC servo control receiver. The output from such units is generally in the form

of a positive pulse whose duration varies between 1.0ms to 2.0ms, repeating about 50 times a second.

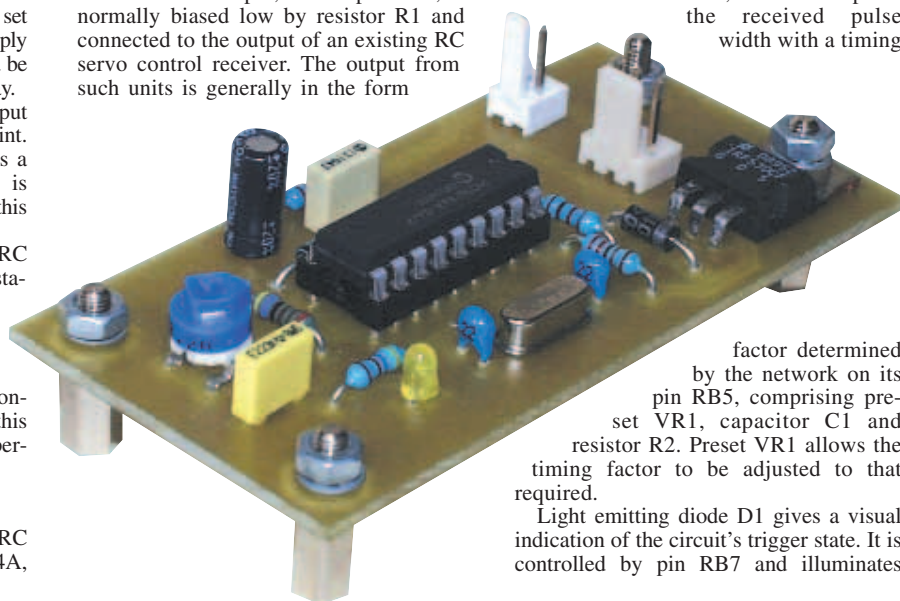In this switcher, the PIC compares the received pulse width with a timing



factor determined by the network on its pin RB5, comprising preset VR1, capacitor C1 and resistor R2. Preset VR1 allows the timing factor to be adjusted to that required.

Light emitting diode D1 gives a visual indication of the circuit's trigger state. It is controlled by pin RB7 and illuminates

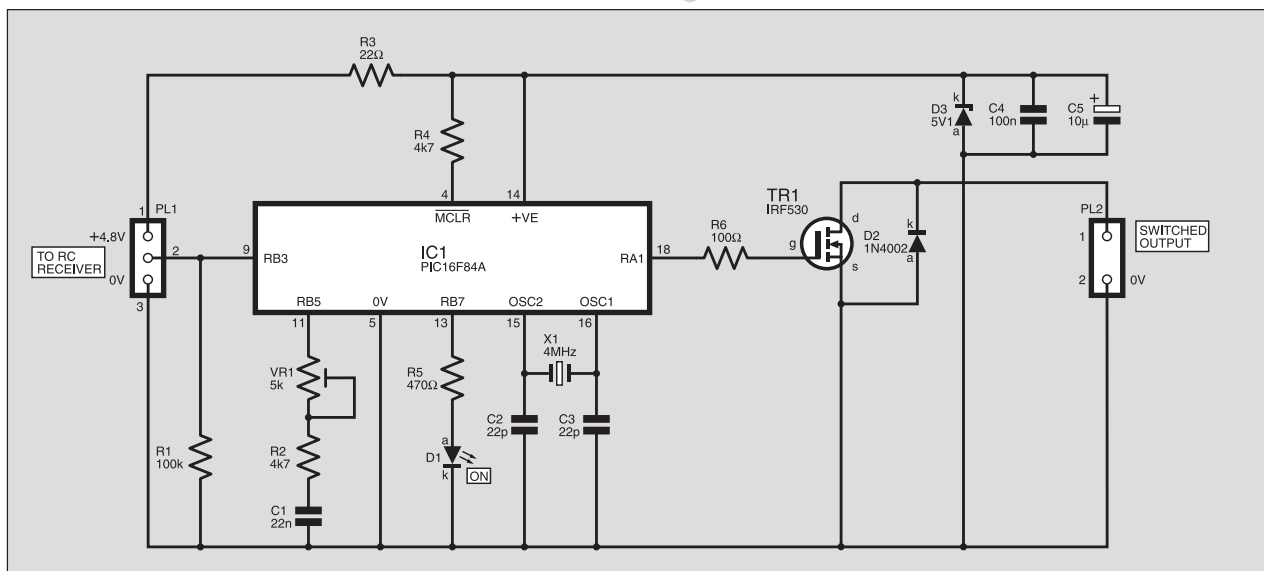


Fig.1. Complete circuit diagram for the Radio Control Model Switcher

when the trigger point has been exceeded by the incoming pulse width.

At the same time as i.e.d. D1 is turned on, the output at pin RA1 is taken high, turning on transistor TR1 via buffer resistor R6. Diode D2 inhibits back-e.m.f. generation when TR1's output is connected to an inductive load.

The circuit is powered by the existing RC receiver, which should provide approximately 4-8V if its supply is from a set of NiCad batteries. Resistor R3 and Zener diode D3 ensure that the voltage supplied to the PIC cannot exceed 5.1V, (a little below the 5.5V maximum that the PIC can accept safely). Capacitors C4 and C5 provide decoupling.

COMPONENTS

Resistors

R1	100k
R2, R4	4k7 (2 off)
R3	22Ω
R5	470Ω
R6	100Ω

All 0.25W 5% carbon film

See
SHOP
TALK
page

Potentiometer

VR1	5k min. round preset
-----	----------------------

Capacitors

C1	22n polyester or ceramic, 5mm pitch
C2, C3	22p ceramic disc, 5mm pitch (2 off)
C4	100n polyester or ceramic, 5mm pitch
C5	10μ radial elect, 35V

Semiconductors

D1	3mm i.e.d., colour of choice
D2	1N4002 rectifier diode
D3	5V1 Zener diode, 1.3W
TR1	IRF530 <i>n</i> -channel f.e.t.
IC1	PIC16F84A-04 microcontroller, pre-programmed (see text)

Miscellaneous

PL1	3-pin header plug, plus socket, 2.5mm pitch
PL2	2-pin header plug, plus socket, 2.5mm pitch
X1	4MHz crystal

Printed circuit board, available from the *EPE PCB Service*, code 504; 18-pin d.i.l. socket, TO220 transistor mounting kit; p.c.b. supports (4 off); connecting wire; solder, etc.

Approx. Cost
Guidance Only

£11

excl case &
batts

The PIC is operated at 4MHz, as set by crystal X1 and capacitors C2 and C3. Connections to and from the circuit are made by two p.c.b.-mounted connectors, PL1 and PL2.

Construction

Component and track layout details for the printed circuit board (p.c.b.) are shown in Fig.2. This board is available from the *EPE PCB Service*, code 504.

Assemble in the usual order of ascending component size. Use a socket for IC1, but do not insert the PIC until the circuit has been thoroughly checked for correctness. Ensure that transistor TR1, diodes D1 to D3, and capacitor C5 are correctly orientated. Since the circuit may be subject to a considerable amount of vibration in use, ensure components are mounted snug to the board.

Note that the tab of TR1 is connected internally to its drain (d). If the transistor is laid down and bolted to the board via the M3 mounting hole provided *ensure the tab is electrically isolated from the rest of the circuit*. Use a TO220 insulating kit, then check the insulation between the earth plane on the p.c.b. and the metal tab with a multimeter. This should read as open circuit.

Following assembly completion and visual checking, check the supply connections. Connect a multimeter, set to a medium resistance range, across the power supply connections to the board. This can be accomplished at pins 1 and 2 of connector PL1. The reading should be high in value. A reading of 22Ω (the value of resistor R2) will indicate a short circuit from one of the power tracks/pads to the earth plane on the p.c.b.

Setting up

Connect the circuit to a current-limited variable d.c. power supply, set to 5V and with a 20mA limit. If you do not have such a supply, temporarily use a one watt 100Ω resistor in series with the positive power lead from the 4-8V battery to limit the current. Check that when the unit is powered the current drawn is no greater than 10mA.

Adjust the wiper of preset VR1 to about the "two o'clock" position, to set the trigger response for a pulse width of about 1.5ms.

Connect the unit to your RC receiver servo output, and the unit's output to a load, such as a torch bulb for instance (see Fig.3).

Completed Switcher board. You must use a TO220 insulating kit when mounting the transistor on the p.c.b.

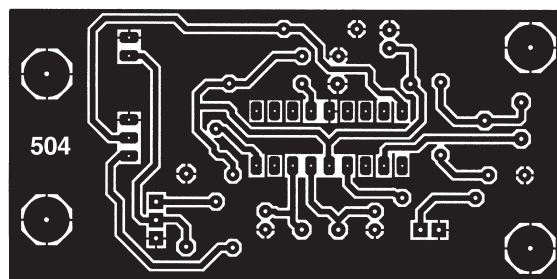
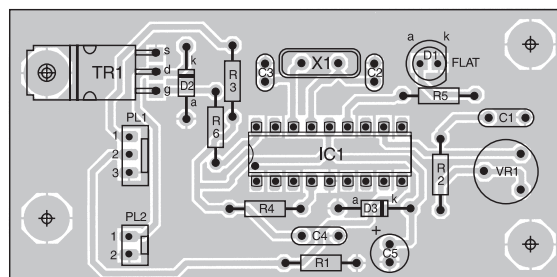
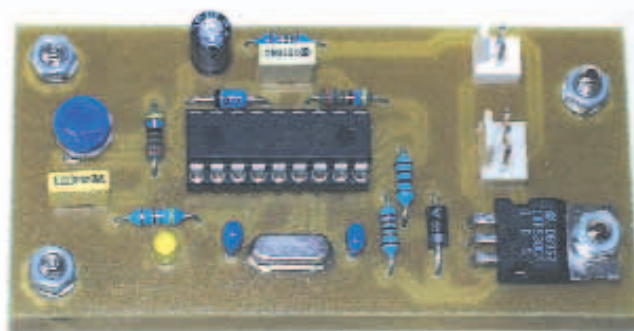


Fig.2. Printed circuit board topside component layout and full-size underside copper track master pattern for the Radio Control Model Switcher

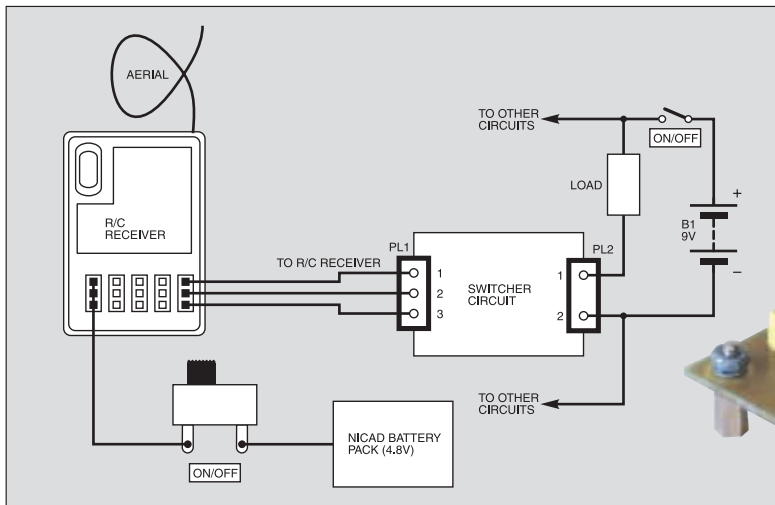


Fig.3. Test set-up showing connection of switcher unit to RC Receiver and switched load (bulb)

Connect the other side of the load to a separate power supply, preferably current limited to about 200mA. Switch on the transmitter, receiver plus switcher, and the load supply.

If the transmitter's control is a toggle switch, switch it back and forth and observe the torch bulb switching on and off. The i.e.d., D1, should respond in sympathy with the bulb switching. If the bulb does not respond, adjust preset VR1 until it does.

The unit has been designed to switch a maximum current of 1.0A. Should a larger switched current be needed, the output from TR1 could be connected to a relay and cause it to switch the required load.


Source Code

The PIC program measures the timing value of the positive pulses of the incoming signal from the receiver. This is compared to a value generated from the timing components VR1, R2 and C1. Should the pulse width be less than the trigger value set, then RA1 output is held low, and TR1 remains unswitched. If the pulse width is greater than the set trigger value, RA1 goes high and turns on TR1 and its load.

Once a change in pulse width value has been detected, there is a built in delay of 200ms. Only following that delay does out-

put RA1 change state. This provides a degree of hysteresis, so avoiding the equivalent of switch bounce.

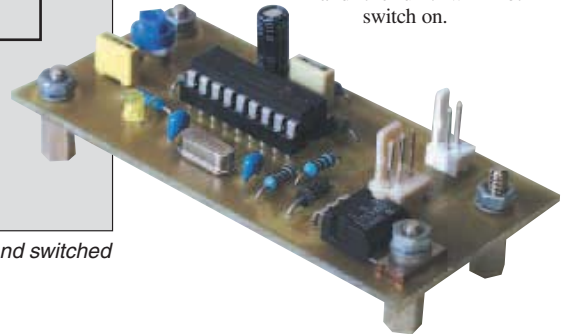The program also takes account not only of a signal not being received, but also of it remaining high, due in either case to a fault in the receiver. In these situations the Switcher will switch off. The circuit only sees a valid pulse width of between 700µs and 3.0ms. Anything outside this window is regarded as an invalid pulse and the unit will not switch on.



Resources

Software, including source code files, for the PIC microcontroller is available on 3.5-inch disk from the Editorial office (a small handling charge applies – see the *EPE PCB Service* page) or it can be downloaded *free* from the *EPE* Downloads page, accessible via the home page at www.epemag.co.uk. It is held in the PICs folder, under RC Switcher. This month's *Shoptalk* provides information about obtaining pre-programmed PICs. □

DrDAQ Data Logger




- Low cost - under £80 (+VAT)
- Built in sensors for light, temperature and sound (level and waveforms)
- Use DrDAQ to capture fast signals
- Outputs for control experiments
- Supplied with both PicoScope (oscilloscope) and PicoLog (data logging) software

For more information on DrDAQ, please visit:

www.picotech.com/drdaq120

PC Oscilloscopes

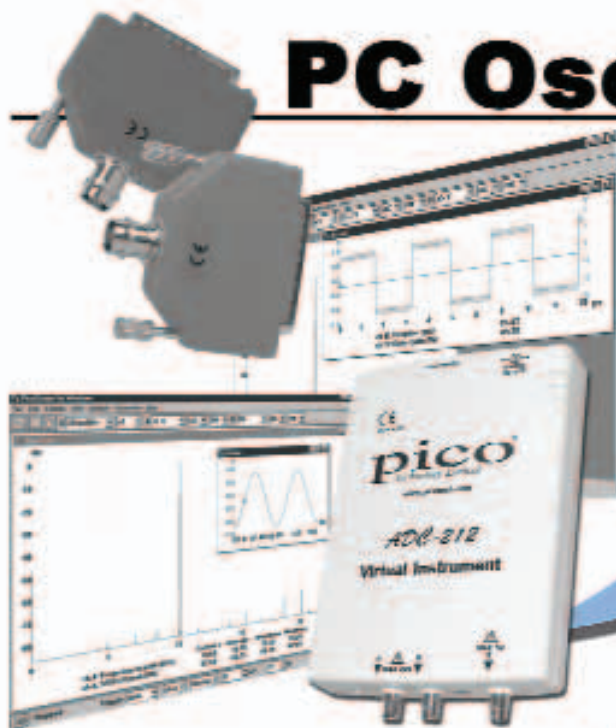

- Scope and spectrum analyser functions
- A fraction of the cost of benchtop scope
- Save multiple setups, for ease of use
- Save, print and e-mail your traces
- FREE technical support for life
- FREE software and upgrades
- Automated measurements

For more information on our scopes, please visit:

www.picotech.com/scope266

Tel: 01480 396395 Fax: 01480 396296 E-mail: sales@picotech.com

Pico
Technology Limited

CLEVER DIY CD AND DVD LABELLING

Barry Fox suggests that you can forget about felt tips to label those CDs and DVDs

BURNING CDs and DVDs is now extremely easy, as the music and movie industries are quick to complain. Labelling the burned discs has become the tricky part. But that too is about to change. The new LightScribe system from Verbatim, Mitsubishi Chemical and Hewlett Packard lets the recording laser in a disc drive print a label direct onto the disc surface.

Most people label their burned discs by marking the surface with a felt tip pen. The result is only as neat as their handwriting. Circular paper labels can be printed with an ink jet or laser printer and then stuck to the disc, but the label can come unstuck and jam in a player. An ink-jet can print direct to the label area of the disc but a completely new printer is needed, with a disc tray instead of paper feed.

LightScribe uses a modified disc drive which prints onto the label side of a new LightScribe blank CD or DVD. This has been factory-coated with a light sensitive dye that darkens when exposed to the drive's laser.

Music or video is first burned to the data recording side of the blank disc in the usual way. Text or pictures are then entered into LightScribe graphics software on the PC. The recorded blank is taken out of the disc drive and flipped over so that the label side is facing the recording laser. The drive rotates the disc and moves the laser while it fires bursts of intense light at the label area. The result is a silkscreen quality image of text and pictures integrated with the disc surface.

A barcode on the label side of the blank disc helps the laser precisely align with the printing area so that extra text can be added to a previously printed label if more recorded music tracks are added to the disc.

Existing drives cannot be modified to write onto LightScribe blanks, but new LightScribe drives for retrofitting to PCs will go on sale over the next month or so. LightScribe blanks will cost more than ordinary blanks, but Verbatim says the extra cost will be less than the price of a sticky label and ink to print it.

The system cannot yet manage colour but this is under development. So too is faster writing; it currently takes several minutes to write a label. But the PC gets on with the labelling while doing other jobs.

Electronic Lens

Room lighting that smoothly focuses to a spot, or spreads wide into a floodlight beam, at the turn of a knob. Car headlights that narrow the beam when a dashboard button is pressed. A vanity mirror that enlarges the image at the flick of a switch. Or a resonant cavity for a laser that can be fine tuned for maximum power output. All this can now be done without any mechanical moving parts reveals Philips of the Netherlands in a series of recently filed patents (WO 2004/102251).

The new system relies on a recently investigated phenomenon known as electro-wetting, whereby the surface tension of a conductive liquid is changed by applying an electric field.

A transparent cylinder has an ordinary flat mirror at one end, and is filled with silicone oil, and salt water with ethylene glycol. These two liquids do not mix, so form a meniscus boundary between them. Indium tin oxide electrodes bonded to walls of the container feed d.c. through the salt water to change the curve of the meniscus. Because the two liquids have different refractive indices, the curved meniscus behaves as a

lens which magnifies or reduces any image reflected by the mirror – like putting a concave lens or magnifying glass in front of an ordinary mirror.

Changing the current strength alters the curve to create a mirror with smoothly adjustable focal length. Because only the fluid meniscus is changing shape, there is no mechanical fatigue. The device is affordable because the flat reflective surface is cheap to make, says Philips.

Layering several different immiscible fluids in the container creates several menisci and a multi-element lens for higher optical power and more accurate focus, like a multi-element camera lens. If the two fluids are carefully chosen so that they have equal density, the mirror can be used in any position.

Barry Fox

Acoustic Helmet

THE Science Museum (London) website recently displayed an interesting safety product – a firefighter's helmet adapted into a life-saving communications tool. A new device using UK developed technology is being coupled to any material with acoustic transmission properties, such as protective headgear, in order to turn that material into a sound generator.

When installed in a fire helmet, the sound is generated within the entire helmet, and is directly processed by the brain's audio system. This leaves the ears free to assimilate any surrounding information at the scene, thereby providing a totally hands and ears free environment for the officers to perform their duties.

Brian Smith MD of Hull-based FeONIC plc, who developed the helmet,

told the Science Museum: "We are all aware of the pressure and danger emergency service workers face. It's vital that emergency messages get through in an environment where every second counts. But in noisy surroundings, say under the downdraft of a helicopter, firefighters and emergency service workers completely lose communications from the speakers from traditional radios.

In the same display there was also a prototype pair of swimming goggles that use the same technology, allowing swimmers to listen to music or hear a coach's instructions while under water, this time using bone conduction.

For more information about FeONIC technology visit www.feonic.com. The Science Museum's site is a www.sciencemuseum.org.uk.

THAT TAKES THE BISCUIT!

Seen recently on the BBC News website was the astonishing story relating how staff at the Mcvitie's laboratory in High Wycombe, Bucks, have designed a Crumb Test Dummy to test which baking techniques produce the most crumbs. The motorised mannikin has plastic teeth and is designed to replicate human eating.

The BBC's story reported that a Mcvitie's spokeswoman said that crumbs produced by a biscuit show if it has been cooked to perfection. But does that cookie crumble correctly for the "dunkers", we wonder?

The BBC's website is at <http://news.bbc.co.uk>. We found the Mcvitie's site via Google, but sadly no reference to their crumbly robot could be found!

Digital Model Railways


Regular readers will recall that in the August 2003 issue we published an article by John Waller on *Digital Command Control for Model Trains* (DCC). It was thus with interest that we have learned of a UK club who are much involved in such things.

The Model Electronic Railway Group (MERG) appears to be a lively club, with around 600 members. They say they cater for all model railways for all guages, and that they are the "leading International forum for all railway modellers interested in the application of electronics to the hobby".

The club issue a periodic newsletter, of which we have been sent several copies. The Spring 2005 issue, for example, has

32 A5 pages of information about model railways in general, and the electronics associated with them. DCC is obviously a topic with which they are well-familiar. Accompanying the newsletter were several other pages of useful information, including details of the various kits they sell to interested hobbyists.

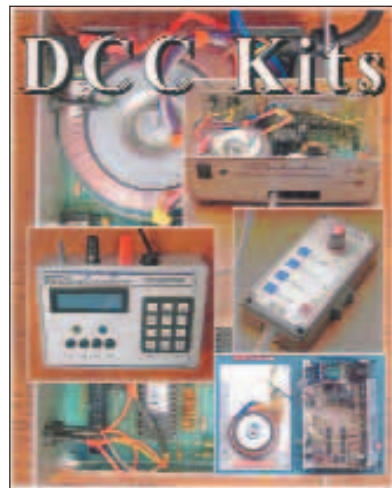MERG's Secretary is John Ferguson, 5 Butts Lane, Danbury, Essex CM3 4NP, who would be delighted to hear from anyone interested in the club. More information can be found via www.merg.org.uk. The club's officers seem to be well scattered in the south of England, but we feel sure that anyone from anywhere would be welcomed.



BIONIC EYES

Browsing the BBC website again, revealed the interesting news that US scientists have designed a bionic eye to allow blind people to see again.

The BBC's report says that the bionic eye comprises a computer chip that sits in the back of the individual's eye, linked up to a mini video camera built into the glasses they wear. Images captured by the camera are beamed to the chip, which translates them into impulses that the brain can interpret. Human trials are said to be started within a year.

Doing a web search via www.google.com revealed many sites relating to this story, and they are worth browsing.

It would appear that the technique has so far been proved on rats, but not yet on humans, and that human bionic eyes may yet be five years away. It is not being suggested that the eye will restore sight to the totally blind, but will be used for those who have suffered partial retinal loss. In these cases, the implant would bypass damaged cells and stimulate the remaining viable ones.

It is expected that the technique would provide enough optical stimulation to allow patients to recognise faces.

The BBC's web site is at www.bbc.co.uk. The Science/Nature/Technology links from the main page often have stories well-worth browsing.

Lead-Free

We have been advised that the latest report on the "Current Status of European Lead-Free Solder" is available for free download from:

www.europeanleadfree.net/POOLED/articles/bf_docart/view.asp?. General information on the subject can also be found at www.europeanleadfree.net.

You will recall from previous *EPE* items, that the use of lead for soldering is to be banned under new legislation which comes into force next year.

First All-Digital TV Viewers

With Barry Fox's alarming report elsewhere in this issue about the UK's readiness for the switch-over to digital TV in mind, it's interesting to note that the first TV viewers have already lost their analogue transmissions.

On 30 March 2005, 400 households in Ferryside and Llansteffan in Carmarthenshire changed to digital only. They had voted to take part in a pilot scheme preparatory for the UK's final switchover, due to occur by 2012.

ROUND THE HORN

"Virtual surround sound" systems take a headphone sound signal and slightly boost and delay some frequencies to try and mimic what the ears hear from all around the head in real life. The effect should be surround sound from stereo but it differs for different people because humans do not all have the same size heads and same-shaped ears.

With funding from the Engineering and Physical Sciences Research Council (EPSRC), the University of York's Department of Electronics has been working with the University of Sydney, Australia, on a practical solution.

Booths, like passport photo cabins, will take 3D images of a customer's head to measure the shape and size of their ears. These measurements are then used to compute the design for a personalized electronic filter (or Head-Related Transfer Function) that alters a stereo signal to create the ideal surround effect for the individual's ears.

The booth loads the filter design into a smart card which the individual takes away and plugs into a new generation of portable stereo music players, video screens or game consoles. The same system can help people with hearing aids exploit the "cocktail party effect" – ignore a boring face-to-face conversation while listening instead to something much more interesting from over the shoulder.

Barry Fox

Progressive HDTV

If you are confused by HDTV, take heart. Even the manufacturers are confused too.

When Panasonic "proudly introduced" the HD quality of the DVD-S97 PAL DVD player, the press release also said that "Panasonic has now developed the technology further, allowing PAL progressive scan to be enjoyed on a standard television."

When asked for some extra information on how Panasonic had cracked the apparently impossible challenge of getting the scan coils of an ordinary cathode ray tube screen to cope with the much higher line frequencies needed for progressive scan, the Panasonic spokesperson soon backed down. "To enjoy a progressive scan picture, a TV with progressive capabilities must be used."

We can only wonder how many glossy magazines are now reporting that the S97 magically turns an ordinary TV into a Progressive Scan TV.

Barry Fox

FIRESTREAMER BACKUP

Most PC owners already own the hardware needed to back up data from their hard drive, to tape – although they don't know it. Cristalink of New Zealand is now selling a software package that lets an ordinary DV (digital video) camcorder work with the back-up program that comes free with Windows.

Firestreamer-DV stores up to 12GB of uncompressed data (equivalent to three recordable DVDs) on a Mini-DV cassette, by replacing each video picture frame with 100 Kbytes of data. The trick is to correct the data errors caused when, as often happens, a picture is lost. Lost pictures pass largely unnoticed on screen but cause massive data errors.

Firestreamer duplicates some of the data and spreads it across several different picture frames so that even if 32 pictures out of 1020 are completely lost, or 2cm of tape in every 64cm is damaged, the recovered data stays intact.

Firestreamer can be bought on line for \$46. The company's web site bravely tells how to test the system's ability to correct tape errors by deliberately erasing up to one second of tape – browse:

www.firestreamer.com/fs/reliability.as.

Barry Fox

Circuit Surgery

Alan Winstanley and Ian Bell

Our monthly “surgery” continues with Ian’s CompactFlash primer, outlining the basic protocols and the typical interconnections needed to interface them with a microcontroller circuit

On The Cards

This month we progress further into the world of CompactFlash (CF) cards, with a more detailed description of their electrical interface. Last month we were more concerned with the mechanical details of using the cards and we included some photos of a printed circuit board (p.c.b.) suitable for experimenting with CompactFlash cards.

This p.c.b. expands the fine-pitched connections of the card header to a 0.1-inch pitch, facilitating the connections of the CF card to stripboard or other prototyping system. Note that the board is intended just for *experimentation* and *prototyping*, as it is *not* suitable for an actual project using a CompactFlash card.


The p.c.b. master of the CF experimenter’s board is shown in Fig. 1, showing

the position of the card header on the board. This board is available from the *EPE PCB Service*, code 507.

The series of holes along the edge of the printed circuit board will align with the strips on 0.1-in stripboard, and bare wires can be passed through the aligned holes. As the copper foil is on upper surface of the experimenter’s board and the lower surface of the stripboard, the interconnecting wires can easily be soldered at both ends to connect the CompactFlash signals to the reader’s stripboard.

It will be seen that the CF card header has 50 fine-pitch connections, which inevitably makes soldering

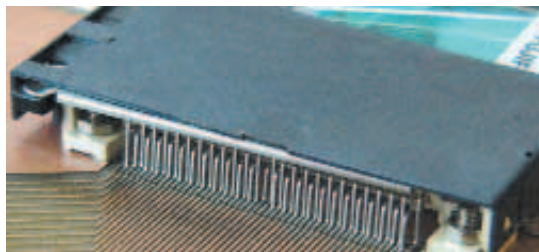a very delicate task. This will really test your skills! However, as we have shown, it can be done with care using an ultra fine tipped low-wattage soldering iron. (Consider building several units to practice the assembly technique.) A good tip to



Card header soldered to interface circuit board


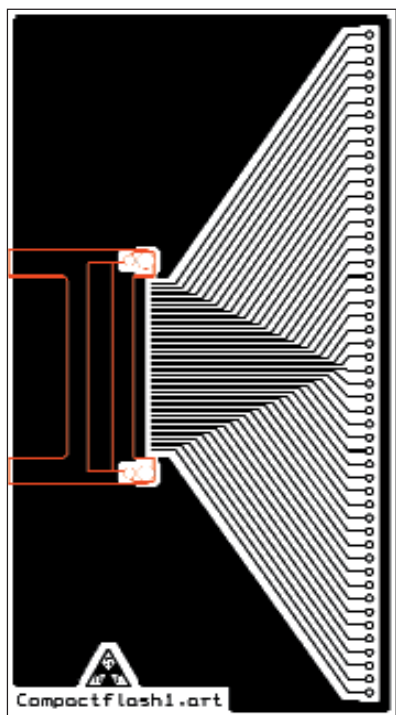


Fig.1. Printed circuit board master for the CF interface board

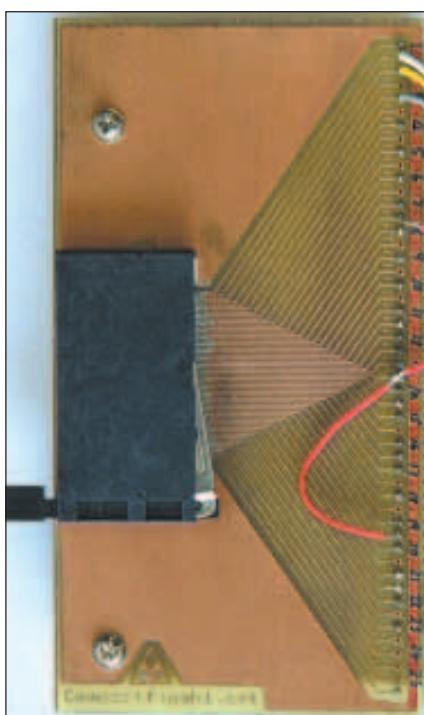

Prototype interface board for the CompactFlash card

help eliminate problems is to ensure that all p.c.b. pads are of the same height, which can be achieved with the careful use of an abrasive rubber block; then wipe the board with a p.c.b. solvent cleaner to remove debris.

The CF headers usually have screw fixings allowing it to be held in place prior to soldering. The two end connections should be soldered first to ensure that the board is correctly aligned. You may prefer to use very narrow gauge silver-loaded solder with a fine tip iron to make each soldered joint. Silver solder enables better quality joints to be made by hand.

Another approach is to try a “reflow” soldering method, in which each copper pad on the p.c.b. is pre-tinned with silver solder, then the pads are levelled very gently with an abrasive block. Apply a tiny amount of silver solder to the CF header connections, and fit the header to the board. Gently reheat the connections to make the solder flow and form the joint.

CF Card Primer

Having covered the mechanical aspects, let us now turn to the electrical principles of CF cards.

CompactFlash memory cards are not simple random access memories (RAM) that can be read byte by byte from any address in any sequence. In fact they

Table1: Pin Functions of CompactFlash Card in PC Memory Card Mode

<i>Pin</i>	<i>Name</i>	<i>Type</i>	<i>Description</i>
1	GND	Power	Ground
2	D03	I/O	Data Input/Output
3	D04	I/O	Data Input/Output
4	D05	I/O	Data Input/Output
5	D06	I/O	Data Input/Output
6	D07	I/O	Data Input/Output
7	CE1	Input	Card Select 1. Set this input low to enable access to the card. With $\overline{\text{CE2}}$ high and $\overline{\text{CE1}}$ low the value of A0 determines if odd or even bytes of the 16 bit word are transferred. This input is pulled up internally and has a Schmitt trigger type input characteristic
8	A10	Input	Address Input
9	OE	Input	Output Enable. This is strobed low in order to read data from the card. During data operations each successive strobe of OE reads the next location of the data buffer. This input is pulled up internally and has a Schmitt trigger type input characteristic
10	A09	Input	Address Input
11	A08	Input	Address Input
12	A07	Input	Address Input
13	V _{CC}	Power	Positive supply
14	A06	Input	Address Input
15	A05	Input	Address Input
16	A04	Input	Address Input
17	A03	Input	Address Input
18	A02	Input	Address Input
19	A01	Input	Address Input
20	A00	Input	Address Input
21	D00	I/O	Data Input/Output
22	D01	I/O	Data Input/Output
23	D02	I/O	Data Input/Output
24	WP	Output	Write protect, but not applicable to CompactFlash so this signal is held low by the card after initialization.
25	CD2	Output	Card Detect 2. Like Card Detect 1 (see pin 26).
26	CD1	Output	Card Detect 1. This pin is grounded internally in the card. If the pin is pulled up externally then insertion of the card is easily detected
27	D11	I/O	Data Input/Output. Only used if 16 bit data transfer is required.
28	D12	I/O	Data Input/Output. Only used if 16 bit data transfer is required.
29	D13	I/O	Data Input/Output. Only used if 16 bit data transfer is required.
30	D14	I/O	Data Input/Output. Only used if 16 bit data transfer is required.
31	D15	I/O	Data Input/Output. Only used if 16 bit data transfer is required.
32	CE2	Input	Card Select 2. Only used if 16 bit data transfer is required. For 8 bit data transfers this input can be held high.
33	VS1	Output	Voltage Sense 1. This is grounded by the card.
34	IORD	Input	I/O Read. This signal is not used in PC card memory mode and can be left unconnected. This input is pulled up internally and has a Schmitt trigger type input characteristic
35	IOWR	Input	I/O Write. This signal is not used in PC card memory mode and can be left unconnected. This input is pulled up internally and has a Schmitt trigger type input characteristic
36	WE	Input	Write Enable. This is strobed low in order to write data to the card. During data operations each successive strobe of $\overline{\text{WE}}$ writes the next location in the data buffer. This input is pulled up internally and has a Schmitt trigger type input characteristic
37	READY	Output	Ready/Busy (RDY/-BSY). The card takes this signal low when it is busy performing internal operations and is unavailable for external data transfer.
38	V _{CC}	Power	Positive supply
39	CSEL	Input	Master/Slave Select. This signal is not used in PC card memory mode and should be grounded externally to avoid floating the input.
40	VS2	Output	Voltage Sense 2. Reserved PCMCIA signal. This is an open circuit on the card.
41	RESET	Input	Reset. Active high reset for the card controller. Can be kept open or high all the time in which case will just perform a reset on power up and not remain permanently reset.
42	WAIT	Output	Wait. This is asserted low by the card to tell the external system to delay completion of the current memory read or write cycle.
43	INPACK	Output	Input Acknowledge or DMA Request. This signal is not used in PC card memory mode and can be left unconnected.
44	REG	Input	Attribute Memory Select. If this input is high memory read or write cycles access the card's common memory. If this input is low the attribute or register memory is accessed. If the attribute memory is not used this pin can be held high. This input is pulled up internally and has a Schmitt trigger type input characteristic
45	BVD2	Output	Asserted High. Not used in PC card memory mode.
46	BVD1	Output	Asserted High. Not used in PC card memory mode
47	D08	I/O	Data Input/Output. Only used if 16 bit data transfer is required.
48	D09	I/O	Data Input/Output. Only used if 16 bit data transfer is required.
49	D10	I/O	Data Input/Output. Only used if 16 bit data transfer is required.
50	GND	Power	Ground

Note: Details shown refer only to PC Memory Card Mode; names and functions of some pins differ in other modes

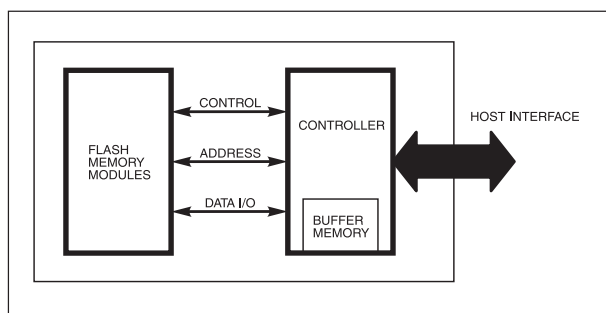


Fig.2. Internal structure of a CompactFlash card

behave like disk drives, and can operate in **True-IDE mode**, allowing them to be connected to the IDE (Integrated Drive Electronics) bus of a PC like any other IDE disk drive, without any additional circuitry.

However, CompactFlash cards have more than one mode of operation, and can also be used in **PC-card I/O mode** and **PC-card Memory mode**. The most convenient mode for using a CF card in conjunction with microcontrollers (e.g. PICmicros) is usually PC-memory mode, because this needs fewer data lines (and hence microcontroller I/O) lines. True-IDE mode requires 16 data lines, whereas PC-card Memory mode can use either 8 or 16 data lines.

In Fig. 2 we show the structure of the internal circuitry of a CompactFlash Card. The data is stored in one or more Flash memory modules, but these are not directly accessible from the card's pins. Instead a controller manages the flow of data between the memory modules and the external world.

Data flowing in and out of the card goes via a buffer memory, as directed by the controller. The actions of the controller are determined by some of the pins on the CompactFlash Card and by commands that can be written to the card via its data bus.

Data is written to and read from the card in chunks equal in size to the buffer memory, which is usually 512 Bytes. This corresponds to one *sector* if the card is regarded as a disk drive. In addition to transferring stored data, the buffer can also be filled with data about the card itself (manufacturer, memory size, serial number etc) by issuing the controller with a "card identify" command. Reading the buffer provides a lot of information about the card.

In Table 1 we show the designated functions of the 50 pins of the CompactFlash Card operating in PC-Memory Card Mode. This information is taken from the "CF+ and CompactFlash Specification Revision 2.1" document, which is published on the web by the CompactFlash Association (www.compactflash.org). This 133-page document provides a complete specification for the CompactFlash card, but as often the case with such heavyweight documents, this takes quite a bit of effort to read!

Note that the details shown in Table 1, refer **only** to the PC-Memory Card Mode; the names and functions of some of the pins differ in other modes and not all pins are used in PC-Memory Card Mode. The table indicates if these unused pins should be left open or connected to a specific logic level. The data lines have high impedance inputs and tristateable totem-pole outputs. The positive power supply can be either +3.3V or +5V and, of course, the logic signals should correspond with the supply voltage.

Take Your PIC

An outline schematic showing how a CompactFlash card could be interfaced to a microcontroller such as a PIC using the CF in its PC-card Memory Mode is shown in Fig.3. This configuration is probably one of the simplest possible and requires 17 configured I/O ports on the microcontroller as shown. We have used this approach successfully

Table 2: Address Decoding

A2	A1	A0	Offset	$\overline{OE} = 0$	$\overline{WE} = 0$
0	0	0	0	(Even) RD Data	(Even) WR Data
0	0	1	1	Error	Features
0	1	0	2	Sector Count	Sector Count
0	1	1	3	Sector No.	Sector No.
1	0	0	4	Cylinder Low	Cylinder Low
1	0	1	5	Cylinder High	Cylinder High
1	1	0	6	Select Card/Head	Select Card/Head
1	1	1	7	Status	Command

The microcontroller monitors the card's READY output. The card takes this signal low when it is busy performing internal operations and is unavailable for external data transfer. The microcontroller should wait for this signal to go high before accessing the card. This signal is also pulled up by a 10kΩ external resistor R1.

The card's RESET input is connected to

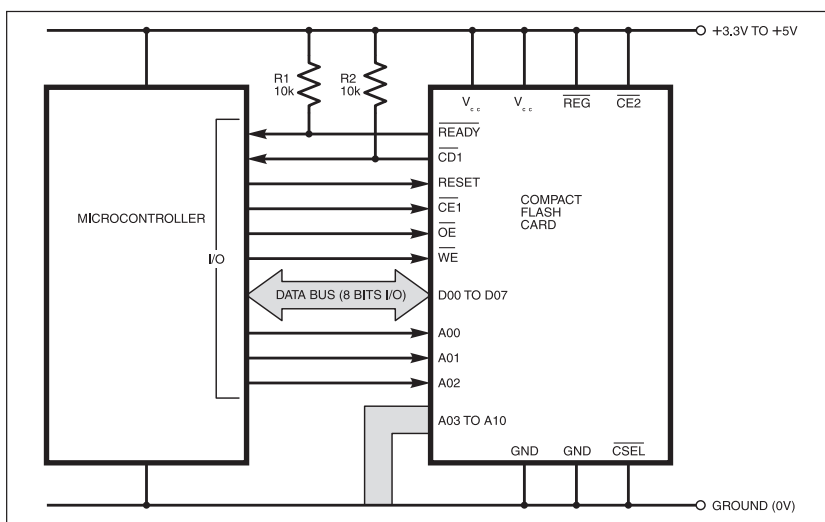


Fig.3. Suggested circuit configuration for connection of a CompactFlash card to a microcontroller, such as a PIC

with a PIC 18F452, but other microcontrollers would be just as suitable.

The card's CE1 input is taken low by the microcontroller during all read and write operations. In the configuration used here, only three of the card's address lines are required; these are connected to microcontroller outputs. The card's OE (Output Enable) input is connected to the microcontroller's output and is strobed low in order to read data from the card. The card's WE (Write Enable) input is connected to the microcontroller's output and is strobed low in order to write data to the card. The card's CE2 input is held high as we are only using 8-bit data transfers.

Table 2 shows the operations performed based on the values of WE, OE, and A0 to A2. Note that with CE2 high and CE1 low, when offset 0 is accessed twice then the first byte accessed is the even byte and the second byte accessed is the odd byte of the current word. The card detect CD1 output from the card is connected to a microcontroller pin configured as an input and is pulled up by a 10 kilohm external resistor R2. If this input is low then the microcontroller knows that a card is present.

a microcontroller output, enabling the microcontroller to initialize the card by taking this signal high.

The WAIT output is not connected in this circuit. This means that the microcontroller has to make sure that read and write cycles (using WE and OE) are long enough to conform to the CF card's slowest memory timing requirements. This approach does not deliver the fastest possible operation but it makes programming the microcontroller simpler.

The card's CSEL input is high so that memory read or write cycles access the card's common memory. The attribute or register memory cannot be accessed directly in this configuration, but information about the card is available by issuing the card identify command.

So far we have described the electrical connections needed between a CompactFlash card and a microcontroller such as a PIC. This is not the complete story however, as we also need to know about the commands and data to send to the card in order to use it. This is the job of the software running on the microcontroller, and will be the subject of next month's discussion on the CompactFlash card. *I.M.B.*

Ingenuity Unlimited

WIN A PICO PC BASED OSCILLOSCOPE WORTH £586

● 5GS/s Dual Channel Storage Oscilloscope

● 50MHz Spectrum Analyser

● Multimeter

● Frequency Meter

● USB Interface.

If you have a novel circuit idea which would be of use to other readers then a

Pico Technology PC-based oscilloscope could be yours.

Every 12 months, Pico Technology will be awarding a PicoScope 3205 digital storage oscilloscope for the best IU submission. In addition a DrDAQ Data Logger/Scope worth £59 will be presented to the runner up.

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're

looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work* and **must not have been published or submitted for publication elsewhere**. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. **Please draw all circuit schematics as clearly as possible**. Send your circuit ideas to: *Ingenuity Unlimited*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. (We **do not** accept submissions for IU via email). Your ideas could earn you some cash **and a prize!**



GPS/Audio Selector *Route March?*

MY brother is a keen motor cyclist and recently purchased a Garmin GPS Street Pilot 2610 to assist him on his annual European biking holidays. The Pilot monitors a pre-programmed route and periodically issues audio navigational instructions as appropriate. These are routed to the earphones in his helmet.

What he also wanted, though, was to listen to his radio/MP3 player, but to use an automatic switching device which would switch in the Pilot's audio signal when it became active, and also mute the MP3 audio. This design fulfils that need.

Referring to Fig.1, the audio output from the Pilot is fed to non-inverting input pin 3 of op.amp IC1 via a.c. coupling capacitor C1. The circuit around IC1, comprising diodes D1, D2 and resistor R2, forms a precision rectifier. The diodes are both germanium types because they have lower forward conduction threshold voltages and better linearity than silicon types.

The d.c. output from the rectifier is then loaded by R3 and smoothed by C2, thus presenting a d.c. voltage level of approximately 0.3V to pin 3 of IC2 when audio output from the GPS unit is detected. The GPS unit issues a "beep" just before commencing to send an audio navigational message and this is ideal for triggering the sensing/switching circuit.

Op.amp IC2 is set up as a non-inverting d.c. amplifier with a gain of around 30, such that when an audio signal is detected then IC2's output immediately

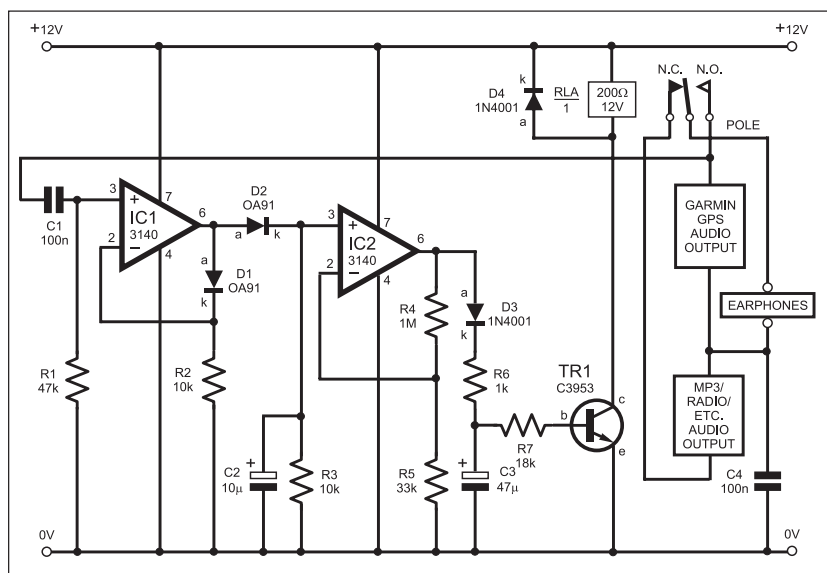


Fig.1. Circuit diagram for a GPS/Audio Selector

swings from zero to about 9V or 10V and charges C3 via D3 and R6. Transistor TR1 is then switched hard on via R7 and energises relay RLA. The relay now selects the GPS audio message and mutes the normal audio signal feeding the earphones.

Because the output from IC2 drops to zero "between words" in the GPS message, it is necessary to keep TR1 switched on for

a few seconds – this is the purpose of D3/C3 and R6/R7. Diode D4 provides protection from reverse voltage generated by the relay coil and C4 enables a.c. coupling to the 0V line for both audio sources.

Although a C3953 transistor was used for TR1, almost any small signal *nnp* transistor may be used.

*George Caldwell,
Londonderry, N.Ireland*

Virtual Bomb *Tickety Boom!*

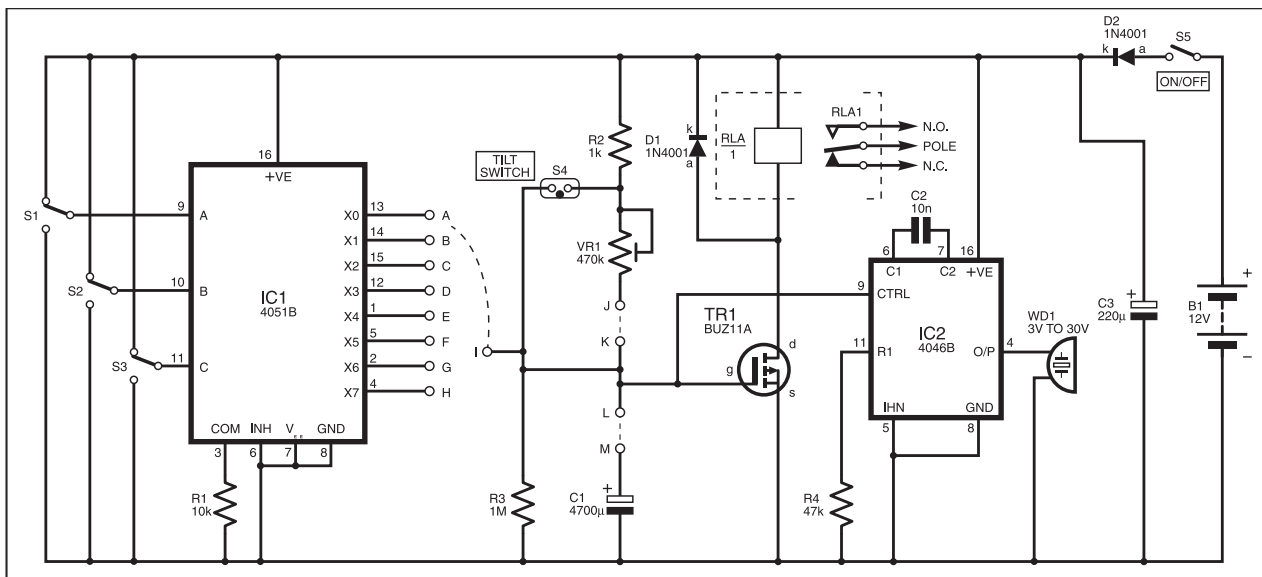


Fig.2. Circuit diagram for a war gamers' Virtual Bomb

RECENTLY a group of war gamers approached the author. They play a game in which one team defends a “bomb”, while the other seeks to locate and defuse it. The disappointing part was that the bomb was just an empty pop bottle. Could the author design a more realistic “bomb” that would present them with a challenge? (By way of reassurance, the circuit described here is far from any that might be put to serious use.)

The war gamers had a number of requirements. As in the movies, the bomb should have a timer counting down the seconds. It should have a number of wires, one of which should be the “hot” wire. If the hot wire were cut, the bomb should be defused. If any other wire were cut, the bomb should instantly “detonate”.

Further, the bomb should have a bank of toggle switches, so that it could be defused by entering the correct combination. If possible, the circuit should be able to trigger e.g. a siren or a standard smoke canister. Not least, it should be possible to reconfigure both the hot wire and the switch combination with relative ease, so that an opposing team would not have the opportunity to learn the routine.

Circuit Details

All of this is provided for in the circuit presented in Fig.2, using just over a dozen components to incorporate every suggestion in some way.

Switches S1 to S3 represent the bank of toggle switches described above. These present IC1 inputs A to C with a three-bit binary code. That is, there are eight possible combinations. By adding dummy switches, the number of combinations could be greatly increased – or, with some rudimentary knowledge of electronics, these switches could be replaced with a keypad.

The combination is altered by changing a single connection between IC1's outputs (the bank of terminals marked A to H), and terminal I. Terminals A to H and I would be nine long solder pins, connected from any one of A to H, to I, by means of a single crocodile

clip. When the correct combination is found, capacitor C1 is discharged through IC1 via resistor R1, and the bomb is defused. (Note that if switches S1 to S3 select the correct combination before the game begins, the bomb will be defused from the start)!

As soon as the circuit is switched on, by means of S5, C1 begins to charge via R2 and preset VR1. The latter sets the charge time between about five seconds and 20 minutes. When C1 is suitably charged, TR1 conducts, and energises relay RLA. If the constructor should wish for RLA to latch, a double-pole double-throw (d.p.d.t.) relay may be used, with the spare set of contacts shorting TR1's drain and source. In this case, the relay is reset by switching off S5. The relay, in turn, may be used to switch the suggested siren.

Terminals J and K, and L and M, are again long solder pins, which are connected by means of crocodile clips – as many as desired – connected either in series or parallel as the need may be. If the connection between terminals J and K is broken, C1 gradually discharges, and the bomb is defused.

If the connection between terminals L and M is broken, the potential at TR1's gate (g) instantly rises to the potential at the junction of VR1 and R3, and the bomb is "detonated". Switch S4 is added as a jiggle switch (or tilt switch), with R2 protecting the switch from surge current as C1 is charged. Thus a brief jiggle is unlikely to trigger the bomb, but too much jiggling soon will.

Lastly, timer IC2 is a voltage controlled

oscillator (v.c.o.), which is controlled by the voltage at the gate of TR1. The v.c.o. selected for this task is surely the simplest and most versatile available. Strictly, it is a phase-locked loop, of which only the oscillator section is put to use.

At first, timer IC2 is completely silent – but as the voltage at TR1's gate rises, so piezo sounder WD1 begins with a slow tick-tick-tick, which eventually reaches a very high pitch – then the bomb “detonates”. The pitch's upper limit is determined by the value of resistor R4. When the bomb is defused, this pitch drops like a falling siren. It drops more slowly when the “hot” wire is cut, since the discharge path is then through R3, not R1.

The circuit could be simplified, by omitting IC2, or by omitting jiggle switch S4. In fact, even IC1 could be omitted, leaving only a bunch of wires with the hot wire to defuse the bomb. The relay could be directly replaced with e.g. a 12V siren (TR1 is capable of carrying 6A with a suitable heatsink). The choice is the constructor's.

The circuit draws less than 1mA current while timing, so that by itself it would run off a set of eight AA batteries for weeks at a time. The heaviest current is drawn, of course, when relay RLA1 closes. If this were closed continually, depending on the type of relay used, the batteries might only last an hour.

The author thanks Jonathan Rempel and his team of war gamers for the idea.

*Thomas Scarborough,
Cape Town, South Africa*

INGENUITY UNLIMITED
BE INTERACTIVE

IU is your forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly win a prize.





Electronics from Down Japan

Get Your **FREE UK Pounds Sterling Priced Catalogue** - all 400+ pages!
Just fill out the catalogue request form at www.jaycarelectronics.co.uk/catalogue

Check our website!

- All of our 6,000+ products with search facilities.
- 128-bit secure on-line ordering - safe & secure.
- Over 3,500 product datasheets & application notes.
- And we're from Australia, so you can trust us!
- Postage and Packing includes airmail to the UK.



www.jaycarelectronics.co.uk

Post and Packing Charges:		
Order Value	Cost	
£20 - £49.99	£5	
£50 - £99.99	£10	
£100 - £199.99	£20	
£200 - £499.99	£30	
£500+	£40	
Max weight 12lb (5kg) - heavier parcels POA. Minimum order £20.		

FREE
400+ page
Catalogue

JUST ONE OF OUR MANY GREAT PRE-BUILT & TESTED CONSUMER PRODUCTS!

Store Your Video Memories Forever

XC-4809 £41.75 + post and packing
Transfer all of your Betamax, VHS, and camcorder tapes to DVD using your computer's DVD writer. It includes powerful editing software to add colour and transitional effects, as well as sound tracks if desired. The box measures just 1 3/8(W) x 3 3/4(H) x 9 1/16(D)" and supports S-Video and composite inputs from NTSC or PAL sources.




Radio Frequency Identity (RFID) Triggered Relay Kit

KC-5393 £26.25 + post and packing

RFID systems can operate much like a conventional lock and key but wireless. The RFID 'tag' transmits a unique code when energised by the receiver's magnetic field. As long as the tag has been pre-programmed into the receiver, access is granted. This project provides a normally open and a normally closed electrically switched output triggered by a tag. Kit includes circuit board, one Keyfob style RFID tag, electronic components, and clear English instructions.

Extra RFID Tags

Keyfob style:	Measures 1 3/16(W) x 1 9/16(L) x 3/16(H)"	ZZ-8950 £3.00
Card style:	Measures 3 5/16(W) x 2 5/32(H) x 1/16(T)"	ZZ-8952 £1.75
Clear insert style:	Measures 13/16(Dia) x 1/16(T)"	ZZ-8954 £1.50

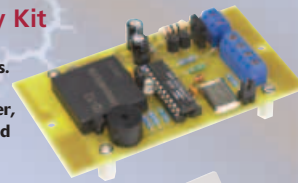

Dual 12V Battery Controller Kit

KA-1782 £14.50 + post and packing

This project connects an auxiliary battery in an SUV to the charging system when your engine is running, then disconnects it when switched off. This prevents your main vehicle battery from going flat. You can safely leave inverters, fridges etc. running overnight with no problems in the morning. It can handle around 100 amps of current at 12VDC. Kit includes circuit board, a weatherproof diecast aluminum case, heavy duty battery binding posts, electronic components, and clear English instructions.



Get the Video Quality You Paid For With Our Doctor Video Kit

KC-5390 £29.00 + post and packing

Copy protection is put in place on videos and DVDs for a good reason, but this robs you of the true high quality reproduction that it is capable of. Get the quality you paid for and strip out these annoying signals! It supports composite and S-video signals and can be configured for NTSC or PAL format. Kit includes case, circuit board, all electronic components, and clear English instructions. Note: Some SMD soldering required.

Caution: During signal conditioning, this unit removes copyright protection. Piracy is a crime, & Jaycar Electronics takes no responsibility for its potential for unlawful use.



We Stock...

Electronic Components

Electronic Project Kits

Test & Measurement
Equipment

Power Products
and Accessories

Audio & Video
Equipment & Accessories

Computer & Telecoms
Accessories

Security & Surveillance
Equipment

Universal High Energy Ignition Kit

KC-5247 £15.40 + post and packing

Get better fuel efficiency and performance from your car! It produces a very intense 0.9ms spark which results in more complete fuel burning, lower emissions, and increased performance. It works with points, twin points, and reluctor ignition systems. Kit supplied with weatherproof diecast aluminum case, circuit board, and all electronic components.

- Works great on points ignition (ie. older cars). Can be used on newer cars with Hall-effect sensor.



Explanation of icons used for kits

Indicates an approximate construction time for each project for a competent constructor. It does not however, include any installation etc that may be required.



Straightforward to assemble, generally built in one session. Requires basic electronics and soldering skills.

Requires a good knowledge of electronics to understand its operation, and troubleshooting techniques may be required.

3 Stage FM Transmitter Kit

KJ-8750 £5.80 + post and packing

The circuit board may measure just 2"(L) x 11/16(W)", but it can transmit signals over half a mile in the open. It has flexible power requirements, with 6 to 12VDC input voltage (so a 9V battery would be suitable). It is quick to build, and fun to use. Kit supplied with circuit board, electronic components, and clear English instructions.



Log on to

www.jaycarelectronics.co.uk/catalogue
for your **FREE** catalogue!

0800 032 7241

(Monday - Friday 09.00 to 17.30 GMT + 10 hours only) For those that want to write:
100 Silverwater Rd Silverwater NSW 2128 Sydney Australia

Jaycar
Electronics

READOUT

Email: john.becker@wimborne.co.uk

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly.

WIN AN ATLAS LCR ANALYSER WORTH £69

An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd., will be awarded to the author of the *Letter Of The Month* each month.

The Atlas LCR automatically measures inductance from $1\mu\text{H}$ to 10H , capacitance from 1pF to $10,000\mu\text{F}$ and resistance from 1Ω to $2\text{M}\Omega$ with a basic accuracy of 1%.



★ LETTER OF THE MONTH ★

Electronics Experiences

Dear EPE,

A while ago I was visiting a university electronics department with which I was loosely connected and was talking to a senior technician about life, the universe etc., when a student came in. He said he was looking for advice because he was building an audio amplifier which would blow all those of his mates "out of the water".

He said that he had a few questions about the circuit which he found a little ambiguous. We both looked at his piece of paper carefully. Even I who am to mains powered circuits what Attila the Hun was to underwater basket weaving was alarmed. There were lots of worryingly meaty components in the circuit and no distinction was made between wires crossing not connected and wires crossing and connected. We asked where he had got this peerless piece of design from. The answer was the Internet. This raised two issues.

Firstly, students nowadays, it seems, know a lot about TTL and CMOS but don't learn much about everyday mains electrical matters. Apparently, the overriding concern for the safety of students (and them not suing their university or tutors) means that they can leave after three years with little if any experience of mains powered circuits.

They do however believe they are competent to tackle more or less any

electric circuit construction task – which may possibly be true if and only if the basic design is sound. When I was young poking about in the back of a valve radio, or valve-based guitar amplifier with a wooden handled screwdriver, soon gave you an appreciation of the potential for nastiness from mains electricity powered devices (if you survived). This lack of appreciation of the dangers led this student into an experiment which could have proved expensive and even possibly fatal.

We are all well aware of the flaky information on the Internet but with computer-based circuit drafting programs even doubtful designs can appear spuriously credible. I have taken digital designs off the internet, knowing that if the worst happened I would lose a few pounds worth of i.c.s. It might be a good idea to remind readers of *EPE* that there is no quality control on the Internet and designs which use mains electric power could kill.

John Cookson, via email

You are so right John, and we are acutely conscious of our role in helping readers avoid early departure to infinity! It's interesting, though, to reflect back on how attitudes to safety have changed over the years since I started learning how to blow fuses, and discovering the painful way not to take

chances over mains electricity remaining tame, or even whether or not h.t. capacitors would self-discharge adequately before I brushed my hand against them.

Looking back, I'm horrified at what the various electronics mags of the time would publish mains-wise. In those days of valves, it was common-place for us to be encouraged to use mains power, albeit via a transformer, to supply those constructions. And I've sure had a "belt or two"! But I don't recall it being drummed into us by the mags that mains electricity can be lethal.

These days we feel it utterly incumbent on us to issue such warnings when appropriate. And it's not only that we want to avoid litigation, but we genuinely want to keep our readers, and for them to enjoy electronics safely. In this respect, of course, we are much helped by most circuits now being powered at low d.c. voltages which present no hazards, unlike years ago when most valves could only be run at higher voltages.

But it is very true that circuits posted on the Net are not subject to such controls as we impose on what we publish. And we echo what you say, John. Readers, take care over those circuit offerings you may find on unknown sites, and if in doubt about them or your capability of discerning good from bad, seek the opinion of someone who is qualified to advise.

Cold Soldering

Dear EPE,

Chris Swinnerton (*Readout* April '05) in his list of "crimes" for which he might in future be prosecuted, did not mention soldering! I refer to the fact that our illustrious uncommon market have decided that the use of lead for soldering is far too dangerous for us to contemplate in the future and we must use other and obviously more expensive alternatives.

Funny thing is, on one TV selling programme they had a thing that apparently did cold soldering and the only thing I can think it does is to use a high speed vibrator that pulverises the lead into taking up another shape, but how conductive that would be I hate to think.

Anyway, the demonstration showed them pouring the lead round a piece of multistrand wire which was going to be

inserted into a terminal. Now this is the worst thing you can do in real life because inevitably the lead migrates, the screw comes loose and you've got an arcing contact. That's why several enlightened manufacturers crimp a brass sleeve over the cable strands and you screw down onto that.

Coming back to speed cameras – if the authorities don't want you to travel at speed then cars should not be able to travel that fast. I believe that coaches have speed governors on them. Would it not be possible to send a radio signal to a car receiver to operate a 31mph speed trip when you're in a 30mph zone?

George Chatley, via email

Whilst I've not come across the soldering product you describe, George, it reminds me of a product I once tried for repairing damaged p.c.b. tracks. It was a

type of metallic paint which was applied using an ordinary artist's paint brush. It was painted across the track break and allowed to dry. I didn't get on with it, so reverted to the time-honoured method of soldering a link wire across any break.

As an aside – I'm reminded of someone who visited my premises in those long-gone days, trying to persuade me that his hand-drawn p.c.b. artwork was superior to the crepe tape and pads technique in widespread use at that time. The examples he showed me were beautifully drawn in ink but utterly impractical in the commercial world.

When asked about making changes to tracking, he replied that sections could be readily redrawn. Not too long after that, PCB CAD packages at reasonable prices became available, and I acquired one. I wonder if he ever did find a commercial outlet for his technique?

Image Scaling and P.C.B. Pads

Dear EPE,

The physical construction photographs in *EPE* are usually reduced in size compared to real life. It might be necessary to fix a circuit board into a box, leaving space for other items such as batteries. Well, here's a quick way to measure the diagram so as to know the "real world" dimensions to apply to the finished item, so as to achieve the correct spacing.

Having obtained the circuit board (or some other easily-identifiable component of definite dimensions), measure the real item and also the size of its image in the photograph. From that, the scale factor is calculated as a simple ratio. I've produced an actual-size try-square layout, 15cm x 30cm and scaled at every 2mm, on my computer's CAD package. It can be printed out whenever required, first setting the scale that the package will apply to the final hard copy.

If anyone would like a paper copy, please send me a C4-sized board-backed envelope, pre-addressed for reply and with return postage, plus one extra stamp (2nd class non-face-value will do) to cover the printing cost. State the scale factor that you need!

Also, I am designing a project which I intend to offer to *EPE* for publication. My PCB CAD package needs precise specifications for both track width and minimum clearance. What's the *EPE* standard? I would prefer to be told in measurement units of thousandths of an inch, if convenient. Also, I can't emulate those nice wide pads for the d.i.l. i.c.s, would round ones do? If so, what diameter? And, what diameter for the discrete component pads?

**Godfrey Manning G4GLM,
Edgware, Middx, via email**

Thank you for the offer Godfrey.

Regarding p.c.b.s, there are no specified track widths etc that we require, but the CAD package I work with (an ancient version of Easy-PC) specifies sizes in thousands of an inch (thou) (as "thou" is a widely used engineering measurement I won't convert to metric), I work with: 15 thou for tracks that pass between i.c. pads, 31 thou for most other tracks, 19 thou sometimes if board space is at a premium in a particular area.

Round pads will be ok for i.c. pads. My oval pads are 50 thou at the narrow point, 100 at full length. The clearance between i.c. pads should be about 50 thou, allowing 15 thou tracks to pass through without danger of etching infill at that point. Overall use of 15 thou is avoided to ease etching for those who do their own, and to avoid current/resistance problems in some situations.

The smaller round pads you see me using are 75 thou diameter but I don't run tracks between them. The pads for 1mm pins I normally use 85 thou dia. Inner hole sizes are normally set for 31 or 35 thou. Pads must have inner holes to allow for correct drilling accuracy (and drill bit slippage – which causes immediate breakage of the 0.8mm tungsten carbide bits I use at 18k r.p.m.!)

BP Monitoring

Dear EPE,

I read George Chatley's letter (*Readout* Apr '05) about measuring blood pressure. I don't think his blood pressure meter needs calibrating at all; the results are varying because his blood pressure is varying, not because the meter lacks precision. Some facts to mull over:

Blood pressure, like heart rate, varies throughout the day. It varies with the way you measure it: whether you are standing up or lying down, for example. It is different when you are stressed compared to when you are relaxed. Depending on your age, you need to leave more "recovery" time between measurements; the body is not perfectly elastic. I suggest at least 15 minutes between measurements.

Perhaps George thinks that measuring blood pressure is like measuring voltage or frequency, i.e. constant if the conditions don't change. It isn't, that's why medics only take one measurement, and the measure is only an indication of trends. I once asked a doctor who had just measured my blood pressure, "What's the error in that single reading?". He just looked at me and probably thought I was an idiot.

**Norman Dyson (Ph.D., not M.D.),
via email**

Thanks for that Norman.

C Side For PICs

Dear EPE,

I have recently discovered your great mag. The PIC articles and projects are really awesome. However, let's face it, most of us, especially newbies to PICs like myself, prefer to code PICs in C, and although assembler is great (?), having the C code as well would be even better.

There is a new compiler/IDE that has a free demo, and the full version is very competitively priced (no I don't work for the company). I believe that this would be an excellent platform for the enthusiast, as it covers all the PICs.

The free version is limited to a generous 2kB of word code. Its URL is: <http://www.mikroelektronika.co.yu/english/product/compiler/mikroc/index.htm>

Maybe (please) you could run a series of articles introducing C, and then include C routines with all future PIC projects and articles?

Dale Stewart, Australia, via email

Thanks for your comments Dale. Personally I have no wish to code in C, preferring the compactness that assembler gives. However, if readers should offer us interesting PIC designs coded in C, we would be quite happy with that, providing the associated HEX file was in the standard MPASM format.

You will have noticed that Andrew Jarvis took a brief look at the "C Side" in his last two PIC 'n Mix columns.

Another Spontaflex Site

Dear EPE,

Referring to the Spontaflex circuit (Apr '05), it might interest some of your readers to know that there is a website

entirely devoted to discussion of the radio circuits of the late Sir Douglas Hall. It is called Radioconstructors and can be found on Yahoo groups.

John North, via email

*Thanks John, I assume you mean:
[www.spontaflex.free-online.co.uk/
database/newsdhcvsdoc.htm](http://www.spontaflex.free-online.co.uk/database/newsdhcvsdoc.htm) and
[http://groups.yahoo.com/group/
radioconstructors/](http://groups.yahoo.com/group/radioconstructors/)*

More Scope?

Dear EPE,

I was wondering if John Becker is considering upgrading his *Dual Channel Oscilloscope* in October 2000 *EPE*. The problem is my college has gone to Windows XP. This makes the printer port and Quick Basic unusable. I was thinking of changing the scope to a USB port; but, what do you do with Windows graphical interface? This was a great inexpensive project for students to build and use while learning. Any other Ideas?

Lynden McIntyre, via email

Well Lynden, I did say to myself after my last scope that that's enough of scopes for this lifetime! However, what with XP and some other platforms unsuitable for the 2000 design, and its ADC becoming obsolete, I may relent sometime, but don't hold your breath!

If you're after something urgent, try Pico Technology's range of PC-based ready-mades.

Waterproof Magnetometer

Dear EPE,

I am in the process of building up your *Magnetometer Logger* (Jul/Aug '04) and am wondering if you have any information regarding construction of an underwater sensor for the logger. I've looked through several forums and their archives with little success. I hate to re-invent the wheel if such information is available. Thank you for your articles and time!

Jim Reagan, Tucson, Arizona, via email

No, sorry Jim, I don't have any advice on waterproofing the unit. It would also need to be pressure-proofed as well as waterproof. As you probably know, water pressure increases by one Bar for every 10 metres of depth, which could readily get round normal seals, and even into cabling.

Text Editor

Dear EPE,

I was shown this text editor while on a course recently: www.editplus.com.

You can install an add-on to allow editing of Microchip ASM files.


David Ardis, via email

Thanks David, it looks interesting. Although I'm content with the editors I variously use (DOS Edit, Notepad, Wordpad) for PIC code writing, readers on the lookout for an editor to suit them should take a look.

It's a shareware product I see, but has 30 days free evaluation time, after which you can purchase full rights for US \$30.

Catch the Wave

Mark Williamson

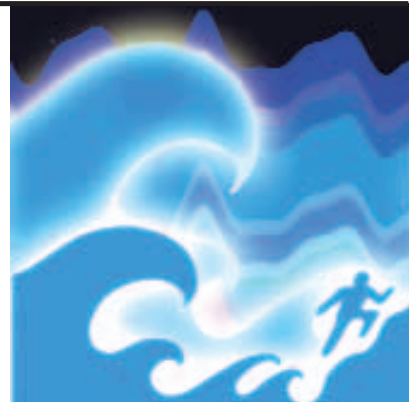

Can science and technology reduce the loss of life associated with such cataclysmic events as the December 2004 tsunami in the Indian Ocean?

THE 26 December 2004 will long be remembered in the Indian Ocean region. It was the day when a magnitude 9.0 earthquake off the coast of Sumatra triggered a tsunami which, within a few hours, had taken the lives of more than 250,000 people.

As is often the case these days, satellite imagery provides a window on the world's disasters. Following the Asian tsunami, the three commercial US imaging firms – DigitalGlobe, Orbimage and Space Imaging – reported the collection of some 80,000km² of imagery of the area in the first week alone.

Since then, the Indian Space Research Organisation (ISRO) has been using four of its own satellites for damage assessment, and processing data from these and other European and Canadian satellites at the National Remote Sensing Agency in Hyderabad. The US government has also helped in the disaster relief effort by declassifying imagery of the region collected by its spy satellites.

But all this is after the event. What about the detection and early warning of tsunamis?

Warning System

Unsurprisingly, in a world where satellites measure sea levels to centimetre accuracy, it falls to orbiting technology to monitor oceans. Perhaps more surprisingly, the technology of tsunami detection via satellite is only in its infancy.

An experimental system, Deep-ocean Assessment and Reporting of Tsunamis (DART), was deployed in the Pacific Ocean by the US National Oceanic and Atmospheric Administration (NOAA) in 1999. Linking six sea-floor pressure sensors to a NOAA satellite, the system forms the latest component of the Tsunami Warning System, a cooperative venture of 26 states and countries that monitors seismic activity and tidal regimes throughout the Pacific Basin. According to David Green, of NOAA's National Weather Service, "DART is unique in its capabilities and scope".

In essence, the system's operation is simple: if a tsunami passes over a sensor, it registers the additional weight of water and uploads the data, in the form of acoustic



Lhoknga, near Banda Aceh on the west coast of Sumatra before the tsunami



Lhoknga, after the tsunami, showing the mosque (white circular feature) as the only building standing




DART buoy

signals, to a hydrophone attached to a buoy on the surface. The buoy then uplinks the data to NOAA's Geostationary Operational Environmental Satellite, *GOES-West*, stationed permanently above the equator, which passes it immediately to ground-based receiving stations. The tsunami warnings themselves are issued from bases in Hawaii and Alaska.

False Alarms

DART's sensors are capable of detecting wave-height differences of as little as a centimetre, which of course occur during normal conditions. However, since ordinary wind-blown waves have a much shorter period, or wavelength, than tsunamis, they can be easily filtered out. Interestingly, it is the long period nature of the tsunami, and the massive volume of water this implies, which leads to its devastating power (see *Tsunamis – What, How and Where?*, on the next page).

According to Eddie Bernard, director of NOAA's Pacific Marine Environmental Research Laboratory in Seattle, apart from better predicting the height and duration of tsunamis, the DART system can help to eliminate false alarms. In 2003, when a tsunami warning was issued by the Alaska centre following a 7.5 magnitude quake in the Aleutian Islands, "the system determined that the tsunami was not a threat to Hawaii," explains Bernard, thus saving the State of Hawaii "about \$68m in lost productivity if the area had been evacuated".

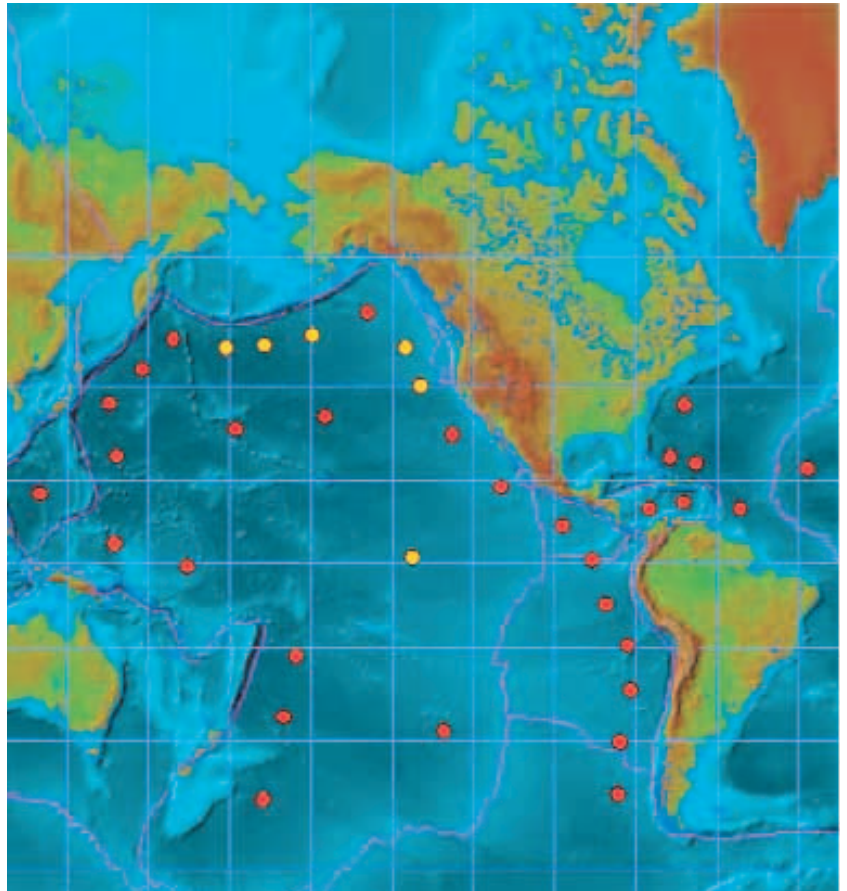

DART sensor sites, in place (yellow) and proposed (red)


The cost of developing and installing the six "tsunameters" was about \$10m. There are currently three in the Gulf of Alaska, two off of the coast of Oregon, and one north of Hawaii. According to David Green, three buoys are "currently awaiting maintenance", which will happen, somewhat ironically, "as soon as the weather permits".

However, following the Asian tsunami the US committed \$37.5m to enhance DART with 32 new buoys and complete a fully-operational tsunami warning system by mid-2007. "This recent tragedy points to the need to complete the Pacific buoy network as soon as possible," said Green. "The additional buoys will enhance DART operations with more efficient, effective and robust capabilities."


According to Simon Day of University College London and the University of California at Santa Cruz, there are "no problems, in principle, in extending a tsunami warning system to the Indian Ocean". Since the region already operates a cyclone warning system, used in anger several times a year and therefore subject to regular tests, its communications network could readily be applied to tsunami warnings.

International Coordination

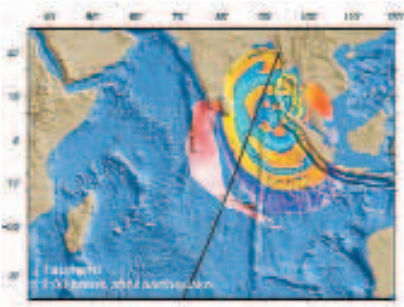
Satellites are crucial to modern-day weather forecasting, climate monitoring and disaster relief. For example, satellites and the associated ground-based infrastructure routinely save hundreds of lives each year by providing hurricane warnings to Florida and the Caribbean islands. In



Tsunami – 2 hours after earthquake

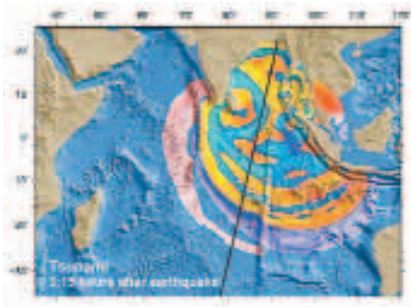


Tsunami – 3.15 hours after earthquake

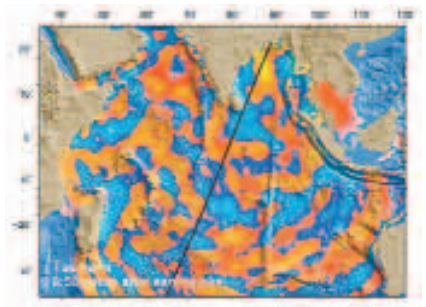

Tsunami – 8.50 hours after earthquake

TSUNAMIS – WHAT, HOW AND WHERE?

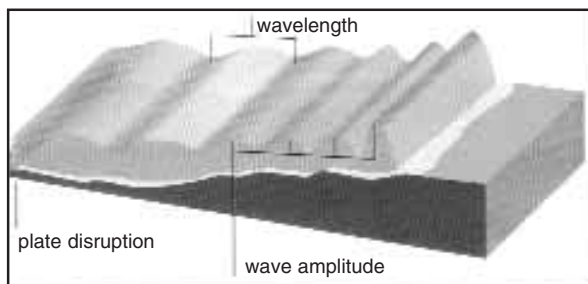

Tsunamis are large waves caused by submarine earthquakes and volcanic eruptions, subsidence and landslides, or even asteroid and meteor impacts. The word itself is derived from the Japanese for port (tsu) and wave (nami), presumably because they were first noticed in the shallower waters of seaports.

Major earthquakes typically occur where an ocean tectonic plate is subducted or pulled under a continental plate. When friction between the plates restricts movement, stresses build up. They can be released either in a gradual process or in a sudden slip which causes an earthquake. When this occurs under the sea it can produce a tsunami.

The Asian tsunami of December 2004 – estimated to be up to 15m in height – was the result of a large earthquake which occurred where the India tectonic plate is subducted beneath the Burma plate. Whereas the Pacific Ocean is surrounded by subduction zones and associated trenches, in the so-called “ring of fire”, the Indian Ocean has only one main zone near Indonesia, marked by the Sunda Trench, which means that quakes and tsunamis should be rare.

Tsunamis in the Atlantic Ocean are far less likely because of the lack of subduction zones, but it has been suggested that an unstable part of Gran Canaria in the Canary Islands could result in a landslide-derived tsunami which would devastate America's eastern seaboard.

Whatever the trigger, any vertical thrust under the ocean acts as a natural wave generator. This is not a problem out to sea, since it manifests itself as a long period swell, typically less than a metre in height. However, its wavelength may be measured in hundreds of kilometres, which means that the wave contains a large volume of water. As it nears the shallows of a coastal plain, the water within the wave has nowhere else to go but “up” and builds into an increasingly high wall of water, a *tsunami*.

Example tsunami:

27 August 1883: Eruptions from the Krakatoa volcano caused a tsunami that drowned 36,000 people in the Indonesian Islands of western Java and southern Sumatra. The waves were so powerful that they pushed 600-tonne blocks of coral onto the shore.

15 June 1896: A wave “more than seven storeys tall”, spawned by an earthquake, killed 26,000 people in villages along the east coast of Japan.

22 May 1960: A magnitude 8.6 earthquake in Chile created a tsunami that hit the Chilean coast within 15 minutes. The surge, up to 25m high, killed an estimated 1500 people in Chile and Hawaii.

17 July 1998: A magnitude 7.1 earthquake generated an estimated 12m-high tsunami in Papua New Guinea that killed 2200.

November 2000, in recognition of the need for better coordination of space-based assets, the European, French and Canadian space agencies created the International Space and Major Disasters Charter.

Since then, joined by other agencies around the world, the charter's standing protocols have been invoked many times, as they were on 26 December 2004 when ISRO, the French civil protection service and the UN Office of Outer Space Affairs all notified other members of the crisis. In effect, the charter provides a 24-hour global watch, which coordinates member nations' satellite infrastructure in an attempt to provide early warning of pending disasters.

In Conference

Certainly, the Asian tsunami has added momentum to these efforts. A conference to discuss the possibility of a tsunami warning system for the Indian Ocean was organised by the 10-member Association of Southeast Asian Nations (ASEAN) within days of the disaster.

Indonesia's President Susilo Bambang Yudhoyono announced in early January that “Indonesia and other neighbouring countries plan to set up an early warning system to prevent natural disasters, including earthquakes and tsunamis”. Meanwhile, at a conference on disaster prevention in the Japanese city of Kobe, the United Nations agreed to develop an early warning system for the Indian Ocean which could be ready in 12 to 18 months.

Moreover, adds NOAA's David Green, “the recent event demonstrates the need for

a Global Earth Observation System of Systems (GEOSS), which would greatly enhance the world's tsunami monitoring capabilities”.

Time To Run?

A crucial question in all of this is how much warning tsunami detection systems can provide. Wave-height data from the French space agency's *Jason* satellite clearly indicates that the east coasts of India and Sri Lanka were hit by the recent tsunami about two hours after the earthquake; for Aceh it was a matter of minutes.

The fact that the Pacific Ocean is much larger than the Indian provides a great deal more breathing space. For example, calculations regarding an earthquake off the coast of Chile show that a resulting tsunami would take more than 14 hours to reach Hawaii and 22 to reach Japan.

Of course, detection is one thing and disaster prevention is another, since it requires fast analysis and reliable communications. As Simon Day points out, “an effective tsunami warning system doesn't just consist of detectors, but the communication systems and public education support as well”.

Part of this is educating people to read nature's signals and act accordingly. While many TV viewers now realise the role of submarine earthquakes in generating tsunami, few would recognise the mysterious withdrawal of the ocean as warning of imminent inundation.

In the case of the Asian tsunami, explains Day, a zone of subsidence to the east of the

plate boundary produced an eastbound wave train led by a trough, as opposed to a peak. This was manifested on the coast of Thailand by a “drawdown” of water into the trough, which exposed a section of the ocean floor, followed by the peak of the wave which brought the well-documented destruction.

According to Day, “the time interval between the two was between 15 and 30 minutes in different places”. Unfortunately, rather than providing a useful warning, this was “more than enough time for people to be tempted down to the shore to look”. What they should have done, says Day, was to “start running when the sea drew back”.

Moreover, tsunami events usually feature anything between half a dozen and a few dozen major waves, formed as the sea level in the source region oscillates up and down. Frequently, says Day, the largest wave crest is somewhere between second and fifth in the sequence, “so another commonly fatal mistake is to go back to the shore to look at the damage from the first wave”.

In the final analysis, local inhabitants may be made aware of the potential dangers, but even then they will have to be awake when the wave comes. And when it does, the only practical option is to flee to higher ground or the upper floors of substantial buildings. Despite such qualifications, it's clear that an effective warning system would have substantially reduced the death toll from Asian tsunami. □

Reprinted from *The IEE Review* by permission of the author and the Institution of Electrical Engineers. ©IEE 2005.

PLAYING TAG

Developments of all kinds are opening ever more applications for the ingenious technology of r.f. ID tags, declares Mark Nelson

TWO years ago in *Tiny Tags Talk Volumes* (May 2003 issue) I reported that barcodes on shopping were set to disappear as new radio-activated ID "tags" took over, also that tagging would take off as soon as the cost of the tags dropped to 1% of the cost of the product they were applied to.

RFID stands for radio frequency identity and the tags act as a kind of barcode mark that is read by radio. Tags can be active (with an integrated battery) or else passive (deriving energy from the r.f. field generated by the reader). Active tags have a longer range and can transmit more information but carry a heavy cost penalty. Passive tags are much lighter, less expensive and should last more or less forever. Back then the chief application for radio tagging was seen as retailing and, to a lesser extent, personal airline baggage.

Fast Forward

That was then and this is now; the retail angle is developing nicely, notwithstanding some rather weak lobbying by civil liberties activists, who think RFID tags will disclose our shopping habits (obviously they are unaware of supermarket loyalty cards). In the best tradition of disruptive technologies, however, radio tagging is developing entirely new, unforeseen application areas for itself and it's these that we shall explore chiefly now.

One of the applications being touted two years ago was the tagging of humans. Not criminal, I hasten to add, but tagged armbands were being trialled for visitors at two theme park attractions in the USA. Wearing the right armband would give you alone access to your own luggage locker, whilst tags programmed in other ways would let you bypass the queue for rides, also pay for merchandise and refreshments without the need for cash.

McDonalds envisaged keyfobs containing RFID tags as a faster means of payment for hamburgers, with Taco Bell and Kentucky Fried Chicken also trialling this system.

Human Barcodes

These days state security is the growth market for tagging, fuelled by mounting concern over global terror and inadequate immigration controls. Under European legislation being considered in Brussels, governments would have the ability to monitor the movements of criminals and suspected

terrorists by installing RFID chips under the skin of immigrants. It's not as abhorrent as it sounds, according to experts, especially as we consider it fine for our pets. These "human barcode" chips are no larger than a grain of rice and can be inserted painlessly in the fatty tissue below the triceps of human beings.

An official think-tank of the European Commission, the European Group on Ethics (EGE), had its controversial proposal for legalising the microchipping of humans approved during March (no, not on 1st April!). Its title is *Ethical Aspects of ICT Implants in the Human Body*, and you can read it at: www.egovmonitor.com/node/248.

According to the EGE the technique can be used for tracking criminals, people on parole and ex-convicts and it also describes a prototype "body-intrusive" satellite tracking device known as the "Digital Angel". This could be used to track stalkers, suspected terrorists, even politicians and others in high-risk occupations. Of course this and other blue skies speculation would of course require legislation that could very likely encounter stiff resistance from civil liberties groups. Public opinion could easily be swayed, however, if we had more city centre outrages of the Madrid variety.

Pay Attention, Bond!

The full text of the report, europa.eu.int/comm/european_group_ethics/docs/avis20en.pdf, goes much further, reading almost like a James Bond scenario. The "Smart Gun" is one idea, announced already in April 2004 by Applied Digital Solutions (ADS), which created the VeriChip in partnership with gun manufacturer FN Manufacturing.

Smart Gun weapons can be fired only if operated by their owner with an RFID-chip implanted in his or her hand. Even more fantastic is the proposal for an audio tooth implant or tooth phone. Nothing to do with Bluetooth, this was designed in 2002 although it exists only in concept form so far.

A micro-vibration device and a wireless low frequency receiver are implanted in the tooth during routine dental surgery. The tooth communicates with an array of digital devices, such as mobile telephones, radio and computers (perhaps it does have something to do with Bluetooth after all!). Sound information is transferred from the tooth into the inner ear by bone transduction. Sound reception is totally discreet enabling

information to be received anywhere at anytime.

If that sounds crazy to you, Bill Gates begs to differ. Microsoft patent number 6,754,472 (22 June '04) concerns the human body as a medium for transmission of data (and energy) to "other devices" such as PDAs (Personal Digital Assistant), cellular phones, medical devices (for surveillance purposes: like for instance in retired people's homes), RFID making it possible to localize other persons. In a family website your children could log onto the surveillance system and look at what their parents or grandparents are doing. The patent does not describe any specific device, however.

Phone Hangup

Staying with the communication theme, but back in the realms of current reality, radio tagging is also seen as a means to stem the escalating theft of mobile phones. Newspaper reports talk of truckloads of mobiles filched by street muggers (300 thefts are reported every day in London alone) being exported to developing markets in Eastern Europe and Russia.

Determined to break the chain, the mobile phone industry is considering fitting chips in phones sold here. In Japan chips are already fitted to many phone models sold for children; parents can then keep tabs on their offspring's location thanks to satellite tracking. Whether this same technique could thwart the mobile mafia is another matter, since even if the tags were fitted in a way that prevented removal without destroying the phone, the chances of recovering the stolen phones and apprehending the criminals might be rather slight.

Enterprise News

Finally, what of retailing? In January Tesco announced a further implementation of RFID tagging for tracking goods between warehouse and store. Marks & Spencer will extend the technology to 53 stores and in Germany the Kaufhof department store chain has completed tests in two of its stores, whereby RFID tags alert till scanners when shelves need restocking of particular goods.

Across the Atlantic, retail giant Wal-Mart uses RFID tags on all cases, containers and pallets to keep precise tables on goods from the moment they leave the maker to the time they arrive in-store. It's still early days but it's unlikely that the progress of radio barcodes will stop now.

PIC Ultrasonic Radar

John Becker

Let your mobile robot listen to the landscape and weave amongst the obstacles with this experimental system

SO it came to pass that Max Maxfield of *Bebop to the Boolean Boogey* fame, and coordinator of our Online site, emailed Editor Mike suggesting that it was time to publish a PIC controlled Ultrasonic Radar scanning module for use with mobile robots. "John?", says Mike. "Yes, why not?", responds the author, intrigued by the scandalous fun that designing one might provide!

Well, the author had already done one many moons ago (maybe 170) for *EPE*'s one-time sister mag *PE*. That circuit had been designed around numerous logic chips, a d.c. motor, and an interface to an early PC via its main bus network, using QBasic as the principle control software for the screen display. It was very effective for its time. But things have moved on, and there are now better ways of doing them ...

Listening to the Landscape

This updated design uses a PIC micro-controller and a stepper motor, with optional serial interfacing to a modern PC (Win 95, 98, ME or XP compatible) with Visual Basic 6 (VB6) providing a more sophisticated visual display.

Whilst the design can be used as a standalone system, with or without PC interfacing, it is intended as a basic electronic framework whose software can be modified by readers to tailor it for use with their own mobile robot models. It is, for example, ripe for integrating with Owen Bishop's recent *Smart Kart* robot buggies.

It must be said, though, that to get the best out of both the *Smart Kart* and this Radar interface, readers should be familiar with writing PIC programs, and have the means for programming their own PICs. They should also have VB6 on their PC, and be capable of using it if they wish to modify the Radar's PC interface.

The module provides a rotating ultrasonic scanner which can be mounted on the model robot. It transmits ultrasonic pulses, listens for returning echo signals and records their amplitude. In the prototype, a 48-step stepper motor (7° per step) controls the scanner's rotation, through a maximum arc of 360°, selectable down to 0° (static scanning).

Stepper motors having other step quantities, such as 96 steps at 3.5° per step, may be used. But it is debatable as to whether

more steps than 48 would be beneficial, because of the ultrasonic radiation pattern (see later).

Ultrasonic Transducers

Conventionally, most ultrasonic transceivers use two transducers, one for transmitting, the other for receiving. The transmitting and receiving transducers for such units are usually manufactured to different specifications. Those designed as transmitters have a low impedance to allow greater power output, whereas the receivers generally have a high impedance.



However, there are situations in which either type may be used interchangeably, as in the author's *Wind Speed Meter* (Jan '03) and *Met Office* (Aug '03), for example, where a pair of transducers alternately exchange roles in order to assess wind speed. It also follows that it is possible with some applications to use a single transducer which transmits the ultrasonic pulses and then receives their echoes. Many depth sounders use this technique.

A small drawback of using a single transducer is that the minimum echo detection limit is lengthened due to the "ringing" time of the transducer following the end of the transmission pulse. This can be as long as three milliseconds. In air, at sea level and at 0°C, sound travels at 1120 feet per second (330 metres) and so 3ms represents a distance of around three feet (1m) – an echo target distance of 1.5 feet (0.5m).

A compromise between power output and input sensitivity must also be accepted with single transducer units. However, even when using two transducers there can still be sympathetic ringing of the receiver if its circuit is in close proximity to the transmitter.

In the situations where the current prototype (and its predecessor) has been used, a single transducer was found to be satisfactory. It worked equally well with either transmitting or receiving devices as the transducer. The circuit has been designed, though, to allow constructors the choice of twin transducers if preferred.

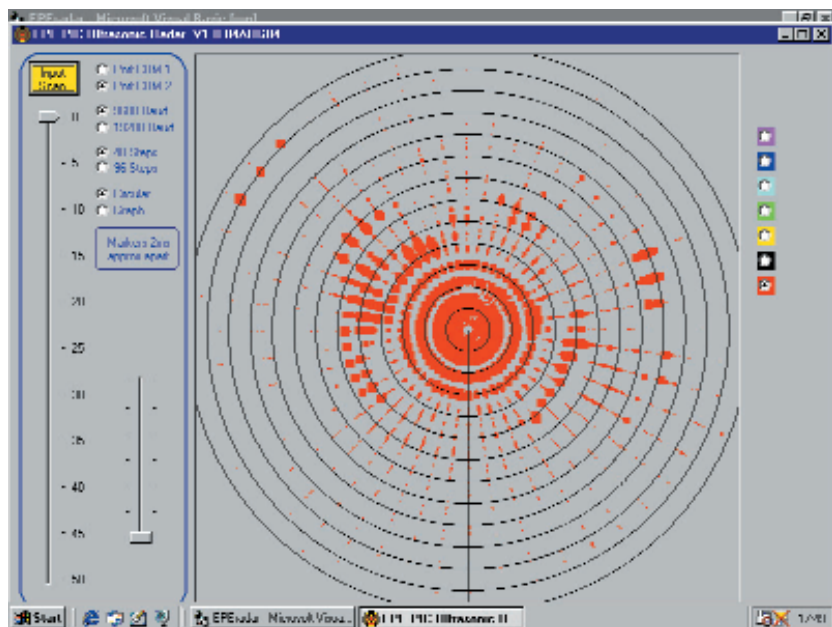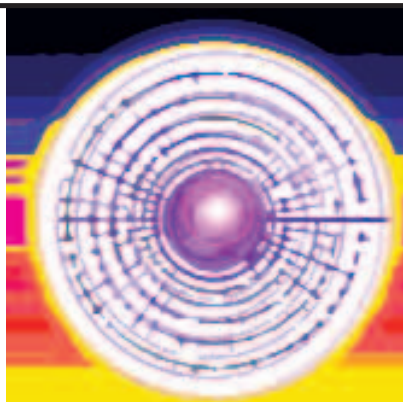Ultrasonic transducers tuned to a variety of frequencies from 25kHz to over 455kHz



Example scan display as produced on the PC screen

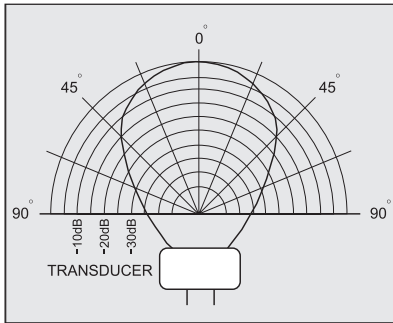


Fig.1. Typical 40kHz transducer directional radiation pattern

are manufactured, although those most widely available to the hobbyist constructor are the 40kHz variety. This Radar module has thus been designed for use with a 40kHz device. Devices having other frequencies may be used, but the PIC software would need to be modified to generate the output frequency.

The 40kHz variety have a transmission beam width of typically between 20° and 30°, as illustrated in Fig.1, for a 30° device. This wide angle inherently restricts the resolution of echo-direction determination. Ultrasonic distance and direction finders can never provide the clarity of information as can be achieved, for example, by laser-based designs, let alone the pin-point clarity of images that can be achieved optically, as in camera-based systems.

Nonetheless, in robotic applications such as those envisaged for this design, the resolution is more than adequate for the robot's software to determine whether or not a reasonably sized object is in its path, as might be presented in a maze or target avoidance application. It is up to the user, though, to write the PIC program to suit the size and distance at which responses to targets should occur. As said, this design is just a basic *framework*, and the software must be tailored to suit the user's needs.

As a suggestion, it might be worth experimenting with the number of ultrasonic pulses transmitted with each batch (12 at present) to perhaps sharpen the definition (fewer) or distance (more). You might also try narrowing the ultrasonic beam width by mounting the transducer in a tube of some sort (one whose walls are impervious to 40kHz signals).

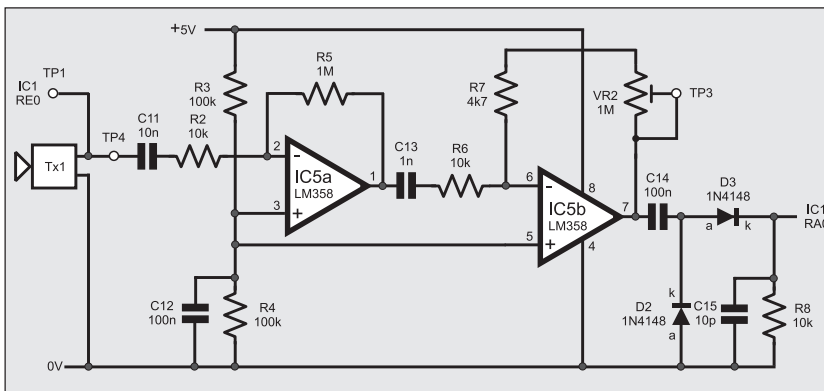


Fig.2. Circuit diagram for the ultrasonic transmitter/receiver

Transceiver Circuit

The circuit diagram for this design's ultrasonic transmitter/receiver function is shown in Fig.2. The ultrasonic transducer is notated as TX1 and, as said, is used bi-directionally. The 40kHz transmission pulses are output to TX1 by the PIC microcontroller, from its pin RE0, as detailed later. TX1 is also capacitively connected (via C11) to the ultrasonic amplifier based around op.amps IC5a and IC5b, whose output signal amplitude is read via the PIC's pin RA0.

Although the amplifier will react to the transmission pulses, the PIC ignores the signal on pin RA0 during transmission. Once transmission has ceased, the amplifier's gain allows it to pick up the returning echo signals, raising them to a level suitable for reception and processing by the PIC. The gain at IC5a is about 100, while that at IC5b is adjustable by preset VR2 to between about 0.5 and 100, allowing plenty of amplitude range to be set.

The output from IC5b is a.c. coupled by C14, half-wave rectified by diodes D2 and D3, and then very slightly smoothed by capacitor C15 and resistor R8.

For those who might care to use separate transmitting and receiving transducers, Fig.3 shows the simple modification to the circuit in Fig.2. On the printed circuit board, a single link wire physically determines which mode applies. The software *does not* need changing if the Fig.3 configuration is used.

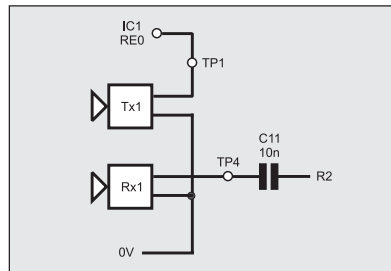


Fig.3. Connections for separate transmitting and receiving transducers

Stepper Motor

Stepper Motors and their control were discussed at some length by (sadly missed) Andy Flind in his *PIC QuickStep* article of June 2004. Readers are referred to this article for more information on stepper

motors. It is, though, worth repeating a few facts from Andy's excellent text.

Andy comments that there are various types of stepper motor and that his article is concerned only with the four-phase type as it is the most common. Such motors may be bought new from suppliers or salvaged from old computer equipment, such as printers and scanners.

They may have several step ratios per revolution, such as 48 or greater, having equivalent step angles of 7° or less. (The prototype Radar uses a 48-step motor, although the software can alternatively be set to suit 96-step motors, step angle 3.5°).

The motors are likely to have either five or six connecting wires, four of which connect to four internal stator coils whilst the other(s) are "common" connections to the coils. Sometimes the coils will be arranged as two pairs with a common lead each (see Fig.4), sometimes all four will share a common lead. Fig.5 shows a greatly simplified diagram of the connections to a four-phase stepper motor.

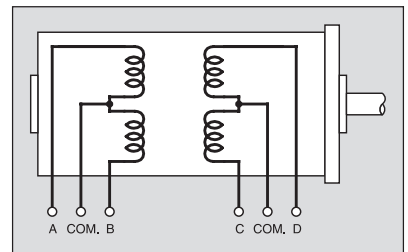


Fig.4. Connections for a four-phase unipolar stepper motor

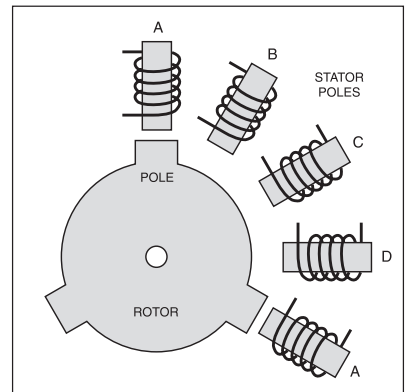


Fig.4. Connections for a four-phase unipolar stepper motor

The rotor poles are shown facing stator coil A. If coil B is briefly energised, the rotor will turn one step to face it. If coil C is then briefly energised the rotor will turn to face it; similarly for coil D, and for coil A again. By energising each coil in the sequence A, B, C, D, A, etc, clockwise rotation is achieved. Powering the coils in the opposite sequence, A, D, C, B, A, etc, produces anticlockwise rotation.

Powering one coil at a time is known as *wave* operation and has the advantage of low supply current and, if the supply is turned off, the motor is likely to stay where it is due to the attraction of the permanent magnet rotor to the last energised pole.

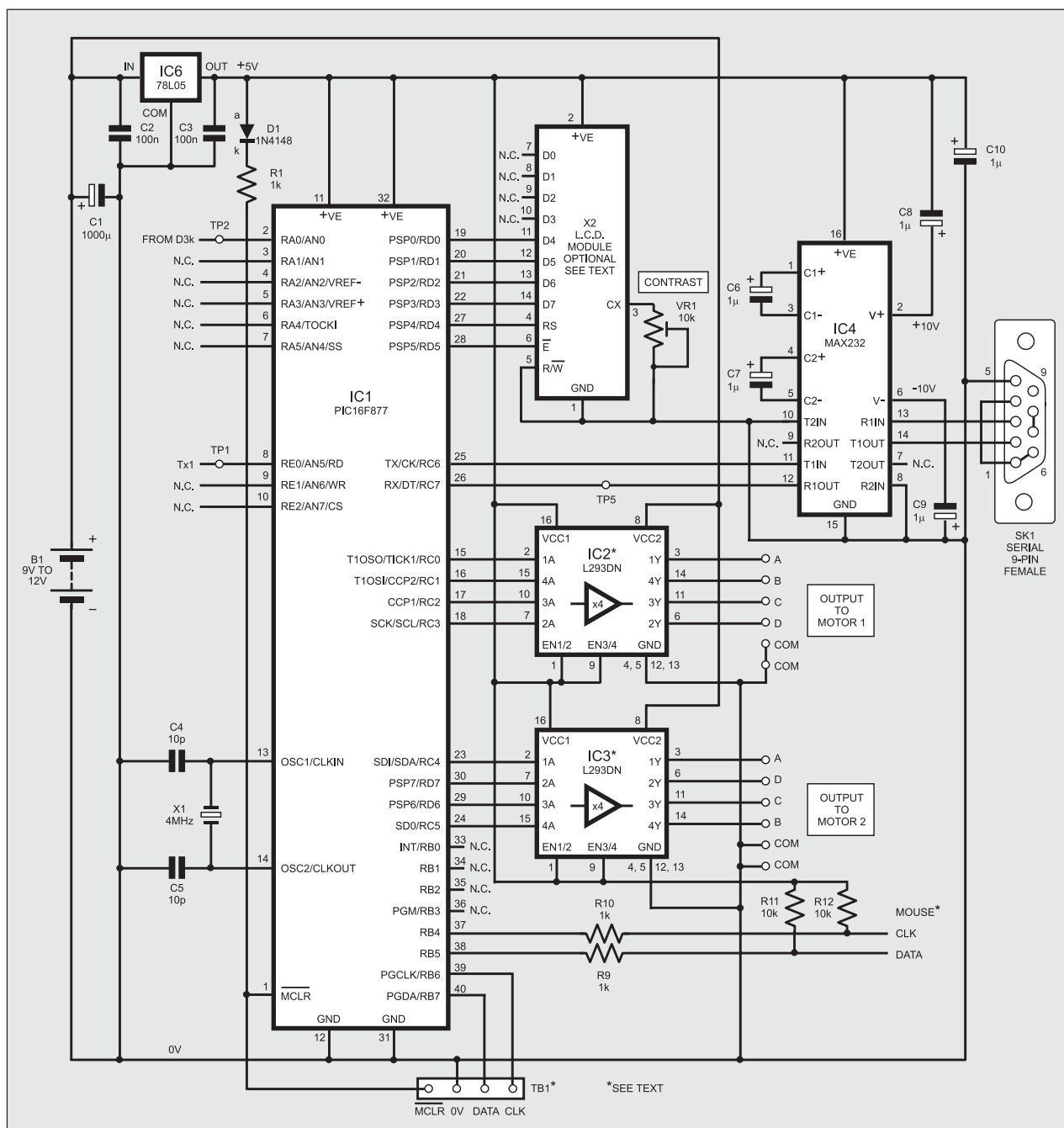


Fig.6. Circuit diagram for the Digital Control aspect of the Ultrasonic Radar


Motor Drive

It is the wave mode of operation that has been set into the PIC's Radar software, each coil being put under the control of PIC pins RC0, RC1, RC2 and RC3. The full circuit diagram for the Controller is shown in Fig.6.

There are several techniques by which the coil control signals can be boosted to suit the current required by the coils. Andy chose to use discrete transistors. In this Radar module, though, a quad amplifier chip designed for such applications has been used.

It is known as a half-H type driver and the type chosen is an L293DN. It accepts logic-level control signals (i.e. from a PIC or other digital device) and has internal

Fig.7. Schematic diagram and truth table for a single L293DN amplifier

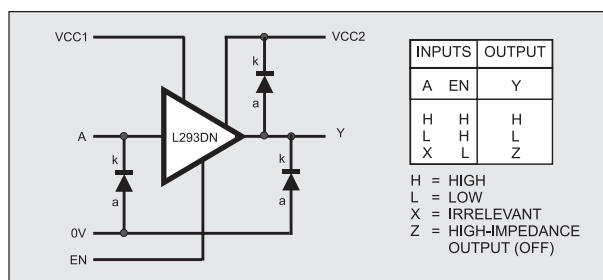

transistors whose outputs can each sink or source a load current of around 1A. Additionally, it has internal back-e.m.f. suppression diodes on each output to eliminate high voltage spikes generated when coils have their power turned off (external diodes were required with Andy's transistor drivers). The schematic diagram of one L293DN amplifier is shown in Fig.7.

It is emphasised that the L293DN *must* have the suffix DN. Other devices of similar name without the suffix have different characteristics which are not suited to this design.

The input and output sections of the L293DN can be powered by separate power supplies, typically +5V for the input, and up to about 36V for the output. This

allows the motor to be powered from a higher voltage source than the control circuit. In this case it is powered directly from the battery which supplies the complete system, B1 in Fig.6, providing between about 9V and 12V d.c.

Interfacing of this chip to the PIC is shown in Fig.6, where it is notated as IC2. It will be seen that a second L293DN (IC3) is also connected to the PIC, via pins RD6, RD7, RC4 and RC5. The use of IC3 is optional, and allows the user to amend the software to control a second stepper motor if desired. The demo software provided with the Radar unit does not include routines for this second motor control.

Note that four consecutive PIC pins (e.g. RC4 to RC7) could not be used for the second motor control, as they are specifically required by other control aspects (Port B being reserved for switch use if desired as it has internal pull-ups, removing the need for bias resistors).

In this application the motor is controlled by positive logic. The PIC outputs +5V to set the respective L293DN output high (e.g. to 12V for a 12V battery). The motor's common terminals are connected to the 0V line and a positive voltage across a coil turns it on.

Optional L.C.D.

The unit has been provided with software and facilities to control an optional liquid crystal display (l.c.d.). This does not *have* to be used, but it could be found useful when writing your own PIC code, using the l.c.d. to monitor the operation of your code. A binary to decimal conversion routine is included with the software to facilitate value monitoring.

The l.c.d. is operated in the author's standard 4-bit control mode, in this case via Port D. Preset VR1 adjusts the screen contrast, and once set for adequate display legibility can be ignored. The demo PIC code shows examples of how the l.c.d. can be used.

Serial Interfacing to PC

Another optional facility allows the radar's scan data to be output to a PC via a serial link. This is provided by the RS232 interface chip, IC4. The facility is the same as that provided by several of the author's previous designs. In common with those designs, the PC's serial software includes Joe Farr's excellent Serial OCX software (originally discussed in *EPE* Oct '03).

The PIC's software basically outputs at 9600 Baud, one stop bit, no parity. However, the PC software provides the option to serially interface at either 9600 Baud or 19200 Baud, the latter rate providing a faster transfer of scanned data. When the PC is set for the faster rate, it automatically sets the PIC to interface at that rate as well.

It is worth noting that if the PIC is operated at a crystal clock speed greater than 4MHz (as set by X1 in Fig.6), higher Baud rates can be achieved if preferred (and your PC allows them). The author's *Toolkit TK3* programming software (V1.5 and upwards) has a Baud rate calculation facility which provides the coding values needed by the PIC for various Baud rates.

It is stressed that the Radar unit can be used on its own without a PC link if you prefer, relying on the PIC program to perform those functions that you need (and have written for yourself!).

Keyboard or Mouse Interfacing

Still in the vein of this Radar module being a "framework" for your own software, the hardware facility to control the unit from either a PS/2 mouse or PS/2 keyboard has been provided. Such concepts were discussed in the author's *PIC to PS/2 Mouse and Keyboard Interfacing* article of Aug '04, with practical demonstrations provided through his *AlphaMouse Game* (Sept '04) and *Moon and Tide Clock Calendar* (Oct '04).

Whereas in the last three articles, Port A was used for the interface, in this Radar module, PIC pins RB4 and RB5 have been allocated for the mouse or keyboard, with buffering and pull-up of their data and clock lines provided by resistors R9 to R12.

The Radar demo software does not include examples of mouse or keyboard interfacing, and interested readers are referred to the previously mentioned three articles.

Other Interface Options

It will be seen that there are several PIC pins which are unallocated. Any of these can be put to use to suit your own programming. For instance, the Radar software has Port A pins RA0, RA1 and RA3 set as analogue inputs, of which only RA0 is used for the Radar.

So, for example, RA1 could be used to monitor the wiper of a potentiometer connected across the +5V and 0V power rails. The PIC could be told to read the analogue voltage at the wiper, and perform a particular function in response to a certain voltage. This would allow external control of any chosen aspect of the Radar's (or robot's) behaviour.

Any of the other unused pins of any port can be put to digital input or output use. For instance, Port B's "light pull-ups" option has been set active by the software, allowing switches to be connected between Port B and 0V. Your software can then be told to read these pins (active-low) and then to take any appropriate action you wish. Such action could include the selection of the number of steps through which you wish the motor to scan back and forth. (This option is provided as standard through the PC interface program.)

The final option provided by the Radar circuit is to allow on-board PIC programming via the terminals notated in Fig.6 as TB1. These are in the author's standard order on the p.c.b. and are compatible with the equivalent pins on the *TK3* p.c.b. Diode D1 and resistor R1 protect the Radar from adverse voltages during programming mode.

Resources

Software, including source code files, for the Radar module is available on 3.5-inch disk from the Editorial office (a small handling charge applies – see the *EPE*

COMPONENTS

Resistors

R1, R9, R10	1k (3 off)
R2, R6, R8, R11, R12	10k (5 off)
R3, R4	100k (2 off)
R5	1M
R7	4k7

All 0.25W 5% carbon film or better

Potentiometers

VR1	10k min. round preset (optional – see text)
VR2	1M min round preset

Semiconductors

D1 to D3	1N4148 signal diode (3 off)
IC1	PIC16F877 micro-controller, pre-programmed (see text)
IC2, IC3	L293DN quad half-H driver (2 off – see text)
IC4	MAX232 RS232 serial interface (optional – see text)
IC5	LM358 dual op.amp
IC6	78L05 +5V 100mA voltage regulator

See
SHOP
TALK
page

Capacitors

C1	1000µ radial elect, 16V
C2, C3, C12, C14	100n ceramic disc, 0.5mm pitch (4 off)
C4, C5, C15	10p ceramic disc, 0.5mm pitch (3 off)
C6 to C10	1µ radial elect. 10V (5 off)
C11	10n ceramic disc, 5mm pitch
C13	1n ceramic disc, 5mm pitch

All capacitor voltages are minimum working values

Miscellaneous

TX1	40kHz transmitter
RX1	40kHz receiver (optional – see text)
SK1	9-pin serial connector, female (optional – see text)
X1	4MHz crystal
X2	2-line 16-character (per line) alphanumeric l.c.d. (optional – see text)

Printed circuit board, available from the *EPE PCB Service*, code 503; 8-pin d.i.l. socket; 16-pin d.i.l. socket (3 off – see text); 40-pin d.i.l. socket; connecting wire; solder, etc.

Approx. Cost
Guidance Only

£37
excl batt &
hardware

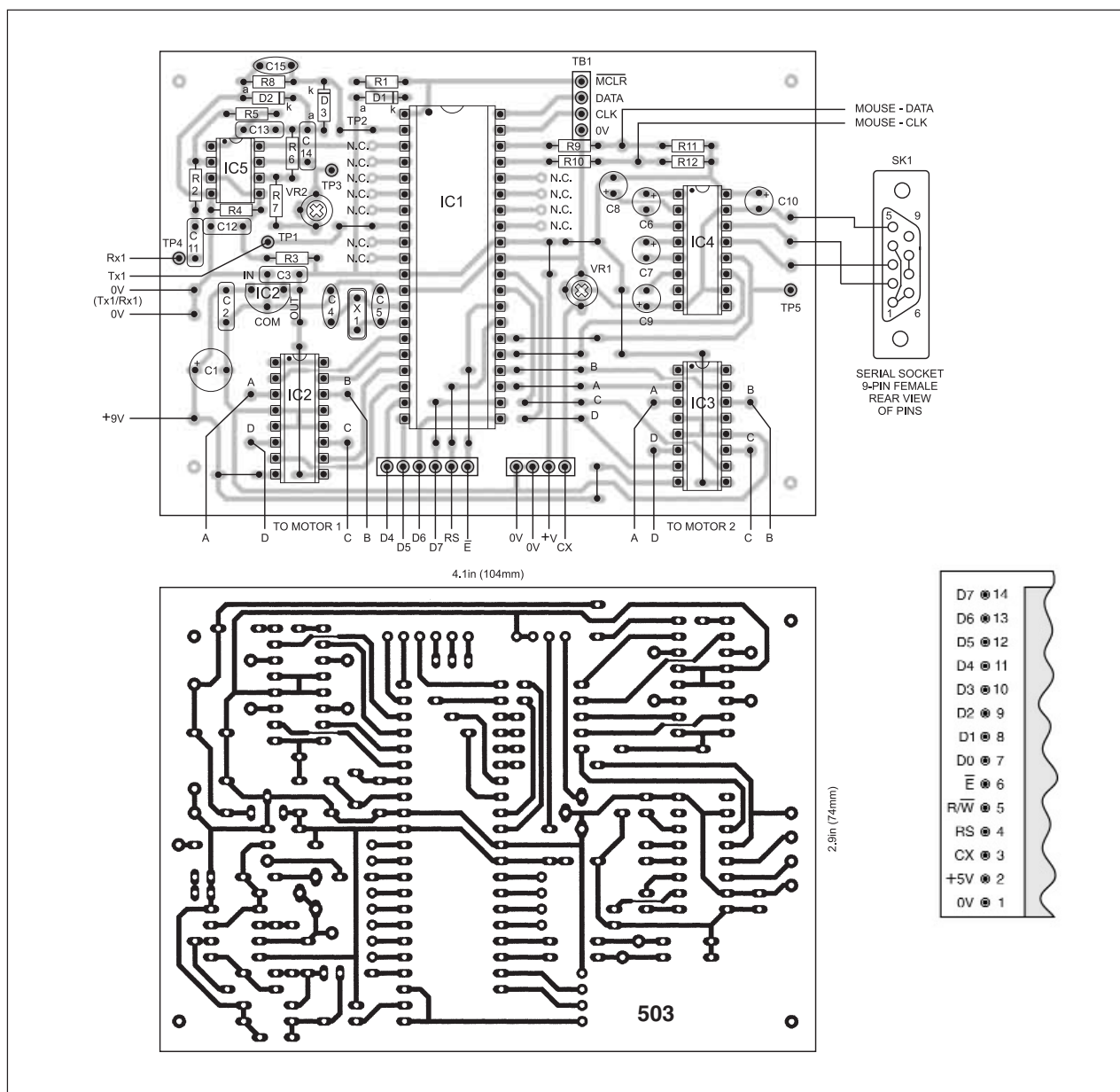


Fig.8. Component and track layout details for the Ultrasonic Radar printed circuit board, plus pinouts for the optional I.C. module

PCB Service page). It can also be downloaded *free* from the *EPE* Downloads page, which is accessible via the home page at www.epemag.co.uk. It is held in the PICs folder, under PICradar. Download all the files within that folder.


This month's *ShopTalk* provides information about obtaining pre-programmed PICs, although it is expected that readers will wish to program their own with their modified software.

The PIC program source code (ASM) was written using *TK3* software (also available via the Downloads page) and a variant of the TASM dialect. It may be translated to MPASM via *TK3* if preferred.

The run-time demo assembly is supplied as an MPASM hex file, which has configuration values embedded in it (XT oscillator, WDT off, POR on, all other values off).

Construction

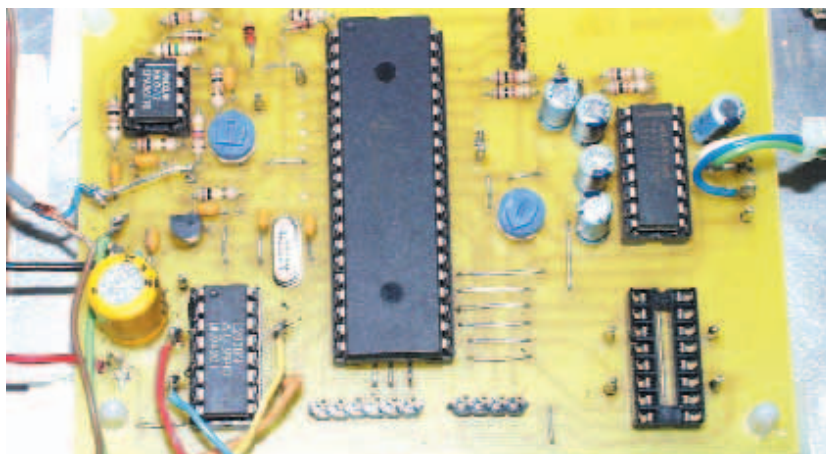The component layout and off-board interconnections for the Radar printed circuit board (p.c.b.) are shown in Fig.8. This



board is available from the *EPE PCB Service*, code 503.

As usual, assemble the components in any order you prefer, but preferably in order of link wires (noting that some go

under i.c. socket positions), and then in ascending order of size. Sockets should be used for all d.i.l. (dual-in-line) i.c.s., but these i.c.s should not be inserted until you have satisfactorily checked

EPE USONIC RADAR
BAUD9600 STEPS48

that the p.c.b. is assembled properly, that all its polarity-sensitive components are oriented correctly, and that the power supply voltages are correct.

The layout details in Fig.8 show connections for both transducers. If only transducer TX1 is to be used, as with the prototype, link TX1 as indicated, omit RX1, and link p.c.b. points TP1 and TP4.

Apply the battery power and check that +5V is present at the output of regulator IC2, and where expected on the i.c. pins, as indicated in Fig.6. Raw battery power should be present on pin 8 of the sockets for IC2 and IC3.

Observe the mandatory requirement that power should be disconnected before making any change to the p.c.b. and its components.

When satisfied by the preliminary checks, insert the pre-programmed PIC and connect the l.c.d. (if required), whose typical pinouts are shown inset in Fig.8. From hereon it is assumed that the l.c.d. is connected.

When power is re-applied, adjust preset VR1 until the l.c.d. screen contrast is satisfactory. It should be apparent that both lines of the l.c.d.

Motor Connection

The next stage is to connect the stepper motor. This will depend on the type of motor which you are using. Guidance on such choice is best provided by what Andy Flind had to say on the matter, of which the following is a precis:

If the motor came with connection data there should be no problem connecting it up to the circuit – letter-notated coil wires going to the same lettered pins alongside IC2, with the common wire(s) connected to one or other of the 0V connection points on the p.c.b.

If the motor was salvaged from scrap equipment, the leads will have to be identified. The “common” leads can be located with a meter. Where a resistance can be measured across any two leads, it will be found that it will be either the value of the coil lead to a common, or twice that value, i.e. two coil leads in series via a common (see Fig.4). So the common(s) will be the lead(s) having the lower resistance value compared to two or more of the others.

Having identified the common(s), connect it/them to the 0V output of a suitable power supply (the Radar uses the opposite control voltage logic to Andy’s *QuickStep*). Next take one of the coil leads, label it A, and touch it to the positive battery supply

motor and transducer separately to the work bench (using Blu-Tack or self-adhesive Selotape Fixer Strip, for example).


Scan Arc

When the motor has been wired in and power is applied to the circuit, the PIC will step the motor through its 48 steps, covering a 360° arc (actually 353° because it takes a 49th step to return to its starting angle). It then reverses direction, stepping back to its start position, before stepping forward again, and so on.

Following each step of the motor, the PIC transmits a brief sequence of 40kHz pulses, it then monitors the echo signal at its RA0 input, sampling it 96 times over the next 25 milliseconds. Each sample is stored to a temporary memory block commencing at PIC Bank 1 address H'A0'. Although sampling is done with 10-bit resolution, only the upper eight bits are used, the lower bits ignored. An 8-bit resolution is quite adequate in this application.

When the PC is connected and its VB6 Radar program running, each 96-byte block is output serially to the PC following the PIC's receipt of the 96th byte. The sequence will be discussed presently.

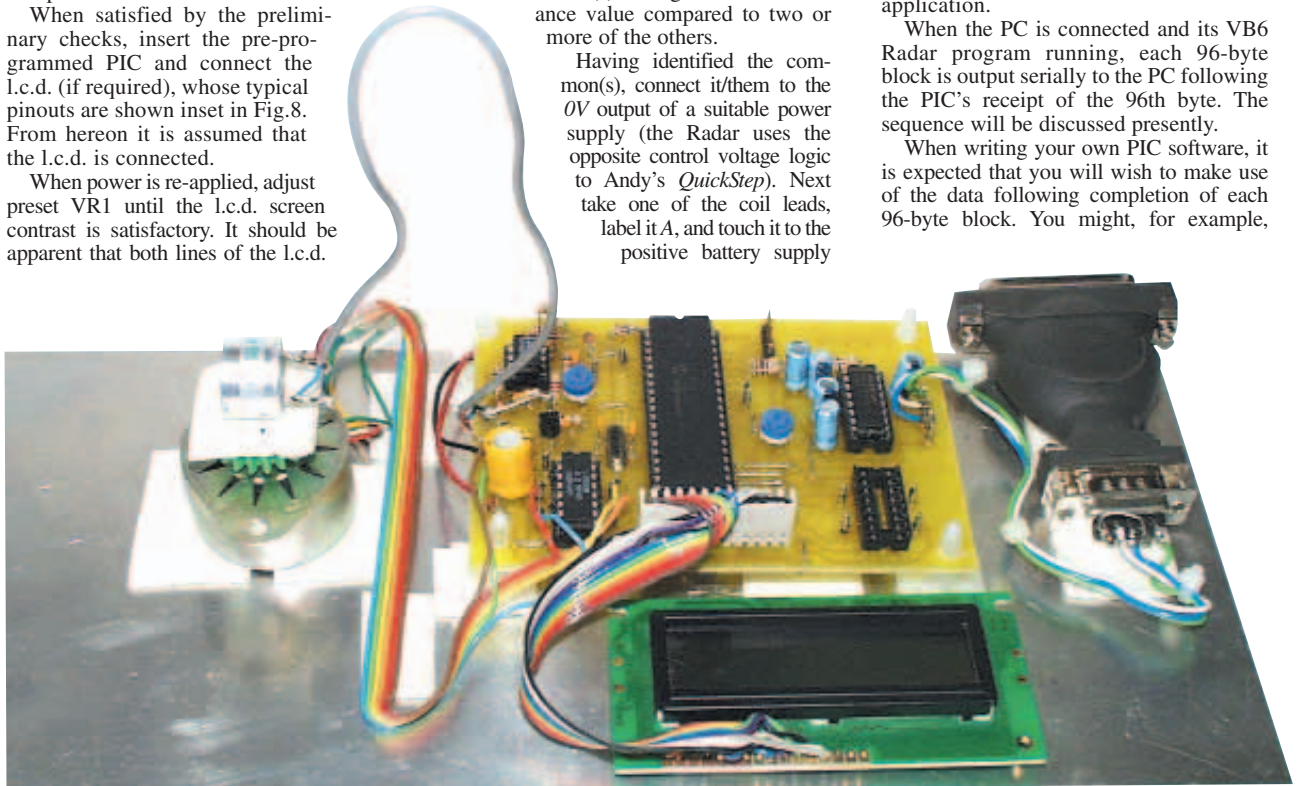When writing your own PIC software, it is expected that you will wish to make use of the data following completion of each 96-byte block. You might, for example,



The prototype mounted on an aluminium test platform while undergoing development tests. Note how the cable to the stepper motor is looped and self supporting (see text)

are in use. If only the upper line is visible, showing 16 dark character cells, there is a fault in the l.c.d.'s initialisation process, likely to be due to incorrect connections to it.

On start up, and the l.c.d. having initialised, its screen displays the two-line message, shown above, confirming that the software is set for the default Baud rate of 9600 and the motor has a rotational limit of 48 steps. Both of these factors are changeable through the PC interface (for 19200 Baud and 96 steps). If you are not using a PC with this unit, however, and you want to set the PIC program for different defaults, you will need to amend its code (the relevant ASM code sections are suitably notated).

pin on the p.c.b. The motor will probably “jump” slightly. It may be necessary to attach something to the motor shaft so that the movement can be seen more clearly (the prototype motor had a cog on its shaft and the movement was readily observable).

Now find the coil lead that gives the smallest clockwise movement when touched to the positive supply. Label this lead B. The motor can be taken back to the starting point before trying each lead by touching A again. Continue similarly to find C and D, following which the leads can be connected to the p.c.b. in the designated order.

At this stage it is recommended that you test the motor without the ultrasonic transducer mounted on it. Simply secure the

wish to determine which echo value occurs in relation to a set field of distance, and then instruct the robot to take a particular course of action in relation to that information.

The sampling period and quantity have been chosen as a compromise between the amount of PIC memory readily available and a reasonable echo distance. The 96-byte value is the number of bytes between H'A0' and H'FF' in PIC Bank 1. You could actually add a further 16 memory bytes if you were to use PIC Bank 2 and its register bytes between H'110' and H'17F'.

The timing value of 25ms represents an approximate signal distance for transmission and echo return of about 25 feet (7.5m), taking the speed of sound as a rounded value of 1000fps. This represents

a maximum target distance of about 12.5 feet (3.75m). In practice, the maximum echo amplitude at that distance will vary with the nature of target, hard reflective surfaces providing stronger echoes than soft targets. It is an area in which you are recommended to experiment, both in terms of the target type, and the gain setting given to the echo amplifier by preset VR2.

When writing your detection software, you may also care to choose the scan angle at which you wish the robot to respond. As the motor is stepped and sample blocks are received, so a counter is incremented in relation to the number of steps taken during the scan arc, i.e. it represents angular values. This value can be read in relation to the echo response signals.

Be aware that the PIC can only store data for one angular step at a time. Although Bank 3 could be used to cover two angles, complications arise in relation to the 16 bytes that are common to all Banks. If you wanted to store all samples for all scan angles, you would need to add an external serial memory chip to the PIC, a facility which has not been provided by the Radar circuit.

It seems unlikely, though, that extra memory would actually have any benefit because of the duration over which the full sampling of the scan arc occurs. In principle, 48 steps at 25ms gives a minimum full-scan duration of 1.2 seconds. But, to this must be added the extra time needed to actually process and do anything with the scan data. The period is also extended considerably when data is output to the PC, since this is affected by the Baud rate used.

Experiments suggest that a full scan period of about 10 seconds minimum is probably realistic for most applications. Whilst this period can be shortened, you may be in danger of losing scan data, and perhaps erratic stepping of the motor.

Transducer Mounting

Having proved the motor's action, the ultrasonic transducer can be mounted on its shaft, with Blu-Tack (etc) or even holt-melt glue, if it has a flat plate such as a cog on its shaft, or via a plate of your own making secured to the shaft in some way. (You are strongly recommended to choose a motor that already has its own shaft attachment.)

The connecting wires to the transducer need to be chosen carefully. Because the transducer rotates through 360°, the wires need to be flexible and long enough to allow them to also rotate smoothly, without getting twisted or imposing strain on the motor.

Originally, the author simply used a length of two-way ribbon cable, together with a hooked metal support made from a coathanger and secured to the baseboard on which the motor was mounted. This proved to be highly unsatisfactory, causing more problems than it solved! Next a length of mono screened audio cable was used, still with the support. This got fouled-up too. However, it was found that this cable was capable of supporting itself in a vertical U-shape without the support, and functioned perfectly (see photograph on the previous page).

PC Interfacing

The PC interface software was written under Visual Basic 6 (VB6), and you need VB6 on your PC in order to make full use of it. There is, though, a standalone version

of the software (**Radar.exe**) which you can run without VB6 being installed.

Whether or not VB6 is installed, copy *all* of the Radar files (except the PIC files if you prefer) into a new folder called **C:\Radar**, or any name of your choosing, on Drive C (the usual hard drive letter).

If you do *not* have VB6, and you wish to run **Radar.exe**, you also need three other files, **comdlg32.ocx**, **Mscmmct.ocx** and **Msvbm60.dll**, held on our 3.5-inch disk named Interface Disk 1, and in the *Interface* folder on our Downloads page (they are also included with the *TK3* software, in Disk 2). These files must be copied into the same folder as the other Radar files.

These three files are not supplied with the Radar software as they are common to several *EPE* VB6 projects and amount to about 1MB of data.

Additionally, the VB6 source code makes use of Joe Farr's *Serial Interface for PICs* (Oct '03) software. In order to access and modify for your own purposes the Radar VB6 source code files, you need to have Joe's software installed on your PC as well (see his published text). This is also available via our Downloads page.

Without Joe's software installed, if you try to access the Radar source code, it will crash.

Note that you should not attempt to "install" the Radar VB6 files via Explorer or other similar PC facility. Use Windows' own normal Copy facility.

Guided Tour

To run **Radar.exe**, double-click on its file icon in the Radar folder. On first running, the program creates a couple of its own run-time files which hold various facts about what settings it should use on your PC, initially setting them to default values. More on this in a moment.

Radar's main screen then appears, as shown earlier, but without data yet of course. Dominating it are several concentric circles, the spacing between each representing a scan period of about 2ms. It is on this screen that blocks of radar scan data are plotted radially in relation to the stepper motor's scan angle.

At the top of the boxed panel at the left are two "radio" buttons relating to the PC COM port through which you wish to

import data from the PIC unit. Click the setting you wish to use, COM 1 or COM 2. The initial default is COM 1. This software cannot be run via a USB port.

Having selected the COM port, this setting is stored to the **RadarSettings.txt** file in your Radar folder and is recalled next time the program is run. It may be changed again via the radio buttons should you wish.

Below the COM port buttons are two more buttons relating to the Baud rate at which you wish to import serial data. The selected value is also stored to the Settings file for future recall. Leave the setting at 9600 Baud for now.



The next two buttons select the number of steps per revolution for your motor. This selection is also stored to disk for future recall. The default is 48 steps. If your motor has a different number of steps, you may amend the VB6 code to suit, in which case you must also amend the PIC program to the same value (the commands are notated in the ASM file).

Below these buttons, two others select which screen display mode you want to use. Circular mode is that currently shown. Graph mode displays the scan values as oscilloscope-type waveforms horizontally across the allocated screen area. The display setting is not stored to disk and always defaults to Circular.

The large circle below the display mode buttons is a graphical representation of the total scan arc covered by the motor, initially relating to 360°. The arc can be changed using the small slider (Slider2) below the circle, from 360° down to 0° (static motor, angle unchanging). Use the slider now to see the effect on the symbol. The value is not stored to disk and always defaults to 360° when the program is loaded.

At the far right of the screen are seven coloured buttons. These select the colour in which you want the scan data to be plotted on screen. Click them now and observe the effect on the arc symbol at the left. Again the setting is not stored to disk, the default being red. You can, of course, amend the default colour from within the VB6 source code. For now, return Slider2 to 360°.

The large slider (Slider1) at the far left deducts the selected value from the incoming scan data and it is the resulting value that is plotted to screen. It is only of use when data is actually being input, and its default value is always 0.

Starting Scan Input

To start inputting scan data from the PIC unit, first plug the unit into the PC at the required COM port socket. Ultimately, the connecting cable between the PC and PIC unit should be assembled from the thinnest three-core cable that you can find, at a length suited to how far you expect the robot to move away from the PC. You may also prefer to provide overhead supports on which the cable can be held above the robot's track area, in order to prevent cable/robot entanglement!

Connect power to the unit. It will start to run in "free" mode (as described previously), but not yet output data to the PC. Now click on the Input Scan button.

This triggers several actions. First the button caption changes to Stop, and the unselected radio buttons are "greyed". Slider2 and its arc symbol are hidden, and so too are the colour selection buttons, since none of these can be used during scan input. Any previous scan data is cleared.

Next the PIC is told the current value of Slider2, and thus the number of steps required for the scan arc coverage required, 360° full arc scan at present. The motor's maximum step value is then sent (48 at this time). Finally, the Baud rate at which the PC expects to receive data is sent. Handshakes are exchanged between sending each value.

On receipt of the values, the PIC adjusts its settings to suit, also outputting the values to its l.c.d. screen, Baud and step values on line 2, arc value on line 1. The PIC then starts outputting scan data to the PC for plotting on screen.

Note that the PIC's default Baud rate is always 9600 and the PC first communicates with the PIC at this rate when the Input Scan button is clicked. Following receipt of the Baud rate value, the PIC and PC then communicate at the selected rate.

Each 96-byte block of scan data is sent to the PC as a single sequence, prefixed by the value 255 (H'FF'), and then the current scan angle. The PC acknowledges receipt of the complete sequence. The 255 value is unique and the PC uses it as a sync marker. All scan values are limited to a maximum of 254 to avoid sync conflict. On receipt of each 98-byte (96 + 2) data block, the PC looks for the sync marker and then plots the values in timed (consecutive) order in relation to the sync marker.

Circular Plot

The values are plotted outwards from the centre of the display circles to the outer circumference, at the radial angle embedded in that data block. Any previous data at that angle is first cleared. Only those values above zero are plotted, as colour-filled squares whose dimensions are set by the sample value, with a maximum value limit of 15.

In early tests no limit was applied and the squares plotted directly at the received value. It was found, though, that interpreting the screen display became difficult with such a range of square sizes, many of which bled into squares from adjacent scan angles.

Slider1 can be used to reduce the scan values in order to improve the display "definition" if preferred. The subtraction range, as shown, is 0 to 50.

To stop scan data input, click the Stop button. The PIC is not advised of this cessation (although it could be written into the code if you wish). Instead its software has a time-out routine, set at about two seconds or so.


Following each data block being sent, if the PC's acknowledgment signal (the letter "G") is not received within the time-out period, the PIC reverts to "free running" in which it no longer outputs data to the PC.

Step Rates

In "free-run" mode, the PIC's angle-stepping rate is slightly increased compared to its send-PC rate. Note that the "free" rate has been deliberately slowed below what is actually possible by the inclusion of a delay loop in this mode. It was found that at the fastest possible angle step rate, the motor sometimes failed to correctly follow the stepping pattern, resulting in changes to the positions at which it changed direction.

In relation to this, it was assumed that stepper motors must require a minimum pulse length in order to step correctly. Surprising, datasheets for several stepper motor types did not give this information.

Having reverted to "free" mode, the PIC's Baud rate is reset to 9600 Baud, in readiness for the next clicking of the PC's Input Scan button. It should be noted that having stopped the PC's input mode, time must be allowed for the PIC's time-out to be triggered before re-clicking the button. Failure to do so will result in communication failure between PC and PIC. Observing the motor will indicate whether it is in "free" mode or still waiting for a PC handshake (its stepping rate being seen to be slightly faster than in send-PC mode).

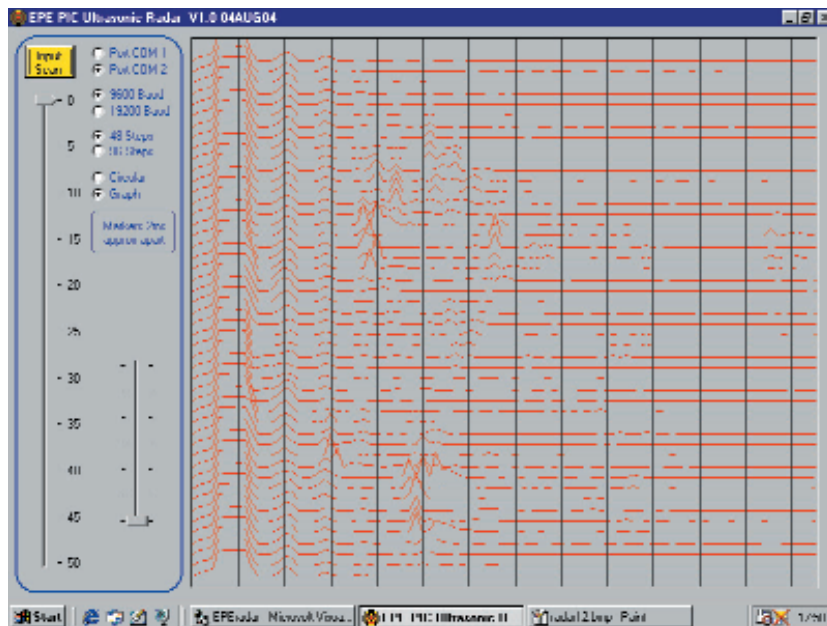

The PC display screen in a typical example of graph mode

The VB6 Radar software also has a time-out embedded into it. If a complete block of data is not received within two seconds of it being expected, an advisory message is displayed on screen and Input mode is exited, the Stop button reverting to show Input Scan.

Having ceased data input, the Radar screen re-enables all the functions hidden during scan mode, and any new settings can be selected, including Graph Mode instead of Circular. Click this option and the main screen area will change format. The concentric circles now disappear, the display width lengthens to the right, and vertical timing lines are added, also spaced at about 2ms intervals (only an approximate value), see above screen dump.

Clicking the Input Scan button now causes data to be plotted in horizontal lines with data values shown as waveforms representing signal amplitude. Their basic vertical positions are in relation to the scan angle, 0° at the top, 360° at the bottom. Having clicked Stop, you may then reselect Circular mode, or stay in Graph mode.

Different Scan Arcs

Screen displays in both Circular and Graph modes are always in relation to the scan arc selected by Slider2, the scan direction changing when the limits set by the slider have been reached. However, a common situation can arise in this respect. If the motor is already at an angle which is outside the newly set scan arc, it will continue to step from its present position, outputting data for those angles until one or other preset arc extreme has been reached. It will then restrict its scanning to within the required limits. The screen, though will continue to show the previously plotted data from outside the limits.

To eliminate this extra data, once the motor is scanning through the required arc, stop the PC's data input, wait for the PIC program to enter "free" mode, then restart PC data input. The display will now show only data for the required arc.

Motor Start-Up Angle


The motor used in the prototype does not have any means of knowing in which angle it is pointing when power is first applied to it. This probably applies to many other stepper motor types as well. Consequently, before applying power to the Radar unit, the motor must always be manually set so that the ultrasonic transducer points in the mid-arc direction ("forwards").

Mechanically-minded readers will recognise that this situation can be avoided by fitting the motor with a lever which activates microswitches at the extreme ends of the motor's rotation. The software could then be provided with a "start-up" routine which causes the motor to rotate until both switches have been activated, and then the motor stepped to its central position. No advice is offered on this modification, though.

Roboscanetics!

While preparing Owen Bishop's *Smart Kart* for publication, the author was struck by how much fun it was likely to create. He feels the same about this Radar scanning module. It has been interesting to create and fun to play with in the workshop.

As said earlier, it is just a basic framework which you can modify for your own purposes. There seem to be lots of opportunities, though, for you to modify it to become part of your own mobile robot, to not only give you pleasure, but a lot more experience at programming robot devices. And just think how much you will entertain and impress those who get to watch your robot being put through its paces! □

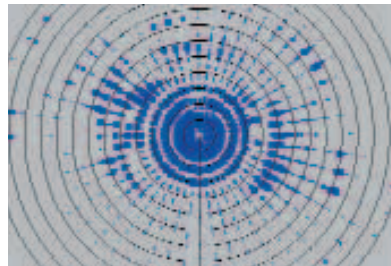

Digital TV Switchover

After studying Parliament's discussions through *Hansard*, Barry Fox updates us on the plans to switch off analogue TV in the UK – and finds there are problems as D-Day looms!

MPs are calling on the UK government to set a firm date for what has now become known as D-Day – the day when the UK starts switching off all analogue TV transmitters and turning them over to digital. Ofcom has called for a start in 2008, and finish by 2012. Electronics and IT trade body Intellect is urging not just a firm date for D-Day but a commitment to change the transmission system, to make room for more programmes and for HDTV.

The downside, Intellect admits, is that many tens of thousands of digital TVs bought by early adopters will "go dark". "Responsibility is shared between the DCMS, DTI and Ofcom, and between Tessa Jowell, Lord McIntosh, Richard Caborn and others. We want clear leadership and ownership", says Laurence Harrison, Intellect's Director of Consumer Electronics. "We have been saying it for years", says Peter Hamblin, Deputy Managing Director, Panasonic and Chairman of Intellect's Digital Television Manufacturer's Forum. "The government must own and lead this project".

"It is the start date for the switchover that matters, not the end date," says Harrison. "There will not be an announcement before the election. But we want it as soon as possible after that. That means the summer. We have to get people to think digital and stem analogue set sales".

In 2004 3.5m Freeview Set Top Boxes (STBs) were sold; 5.5m analogue TV sets; and only 500,000 Integrated Digital TVs (IDTVs). Intellect recently attacked the BBC for promoting STBs over IDTVs. Intellect also wants the government to set a transmission standard based on 64 QAM, as used by ON Digital and ITV Digital and still used by the commercial stations, to get 24Mbps and six TV channels per multiplex – not the 16 QAM system now used by the BBC for Freeview, which gets only 18Mbps per multiplex but makes weak signals more robust.

Rushed Launch

Intellect additionally wants the UK to switch from 2k COFDM to 8k, because this – along with the higher transmission powers that will be possible after analogue services have finished – will give 64 QAM the robustness of 16 QAM. The UK adopted 2k because dual mode 2/8k chips were not available in time for the rushed DTTV launch.

"Digital transmitters currently work at -20dB, one hundredth the strength of analogue" says George Fullam of the Consumer Electronics Technical Committee PH Fullam. "When there is no analogue the digital signals can be at -7dB, one tenth the analogue powers".

Intellect accepts that the change from 2k to 8k will mean that some STBs and IDTVs no longer work. High value IDTVs bought by early adopters are the main problem. "Out of around 75,000 legacy IDTVs, around 50,000 will still be in use at switchover to 8k. We are calling for government support to help the owners who will blame the manufacturers. There should be some kind of compensation. It could be financial or it could be a new set-top box. It must be fair for all parties".

Intellect's announcement followed a few days after Lib Dem MP Steve Webb won time in Parliament for MPs to debate the Ofcom plan for "Driving Digital Switchover". Tessa Jowell and Lord McIntosh were not there so Richard Caborn, Minister for Sport and Tourism, had to try and defend attacks from the opposition's shadow ministers, Tory John Whittingdale and Lib Dem Don Foster. Added Webb: "I wonder how many people are buying cheap sets from the bottom end of the market, which will become obsolete unless they pay almost as much as they did for the telly to get them sorted out".

Sticker System

"The Government now have a sticker system to give people a bit of a clue when they buy a telly, but I still think that awareness out there is very low." John Whittingdale added: "It is possible to get Freesat – although one has to look rather hard to discover how to go about getting it." Said Webb: "Nearly one in three registered social landlords do not allow their tenants to install satellites."

Brian White, Labour MP for Milton Keynes, chipped in: "Consider the history of ONdigital, and the collapse of ITV's digital service. One of the assumptions that was made was that the aerial problem was manageable. Many aerials in the country need a massive upgrade. Why did colour TV come in so quickly and so well? It was because of Radio Rentals. People rented their TV and could get the upgrades without worrying about having to spend money on the TV. It was part of the rental contract. Where are the rentals for broadband and digital TV?"

"It is a market that an entrepreneur could step into and fill. We need to recognise why things worked well in the past, because we could apply that to the future." Don Foster shares Intellect's concern: "One of my real concerns is a lack of leadership from the Government on the issue." Lib Dem Michael Moore warned: "The days are long gone when households might have only the one piece of equipment to be affected by such a change. It is not simply about changing the black and white telly in the corner over to colour, or getting one

with teletext; in many households every room has a television, with VCRs or DVD players attached. Even now pieces of equipment are being sold that are not digital-compatible."

Failure

Said John Whittingdale: "The Government have completely failed to persuade those who are aware of their policy that it is a desirable policy. A survey for the Department of Trade and Industry of 4,000 viewers found that more than 70% are angry about switch-off and suspicious of the Government's motives. More than three million householders said that they would refuse to buy digital equipment and half of them said that they would maintain their defiance even if they had to give up TV completely. My main household television set is digital, but I have three more, which are analogue. I do not think that I am all that unusual in that."

Richard Caborn then made a significant admission: "We are fully aware that some people will need much more information. They may need help to understand what they have to do to install their boxes and check their aerials, and help to understand how to use their new equipment, and we acknowledge that a few might also need financial assistance. Only 73% of UK households can access digital terrestrial television services. That figure cannot be increased before switchover."

Crunch Point

Don Foster revealed: "I, and I suspect others, have received a letter from the chief executive of Ofcom who says quite categorically: 'We will, by late spring/early summer be at the point where operational decisions and political decisions must come together'. In short, a decision crunch point is approaching when a political decision – either to go ahead with switchover or to postpone it indefinitely – needs to be taken."

"If I were working in a TV shop", said Alan Reid, "I would expect a flood of calls from those who missed all the adverts and from those who find that for some reason the untested equipment does not work."

"There will be a third group", predicted Brian White, "the technophobes who do not have a seven-year-old kid to do it for them." Michael Moore agreed: "For many who do not have a seven-year-old child switchover will be a big burden."

Don Foster also worried about "technophobes without seven-year-old children" adding hopefully that if any other MP "does not put himself in that category, if he wants to pop around to my flat afterwards to tune my video in, I would be grateful; I have been trying to get it right for two months." □

Programming PIC 18F Interrupts

Malcolm Wiles

Clarifying the datasheet for the PIC18F family

IN the author's previous article on the Microchip 18F series (*PIC18F Microcontroller Family*, April '05), the temptation to dwell on the subject of interrupts was mostly resisted. But almost at the same time as this article appeared, an email arrived from no less an authority than our illustrious technical editor, who had been having a few problems trying to use 18F interrupts on a project he was working on at the time.

We reasoned that if he was finding the datasheets hard to understand, it's possible that other readers might be as well. So at John's request, this article aims to shed a bit of light on PIC 18F interrupts. Familiarity with the author's previous articles on 16F interrupts (*Programming PIC Interrupts*, April, May '02) is assumed.

There are four example experiments, each with its own test program, **tp1.asm** to **tp4.asm**. These are available as stated later, to accompany this article. Space does not permit them to be printed here, so readers should download and read through them, even if it is not intended actually to set up and run the experiments.

What's Changed?

Perhaps the first reassuring thing to know about interrupts on the 18F is that by default they are hardly any different from 16F interrupts. The interrupt vector is at location h'0008' byte addressed, which is the same as location h'0004' on the word addressed 16F series. They are caused by the same events as on a 16F (Timer wrap, change on RB7 to RB4, peripheral events and so forth). They are enabled by setting interrupt enable bits in familiar registers, and cause interrupt flag bits to be set. They need to be processed in your code by an interrupt service routine (ISR).

In fact, the only slight difference is associated with context saving. Because the bank select bits are no longer in the STATUS register but in the BSR on 18Fs, it is necessary to save BSR as well as STATUS and W on entry to an ISR. The new **movff** instruction, which does not affect STATUS, helps make the job straightforward, as shown in Listing 1.

Only one other thing is worth noting, which is that the save locations for the context registers should always be located in

LISTING 1

```
; data definitions in bank 0

SAVE_S    equ    0
SAVE_W    equ    1
SAVE_B    equ    2
...

; other definitions here

org        0
bra        START
org        8
bra        isr
org        20

START:
...

isr:

    movwf   SAVE_W,A ; save
                        context
    movff   STATUS,SAVE_S
    movff   BSR,SAVE_B

; body of isr here

    movff   SAVE_B,BSR; reload
                        context
    movff   SAVE_S,STATUS
    movf    SAVE_W,W,A
    retfie
```

the Access bank. This is because on entry to the ISR, the BSR setting is unknown, so banked access to data memory must not be used in the ISR until the required setting has been loaded into BSR. Similarly, once BSR has been reset by the ISR "restore context" code on exit, it cannot be used to access data memory in any remaining instructions in the ISR.

Experiment 1

Readers who want to follow along experimentally, and are able to program 18F PICs (e.g. with *TK3* version 3.00 or later), can set up the simple circuit shown in Fig 1. This is best done on a prototyping board like the *TK3* board, but if you don't have such a thing then solderless breadboard should do fine.

The circuit is shown using a PIC18F242, but can be straightforwardly adapted for any PIC18Fxx2 series processor. Load program **tp1.hex** into the PIC. This is a simple flash i.e.d. program, which uses the TMR0 interrupt to time the flash frequency. It uses an ISR with the context saving and restoring code as in Listing 1.

The main loop of **tp1.asm** contains a test that the context saving is working correctly. If it is not, sooner or later an interrupt will occur at the point noted in the code, W will be corrupted by the ISR, and the test that **temp1** is equal to **temp2** will fail. The main loop will then disable interrupts so that the led will stop flashing.

If you want to see what happens if W is not preserved by the ISR, comment out the **movf SAVE_W,W,A** instruction before the **retfie**, reassemble the program, and reprogram the PIC.

Fast Context Save and Restore

Although interrupts can be used in just the same way as on 16Fs, the 18F series provides a number of enhancements, and life would be boring if we never tried anything new. So the first of the enhancements we'll look at is fast context save and restore.

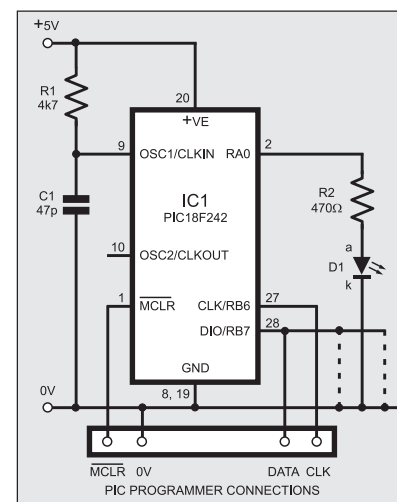


Fig. 1. Demo Test Circuit

Whenever an 18F processor vectors to an interrupt, it automatically saves W, STATUS, and BSR for you in a private memory area of its own, that you can't access directly. It always does this whether you like it or not. You can't turn this feature off, or affect it in any way, but there's no overhead or time penalty associated with this save, so it's nothing to worry about.

But what you can do is choose whether, on exit from the your ISR, the processor will automatically reload W, STATUS, and BSR from its private memory area or not. If you don't want it to, then you exit from the ISR just as you did on 16Fs with a **RETFIE** instruction, just as we did in Listing 1.

But if you want to use the hardware's context restore, you simply modify the **RETFIE** instruction as follows:

```
retfie    FAST
```

Now W, STATUS, and BSR are automatically reset to the values they had at the time the ISR was entered. You don't need to save and restore these registers in software. So ISR path lengths can be shorter, and hence interrupt response times can be a little quicker. The maximum interrupt rate that can be handled (since a good ISR will typically only be a few instructions long, often of the same order of length as the context saving and restoring overhead) can often be doubled, or nearly so. The **RETFIE FAST** instruction executes in the same time as a plain **RETFIE**, so there's no hidden overhead here either.

Almost all good news then. But as we'll see in a bit, you can't always use fast context save and restore, so don't forget how to save and restore context by software, as discussed in the previous section, just yet.

Experiment 2

Load program **tp2.hex** into your PIC and run it. It is the same as **tp1.asm**, except that its ISR uses fast context save and restore. Observe that the l.e.d. continues to flash so the program is interrupt safe, even though no context save and restore is done by the software.

Fast Call and Return

This section is a short digression from the main topic of interrupts, but closely related to fast context save and restore, so we'll briefly mention it here. It is also possible to have the hardware save W, STATUS, and BSR for you when you make a subroutine call, and restore them when you **RETURN** from the subroutine. But in this case you have to explicitly tell the hardware to do it; by default it will not do either the save or the restore. The assembler syntax is similar, as in Listing 2.

Listing 2

```
call    SUB1, FAST
...
SUB1:
...
return  FAST
```

You cannot safely do fast call and return if any interrupts are enabled, because if an interrupt occurs during execution of the subroutine it will overwrite the hardware's save area, whether or not fast context save and restore is being used. The **RETURN FAST** would then reload the values stored when the most recent interrupt was taken, not when the subroutine was called. The result would be a program that behaved unpredictably giving different and non-reproducible errors, which could include program crashes.

This is not generally such a useful feature, because usually you want to return results from subroutines, and W and/or the STATUS flags are often convenient ways to do that. But it may occasionally have uses.

A Gotcher - MOVFF

The **movff** instruction is a bit odd. Although written as one assembler instruction, it is double length and takes two instruction cycles to execute. It sometimes behaves as if it were two instructions, and it is not completely "atomic" with respect to interrupts. Although safe to use to save and restore context in the ISR as illustrated above, it is not safe to use the **movff** instruction to access any of the interrupt related SFRs shown in Table 1 while interrupts are enabled.

Table 1: Interrupt Enabled SFRs

```
RCON
INTCON
INTCON2
INTCON3
PIR1
PIR2
PIE1
PIE2
IPR1
IPR2
```

Also note that it is not safe to use **movff** to read PORTB in order to clear the mismatch condition before clearing a RBIF interrupt. If a soft copy is required, PORTB must be loaded and saved via W, as on the 16Fs:

```
movf    PORTB,W,A
        ;NOT movff PORTB, SOFTB
movwf   SOFTB,A
```

Priority Interrupts

The major enhancement to interrupts on the 18F series is its priority interrupt scheme. Apart from the INT0 interrupt, all interrupts on the 18F series can be programmed to be either high or low priority. INT0 is always a high priority interrupt. (In the *PIC18F Microcontroller Family* article, TMRO was erroneously described as the interrupt source which is always high priority.)

High priority interrupts vector through location h'0008', but low priority interrupts vector through location h'0018'. Although it is possible to have both interrupt vector locations point to the same ISR, it is usual to have two separate ISRs in a program that uses priority interrupts, one for high priority interrupts and one for low priority interrupts. This is because each separate ISR only needs to process its relevant interrupts, so each one can be simpler and faster than a combined one would be.

High priority interrupts pre-empt the processing of low priority interrupts. A low priority ISR will be interrupted by the occurrence of a high priority interrupt event. So some rethinking of how to write low priority ISRs is necessary; we'll return to this point a bit later.

Possible Uses

Why would you want to use priority interrupts? Perhaps the most obvious reason is to get the fastest possible response to emergency events. If your overheating sensor triggers, or the microswitch in the endstop operates indicating that something has hit the buffers, you want to get the power disconnected as soon as possible. A high priority ISR dedicated to handling such emergencies would provide a good way to do that.

More generally, PICs often have to perform several functions simultaneously, and these are often not of equal importance. As an example, one of the author's PIC projects is a fridge controller, designed and implemented in some haste when the original equipment thermostat in his fridge failed. A block diagram of this circuit is shown in Fig 2.

The same set of I/O lines drives both led displays, and the standard multiplexing technique in which the l.e.d.s are driven alternately and switched rapidly is used. PIC timer interrupts are used to control the

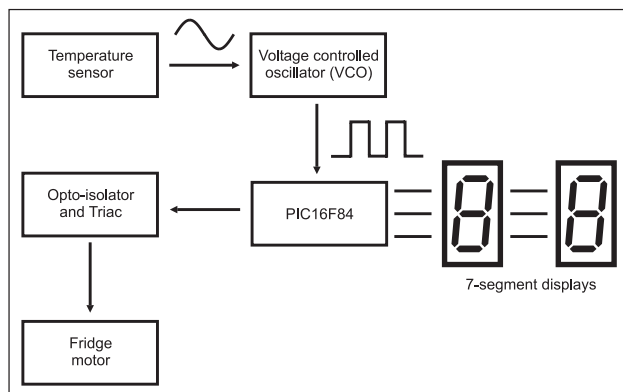


Fig.2. Block diagram for the author's fridge control, which is suited to upgrading using an 18F and its interrupts

multiplex display switching, and the VCO pulses generate interrupts which are counted to calculate the temperature. The software's main loop worries about keeping the fridge at the right temperature by switching the motor on and off as necessary.

The VCO output frequency can exceed 100kHz, and without going into all the design calculations it turns out that it is

not possible to count the VCO pulses and multiplex the I.e.d. temperature display at the same time, when both have to be given equal weight in the interrupt processing. While switching the display, VCO pulses can be missed. So every 30 seconds, while the PIC rechecks the temperature, the display has to be blanked for 100ms or so.

While this is not a severe problem in this circuit, it would be rather neater if this blinking of the display were not necessary. If a PIC with priority interrupts had been available at the time the circuit was built (and the author's wife had not been breathing down his neck demanding a quick repair!), the VCO input could have been made high priority, ensuring the necessary counting accuracy. The I.e.d. multiplexing could have been made low priority and simply allowed to take whatever PIC processing power remained. This might well have been sufficient to maintain a reasonable I.e.d. display.

Programming Priority Interrupts

In order to use priority interrupts, the programmer has to do two additional things:

- assign a priority to each interrupt used
- enable the priority interrupt system

As well as the interrupt flag bit and the interrupt enable bit, each interrupt source on the 18F, except for the INT0 interrupt, has an interrupt priority bit associated with it. By default at power on all interrupt priority bits are zero, which is interpreted as high priority. By setting the interrupt priority bit, which should be done before the interrupt is enabled, the corresponding interrupt is made low priority. This means that when the interrupt event occurs, the processor will jump to location h'0018', not h'0008'.

The priority interrupt system is enabled by setting the IPEN bit in the RCON register. If this bit is clear, the settings of the priority bits are ignored and all enabled interrupts behave as high priority interrupts. It doesn't matter in which order your program sets IPEN and the priority bits.

When IPEN is set, the GIE bit still does the same job of enabling and disabling all interrupts. GIE is called GIEH when IPEN is set, but is physically the same bit. Similarly, PEIE is called GIEL when IPEN is set, but is physically the same bit.

Low priority interrupts have to be additionally enabled using the GIEL bit, and can be separately disabled as a group by clearing the GIEL bit. So it doesn't really make much sense to have just low priority interrupts in a program, because to make them work both GIEH and GIEL have to be

Table 3. Non-peripheral Interrupts

TMR0IF
RBIF
INT0IF
INT1IF
INT2IF

set. If you only want one level of interrupts, disable the priority interrupt system and just have high priority interrupts.

The interrupt sources shown in Table 3 are non-peripheral interrupts. All other interrupts are peripheral interrupts – the exact list of these varies slightly with the device type. In high priority mode (IPEN=0) any non-peripheral interrupt will be enabled if its particular source enable bit (XIE) is set and GIE is set. The peripheral interrupts additionally require PEIE to be set. This is the same as on 16Fs.

Be aware that XIE is not a real bit but here stands for any interrupt enable bit. These bit identifiers always end in IE, for example EEIE is data EEPROM/FLASH write complete interrupt enable, and RCIE is USART receive interrupt enable. Similarly, bit identifiers ending in IF and IP signify interrupt flag and interrupt priority, respectively.

If priority interrupts are enabled (IPEN=1), then there is no distinction made between peripheral and non-peripheral interrupts. A low priority interrupt will be enabled if XIE, GIEL, and GIEH are all set. A high priority interrupt will be enabled if XIE and GIEH are set.

If that's all a bit confusing, maybe Table 4 will help.

The rest of this article assumes that if low priority interrupts are in use, then high priority interrupts are being used also.

Context Saving in Low Priority ISRs

We previously noted that low priority ISRs can be pre-empted by high priority ISRs. This means that low priority ISRs cannot safely use the fast context save and restore mechanism, because there is only one hardware fast save area. If a high priority interrupt event occurs during a low priority ISR, the fast save area will be overwritten. As a general rule, low priority ISRs must save and restore context in software as described earlier.

Experiment 3

Example program **tp3.asm** flashes two I.e.d.s. One I.e.d. on RA0 is driven using TMR0 interrupts at high priority, the other on RA1 by RBIF interrupts (from RB5) which are configured as low priority.

Make a small modification to the test circuit of Fig.1 by adding a second I.e.d.

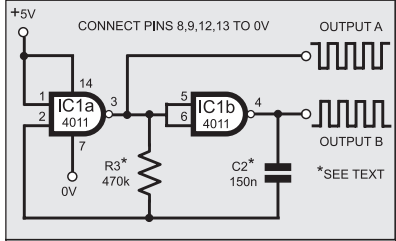


Fig.3. Square Wave Generator

and suitable current limiting resistor connected between RA1 and ground.

If you have a signal generator, set it up to generate 5V square waves at less than 30Hz (or you won't be able to see the I.e.d. flashing) and connect its output to RB5. If you don't have a signal generator, then you can easily make some square waves using the circuit shown in Fig. 3 (there are many other possibilities – see for example *Logic Gate Inverter Oscillators*, Sep/Oct 2002). In this circuit the frequency of the square waves is set by R3 and C2, which should be a non-polarised type. Choose R3 = 470kΩ and C2 = 150nF initially to get square waves at about 10Hz.

Load **tp3.hex** into the PIC and run it. Both I.e.d.s. should flash. Wind up the output frequency of your signal generator, and the second I.e.d. will just appear to be on dimly as it flashes too fast for your eye to perceive, and notice that the flash rate of the first I.e.d., which is driven by high priority interrupts, is unaffected.

If you are using a circuit such as in Fig.3 to generate your square waves, reduce the values of the resistor and capacitor to get higher frequencies.

If you are using PIC clock RC values as specified in Fig.1, then your PIC clock should be running at around 2.5MHz. So the PIC instruction execution rate will be (2.5 × 10⁶)/4 or about 625,000 instructions/sec. **tp3.hex** takes 16 instructions, of which five are double length so really equivalent to 21 instructions, to process a low priority interrupt. So if you set your signal generator to more than about 625,000/21 = 29.8kHz, then you will be saturating the PIC with low priority interrupts, in other words generating them faster than the low priority ISR can process them. Try this, and observe that even under these extreme conditions, the high priority I.e.d. flash rate is unaffected.

Writing Low Priority ISRs

Low priority ISRs can be quite tricky to write. As they are interruptible, they might have critical sections in them that would not be safe if interrupted (see *Programming PIC Interrupts* for more on critical sections).

Table 4. High And Low Priority Interrupts

IPEN	Priority Interrupt System	INTCON (7)	INTCON (6)	Non-peripheral interrupts enabled by:		Peripheral interrupts enabled by:	
0	Disabled	GIE	PEIE	GIE + XIE		GIE + XIE + PEIE	
1	Enabled	GIEH	GIEL	Low priority	High Priority	Low priority	High priority
				GIEH + GIEL + XIE	GIE + XIE	GIEH + GIEL + XIE	GIEH + XIE

You can disable high priority interrupts round critical sections in a low priority ISR, in order to make the program interrupt safe. But you probably don't really want to, because you made certain interrupts high priority for a reason: in order to guarantee them the fastest possible response time, or to ensure that they get guaranteed access to the processor irrespective of other loads on the PIC. Disabling high priority interrupts will tend rather to defeat their purpose.

Prevention is usually better than cure. The advice given in *Programming PIC Interrupts* that all ISRs should be short, sweet and simple, applies even more strongly in this case. The shorter and simpler a low priority ISR is, the less likely it is that it will contain anything that will cause trouble. In particular a low priority ISR should not make any reference to any variable that is used in a high priority ISR.

Experiment 4

To illustrate the kind of thing that can happen, **tp4** is a program that breaks the above rule. It flashes two l.e.d.s. similarly to **tp3**, but the ISRs now maintain counts of interrupts. There is a count of total high and low priority interrupts (COUNTHL), and separate counts of low priority interrupts (COUNTL) and high priority interrupts (COUNTH). Both ISRs update COUNTHL, and the low priority ISR does it in a way that is not interrupt safe:

```
movf COUNTHL,W,A ; total interrupts
                        count to W
addlw 1             ; bump
movwf COUNTHL,A    ; and save back
                        in memory
```

Suppose COUNTHL contains 23 when a low priority interrupt occurs. The first instruction loads 23 into W. Now suppose that at this point a high priority interrupt occurs. The high priority ISR

will run, it will preserve W containing 23, and it will bump COUNTHL to 24. When the low priority ISR resumes it will add 1 to W, getting 24, and save that in COUNTHL. So COUNTHL will end up containing 24, but it should have been bumped twice by this sequence of events to 25.

The main loop continually checks that COUNTHL is equal to the sum of COUNTH + COUNTL, and halts the program if it finds that it does not. This main loop test needs to be protected from interrupts occurring while it is done, otherwise the counter values being tested could change "under its feet".

Using the same test setup as for **tp3**, set your signal generator to about 500 Hz, load **tp4.hex** into the PIC and run it. If you are using Fig.3 to generate square waves, choose $R3 = 4k7\Omega$ and $C2 = 150nF$.

You should find that the program will run for some random amount of time, which may be in the region of two seconds to two minutes or so, but eventually the l.e.d.s. will stop flashing. Reset the PIC and rerun a few times, and observe that the length of time for which it will run, and the state of the l.e.d.s. when it stops, either both on, both off, or one on, is genuinely random. It depends on what the state of the circuit was in when a high priority interrupt happened to occur at the critical time.

Program **tp4** is obviously somewhat contrived. It can be fixed by replacing the three-instruction sequence to update COUNTHL shown above with a single `INCF COUNTHL,F,A` instruction – try this if you wish. The `incf` is atomic with respect to interrupts and therefore is safe. But hopefully **tp4** illustrates the kind of things that can go wrong if care is not taken, and also the random and unpredictable effects that can occur as a result.

It is, unfortunately, not easy to give a simple definition of what is interrupt

safe and what is not. The rule given above of not accessing any variable used in a high priority ISR from a low priority ISR is unnecessarily conservative, but in practice is not too difficult to follow, and should avoid most of the pitfalls.

Acknowledgement

The author thanks John Waller for helpful comments on the draft of this article, and for testing all the example programs.

Demo Software

The example demo software referred to in this article is available for free download via the Downloads link on our site at www.epemag.co.uk. It is in the Toolkit TK3 folder. □

ANDRÉ LAMOTHE'S

XGAMESTATION

LEARN STEP-BY-STEP HOW TO DESIGN AND BUILD YOUR OWN VIDEO GAME CONSOLE!

Design inspired by the Atan 800/2500, Sinclair ZX Spectrum, Apple II & Commodore 64!





Complete Package eBook Integrated IDE

5X82 CPU 80 MIPS!



FEATURES:

- Great for Hobbyists AND Students!
- Complete Software Development KIT!
- eBook on Designing the XGS Console!
- Parallel 5X-Key Compatible!
- Fully Assembled XGS Micro Edition Unit!
- The Fun Way to Learn Embedded Systems!

PAL & NTSC COMPATIBLE!

WWW.XGAMESTATION.COM

SUPPORT@XGAMESTATION.COM 025 736 2005uk


BUY AND DOWNLOAD YOUR ISSUES FROM THE WEB



\$14.99 (US) – approximately £8.00
per year
www.epemag.com

electronic **surveillance** equipment

- ◆ Professional quality UHF crystal equipment
- ◆ Cost effective VHF FM equipment
- ◆ SENSIBLE prices from a long established, discreet and reputable company
- ◆ Everything designed, developed and manufactured by us in-house and under our control
- ◆ We are dedicated to surveillance products... we make *nothing* else
- ◆ Latest surface mount technology on all modules for maximum performance and micro size
- ◆ We ship worldwide and accept cards, cash and cheques

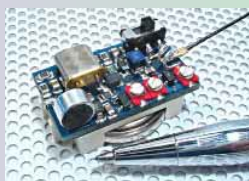


SDX-200S
Ultra-miniature UHF crystal controlled surveillance bug
£69.95 + p&p

A couple of our audio room devices shown complete with battery fitted. The pen tip is shown for size comparison....

Yes they really are this small...

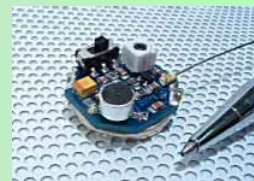Get hold of a copy of our catalogue for full details of these and many other audio surveillance devices. Full of interesting info.



SDV-2
Ultra-miniature VHF surveillance bug
£29.95 + p&p




Phone, fax or e-mail sales@suma-designs.co.uk for our free 2005 illustrated catalogue of audio surveillance equipment, or visit us on-line at www.suma-designs.co.uk

The Workshops, 95 Main Road, Baxtersley, Warwickshire, CV9 2LE UK
Tel/Fax: 01827 714476
www.suma-designs.co.uk

EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS

ELECTRONICS PROJECTS

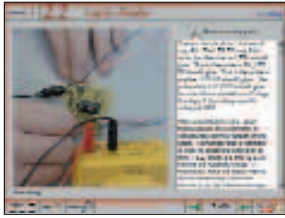


Logic Probe testing

Electronic Projects is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included.

The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.

ELECTRONICS CAD PACK

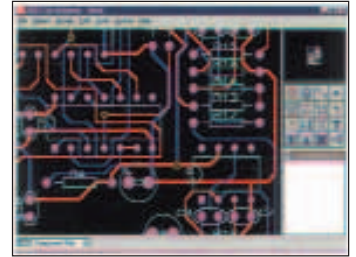

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules. (These are restricted versions of the full Labcenter software.) **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and an autorouter operating on user generated Net Lists.

ELECTRONIC CIRCUITS & COMPONENTS V2.0



Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals**: units & multiples, electricity, electric circuits, alternating circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors, op.amps, logic gates. **Passive Circuits**. **Active Circuits**. *The Parts Gallery* will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

ANALOGUE ELECTRONICS




Complimentary output stage

Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits.

Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections). **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

DIGITAL ELECTRONICS V2.0

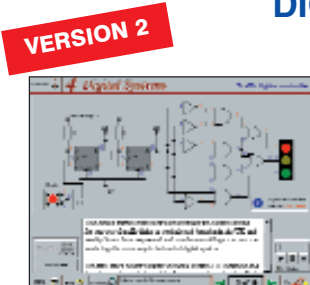


Virtual laboratory – Traffic Lights

Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen.

Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

ANALOGUE FILTERS

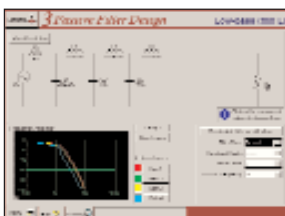

Filter synthesis

Analogue Filters is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev

ROBOTICS & MECHATRONICS



Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations

PRICES

Prices for each of the CD-ROMs above are:

(Order form on third page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student	£45 inc VAT
Institutional (Schools/HE/FE/Industry)	£99 plus VAT
Institutional 10 user (Network Licence)	£249 plus VAT
Site Licence	£499 plus VAT

PICmicro TUTORIALS AND PROGRAMMING


HARDWARE

VERSION 2 PICmicro MCU DEVELOPMENT BOARD

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 13 individual I.e.d.s, quad 7-segment display and alphanumeric I.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- All inputs and outputs available on screw terminal connectors for easy connection

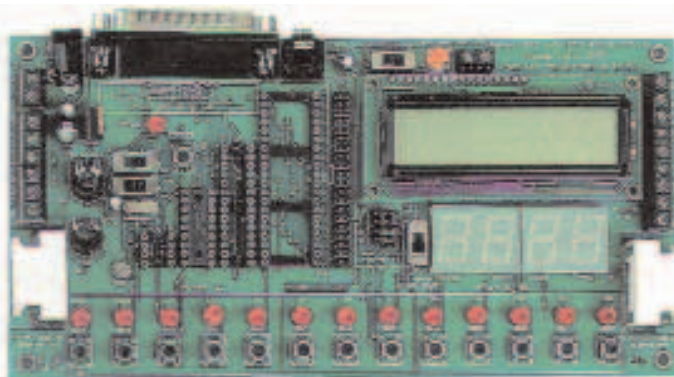

£145 including VAT and postage

12V 500mA plug-top PSU (UK plug) £7

25-way 'D' type connecting cable £5

SOFTWARE

NEW V3

Suitable for use with the Development Board shown above.

ASSEMBLY FOR PICmicro V3 (Formerly PICTutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICTutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes. The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.




Virtual PICmicro

'C' FOR PICmicro VERSION 2

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

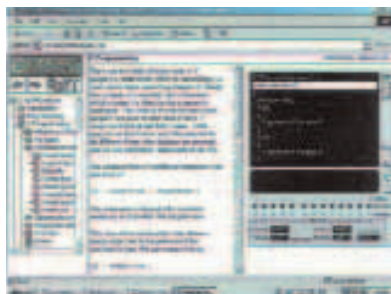- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running Windows 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.

FLOWCODE FOR PICmicro V2

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex robotics and control systems in a matter of minutes.

Flowcode is a powerful language that uses macros to facilitate the control of complex devices like 7-segment displays, motor controllers and I.c.d. displays. The use of macros allows you to control these electronic devices without getting bogged down in understanding the programming involved.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 2 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols (ISO5807)
- Full on-screen simulation allows debugging and speeds up the development process
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- Professional versions include virtual systems (burglar alarm, buggy and maze, plus RS232, IrDa etc.).



Burglar Alarm Simulation

PRICES

Prices for each of the CD-ROMs above are:

(Order form on next page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student
Flowcode V2 Hobbyist/Student
Institutional (Schools/HE/FE/Industry)
Flowcode Professional
Institutional/Professional 10 user (Network Licence)
Site Licence

£45 inc VAT
£57 inc VAT
£99 plus VAT
£99 plus VAT
£300 plus VAT
£599 plus VAT


TEACH-IN 2000 – LEARN ELECTRONICS WITH EPE

EPE's own Teach-In CD-ROM, contains the full 12-part Teach-In series by John Becker in PDF form plus the Teach-In interactive software (Win 95, 98, ME and above) covering all aspects of the series. We have also added Alan Winstanley's highly acclaimed *Basic Soldering Guide* which is fully illustrated and which also includes *Desoldering*. The Teach-In series covers: Colour Codes and Resistors, Capacitors, Potentiometers, Sensor Resistors, Ohm's Law, Diodes and L.E.D.s, Waveforms, Frequency and Time, Logic Gates, Binary and Hex Logic, Op.amps, Comparators, Mixers, Audio and Sensor Amplifiers, Transistors, Transformers and Rectifiers, Voltage Regulation, Integration, Differentiation, 7-segment Displays, L.C.D.s, Digital-to-Analogue. Each part has an associated practical section and the series includes a simple PC interface (Win 95, 98, ME ONLY) so you can use your PC as a basic oscilloscope with the various circuits.

A hands-on approach to electronics with numerous breadboard circuits to try out.


£12.45 including VAT and postage. Requires Adobe Acrobat (available free from the Internet – www.adobe.com/acrobat).

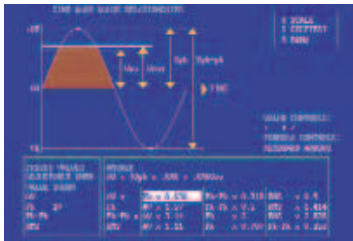FREE WITH EACH TEACH-IN CD-ROM – *Electronics Hobbyist Compendium* 80-page book by Robert Penfold. Covers Tools For The Job; Component Testing; Oscilloscope Basics.



Sine wave relationship values

**FREE BOOK
WITH TEACH-IN
2000 CD-ROM**

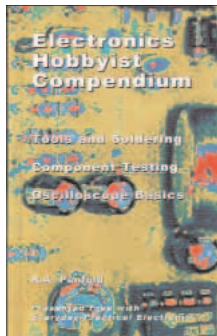

DIGITAL WORKS 3.0



Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability. ● Software for simulating digital logic circuits ● Create your own macros – highly scalable ● Create your own circuits, components, and i.c.s ● Easy-to-use digital interface ● Animation brings circuits to life ● Vast library of logic macros and 74 series i.c.s with data sheets ● Powerful tool for designing and learning. **Hobbyist/Student £45 inc. VAT. Institutional £99 plus VAT. Institutional 10 user £249 plus VAT. Site Licence £599 plus VAT.**

ELECTRONICS IN CONTROL

Two colourful animated courses for students on one CD-ROM. These cover Key Stage 3 and GCSE syllabuses. **Key Stage 3:** A pictorial look at the Electronics section featuring animations and video clips. Provides an ideal introduction or revision guide, including multi-choice questions with feedback. **GCSE:** Aimed at the Electronics in many Design & Technology courses, it covers many sections of GCSE Electronics. Provides an ideal revision guide with Homework Questions on each chapter. Worked answers with an access code are provided on a special website.

Single User £29 inc. VAT. Multiple User £39 plus VAT
Student copies (available only with a multiple user copy) £6 plus VAT
(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

MODULAR CIRCUIT DESIGN

Contains a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects. Version 3 includes data and circuit modules for a range of popular PICs; includes PICAXE circuits, the system which enables a PIC to be programmed without a programmer, and without removing it from the circuit. Shows where to obtain free software downloads to enable BASIC programming. Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinouts, power supplies, decoupling etc.

Single User £19.95 inc. VAT. Multiple User £34 plus VAT
(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

VERSION 3

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.

Please send me: **CD-ROM ORDER FORM**

- ☐ Electronic Projects
- ☐ Electronic Circuits & Components V2.0
- ☐ Analogue Electronics
- ☐ Digital Electronics V2.0
- ☐ Filters
- ☐ Electronics CAD Pack
- ☐ Robotics & Mechatronics
- ☐ Assembly for PICmicro V2
- ☐ 'C' for PICmicro V2
- ☐ Flowcode V2 for PICmicro
- ☐ Digital Works 3.0

- Version required:
- ☐ Hobbyist/Student
 - ☐ Institutional
 - ☐ Institutional/Professional 10 user
 - ☐ Site licence



- ☐ PICmicro Development Board V2 (hardware)
- ☐ Development Board UK plugtop power supply
- ☐ Development Board 25-way connecting lead

- ☐ Teach-In 2000 + FREE BOOK
- ☐ Electronic Components Photos
- ☐ Electronics In Control – Single User
- ☐ Electronics In Control – Multiple User
- ☐ Modular Circuit Design – Single User
- ☐ Modular Circuit Design – Multiple User

Note: The software on each version is the same, only the licence for use varies.

Full name:

Address:

Post code: Tel. No:

Signature:

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

☐ Please charge my Visa/Mastercard/Amex/Diners Club/Switch: £

Valid From: Card expiry date:

Card No: Switch Issue No:

Card Security Code (The last 3 digits on or just under the signature strip)

ORDERING ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version
price includes postage to most
countries in the world
EU residents outside the UK add £5 for
airmail postage per order

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:
Direct Book Service
Wimborne Publishing Ltd
408 Wimborne Road East
Ferndown, Dorset BH22 9ND

To order by phone ring

01202 873872. Fax: 01202 874562

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk

Online shop:

www.epemag.wimborne.co.uk/shopdoor.htm



BS2-IC



BS2-SX



BS2E-IC



BS2P/24



BS2P/40

Parallax BASIC Stamps - still the easy way to get your project up and running!



**Serial Alphanumeric and Graphic Displays,
Mini-Terminals and Bezel kits**

www.milinst.com



Animated Head



3-Axis Machine



Six Legged Walkers



Robotic Arms




Bipeds

Robotic models for both the beginner and the advanced hobbyist



Servo Drivers

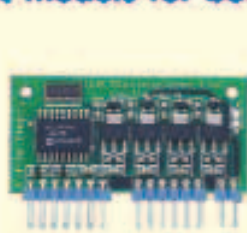

Motor Drivers



On-Screen Displays



DMX Protocol



U/Sound Ranging

Animatronics and Specialist Interface-Control Modules



Quadvox
MP3 & Speech Systems



SensoryInc
Voice Recognition



Parallax
Ubicom Tool Kits



Tech-Tools
PIC & Rom Emulators



BASICMicro
PIC BASIC Compilers

Development Tools

Milford Instruments Limited Tel 01977 683665, Fax 01977 681465, sales@milinst.com

Back to Basics – CMOS Logic Devices

Bart Trepak

Part 3 – Scarecrow and Digital Lock

This short series of articles illustrates how useful circuits can be designed simply using CMOS logic devices as the active components

If you are fed up with cats, foxes and dogs wandering about in your garden breaking all the flowers and fouling your lawn, then this circuit could be the answer. Over the years, many animal deterrent circuits based on transistors, 555 timers and even microcontrollers have been published and they all rely on the fact that most animals can be put to flight by sudden unexplained loud noises.

Although often credited with almost human intelligence by their owners, all pets (as well as their wilder cousins) will undoubtedly have great difficulty in explaining the sounds emitted by this simple circuit so that it should produce the desired effect.

Since we are not trying to put humans to flight, ultrasonic frequencies above the level of human hearing, but perfectly audible to cats, dogs and no doubt foxes, are used instead.

To prevent animals getting used to the sound, the unit is designed to emit a swept frequency sound in short bursts with relatively long intervals between them. This also reduces the average current drawn by the unit, making long term battery operation feasible.

Basic Operation

The circuit diagram for the Scarecrow is shown in Fig.3.1. The heart of the circuit is formed by IC1c, a Schmitt trigger NAND gate, which is configured as a squarewave oscillator. Its frequency is determined by

COMPONENTS

Scarecrow		See SHOP TALK page	IC1	4093 quad 2-input Schmitt trigger NAND gate
Resistors			TR1, TR3	ZVN2110A <i>n</i> -channel MOSFET (2 off)
R1	2M2		TR2, TR4	ZVP2110A <i>p</i> -channel MOSFET
R2	220k		Miscellaneous	
R3	470k			
R4	560k			
R5	390k	WD1	KSN1005 piezo high frequency horn	
All 0.25W 5% carbon film.		Printed circuit board, available from the <i>EPE PCB Service</i> , code 505; 14-pin d.i.l. socket; 9V (PP3 type) battery and connector, connecting wire, solder, etc.		
Capacitors				
C1, C4	47µ radial elect. 16V (2 off)			
C2, C3	100p ceramic disc, 5mm pitch (2off)	Approx. Cost Guidance Only £9 <i>excl batts, hardware & horn</i>		
Semiconductors				
D1	1N4148 signal diode			

the values of resistor R5 and capacitor C3 and lies above 20kHz, which is inaudible to humans but not to dogs and many other animals.

To ensure the maximum possible output power, the output of this oscillator is fed to a simple push-pull amplifier formed by two pairs of MOSFET transistors. One pair, TR1 and TR2, is driven directly by IC1c. The other pair, TR3 and TR4, is

driven by the inverted output of IC1d. Piezo sounder WD1 is thus driven in bridge mode.

This effectively quadruples the output power fed to the sounder, compared to a single-ended output operating from the same supply voltage. The transistors are used because the output current capability of CMOS logic gates is too limited for this application.

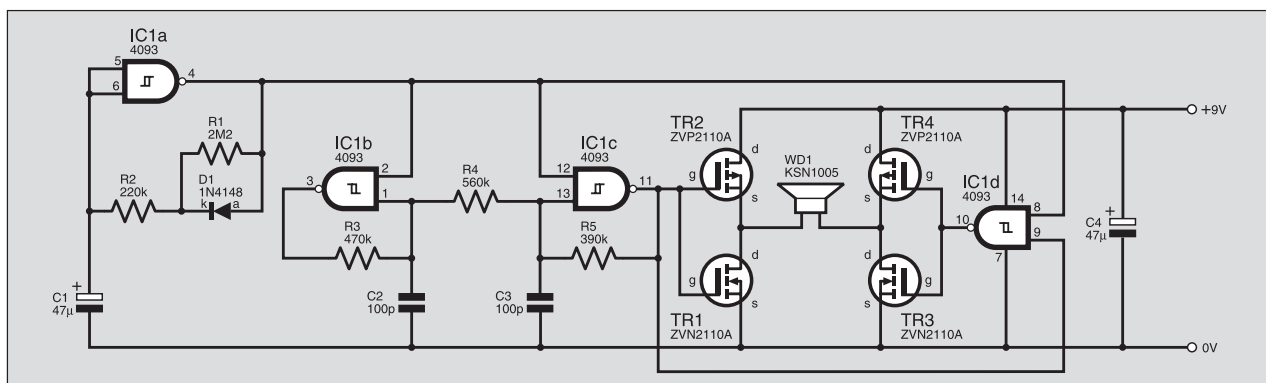


Fig.3.1. Circuit diagram for the Scarecrow Animal Deterrent


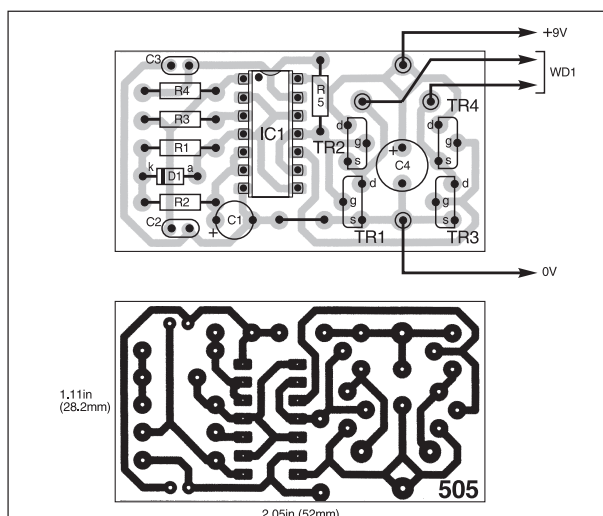


Fig.3.2. Component and track layout details for the Scarecrow printed circuit board

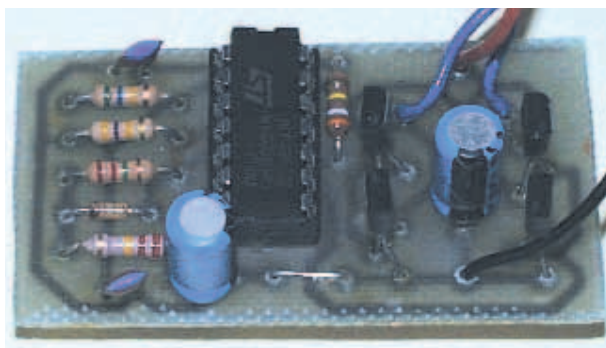

To make the sound less predictable (and hopefully more of an animal deterrent), the basic frequency is swept over a range of frequencies by the inclusion of the oscillator built around IC1b. This oscillates at around 300Hz and the roughly triangular voltage available across capacitor C2 is coupled via R4 to C3, sometimes aiding and sometimes hindering the normal charging and discharging of this latter component via resistor R5.

This results in the frequency of the sound varying between about 21kHz and 25kHz. Varying the output over a range of frequencies also has the advantage of making the sound louder as resonance peaks in the piezo sounder response are reached. These occurrences are more likely with a swept frequency rather than a fixed one, since they will vary from unit to unit.

Finally, the oscillator built around IC1a produces a highly asymmetric waveform due to the action of diode D1. The oscillator's output goes high for only about five out of every 40 seconds. The output of this oscillator is used to switch the circuit on for a short time every 40 seconds, thus contributing to the unpredictability and suddenness of the noise.

The intention is to prevent animals from getting used to the sound and learning to ignore it. It also drastically reduces the current consumption of the circuit, which is consequently switched off for most of this period, thus ensuring that the battery lasts a reasonable time.

Construction

The circuit is built on the printed circuit board using the layout shown in Fig.3.2. This board is available from the *EPE PCB Service*, code 505

Assemble in the preferred order of ascending component size, and use a socket for IC1. Care should be taken to ensure that diode D1, capacitor C1 and IC1 are inserted the right way around. But do not insert IC1 into its socket until final checking has been completed. The transistors should also be identified carefully as two are *n*-channel and two are *p*-channel types and they cannot be interchanged.

Having double-checked that the circuit is correctly assembled, insert IC1. Before handling the i.c., and also the transistors, discharge static electricity from your body by touching an earthed surface. Take care to avoid touching the i.c. pins.

In common with all of the other projects in this series, this circuit can be powered by a 9V PP3 type battery. The current drain is very low (around 500μA average). As the project is likely to be used outdoors, it is recommended that a mains powered d.c. supply should *not* be used with it for safety reasons.

The sounder specified is a special piezo high frequency type. An ordinary audio speaker would not be suitable in this application, not only because of its relatively low impedance, but also its inability to reproduce sounds above 20kHz. The specified sounder, however, does have a paper cone which, although relatively



well protected by the built-on plastic horn, should nevertheless be protected from driving rain or excess levels of moisture. The circuit must be mounted in a weather-proof box.

Testing

Testing the unit can present a bit of a problem, not least because you are unable to hear the results. Furthermore, leaving it out for a few days and observing the comings and goings in your garden over the period is a bit hit and miss, to say the least!

One thing which can be done is to temporarily replace capacitor C3 with a 1nF component. This will reduce the basic frequency down into the audio range so that the results can be heard. As for testing the efficacy of the circuit in its intended application, only the aforementioned method can be used!

CMOS HANDLING

Remember that CMOS circuits require careful handling. The very high input impedance of the gate circuits allows high static voltages to build up which can cause the very thin gate oxide layer to break down, destroying the device. Such voltages are frequently encountered (e.g. simply walking across a carpeted room can generate a voltage in excess of 20kV). Although CMOS circuits normally have protection diodes and resistors internally connected from the inputs to the supply rails to prevent the voltage at the gate from exceeding the supply voltage, you should always discharge static electricity from your body by touching something grounded (earthed) before handling them.

Digital Lock

THE second constructional project for this month's *Back To Basics* is a Digital Lock. Digital locks have many advantages over their conventional mechanical counterparts and perhaps the greatest is that no keys are required. Over the years many circuits for digital locks have been published, usually based on special custom integrated circuits or even microprocessors with many features, such as built-in alarms to detect multiple incorrect entries by someone trying to break the code.

It is possible, though, to construct a simple yet effective combination lock based on a single easily available counter integrated circuit. The design can be further simplified by defining the combination by means of wire links instead of storing it in a memory device. Whilst this makes it more difficult to change the code, it is unlikely that this will be problem.

A coded lock circuit can also find many applications apart from the obvious one of its use in a door. By using the circuit to control a relay, the circuit could be used to switch on the supply to a piece of equipment, for instance, thus preventing its unauthorised use.

Basic Operation

The block diagram for the Digital Lock presented here is shown in Fig.3.3. It is based on a single i.c. forming the counter and decoder blocks. Initially, with the counter reset and decoder output 0 high, AND gate 1 is enabled. Now pressing switch S1 causes the Clock input to go high, so advancing the counter and resulting in decoder output 1 going high.


If any other key, such as S2 or S3, is pressed, nothing happens because decoder outputs 2 and 3 are still low and so AND gates 2 and 3 are disabled. With output 1 high, if S2 is now pressed the counter again advances, enabling AND gate 3, but pressing either key 1 or key 3 has no effect. Only after pressing S1, S2 and S3 in that order does decoder output 3 go high and energise the relay, giving the "lock open" condition.

If any of the other keys such as S4, S5 etc. are pressed at any time, the counter will be reset and again the correct combination of S1, S2 and S3 needs to be entered to open the lock. As well as this, pressing any invalid key holds the counter reset for a short period, so that even a correct entry is ignored. Since no indication of this is given, anyone trying to gain unauthorised entry will not be aware of this. Trying all possible sequences would therefore be unsuccessful, unless this is done very slowly.

The circuit may be configured to open following a valid sequence and remain open until an invalid key is pressed.

The AND gates are a bit more subtle and consist in effect of switch S1 and diode D4, S2 and D5, and S3 and D6. Thus if output Q0 is high and S1 is pressed, the clock input of the counter will go high via D3, advancing the count. If Q0 is low, however, pressing S1 will have no effect because the signal will be shorted to 0V via D4. Resistors R1 to R3 are included to limit the current flow and prevent damage to the i.c. under this condition.

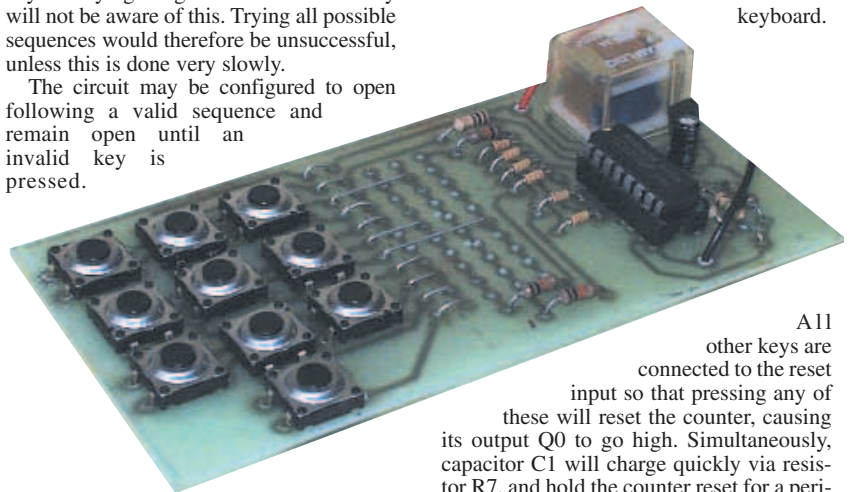In another application, the circuit could be simplified by reversing D4 to D6 and connecting them, via switches S1, S2 and S3 to the clock input. The method used in this circuit, though, was chosen so that all the keys could be connected with a common line, thus reducing the number of connections to the keyboard.



All other keys are connected to the reset input so that pressing any of these will reset the counter, causing its output Q0 to go high. Simultaneously, capacitor C1 will charge quickly via resistor R7, and hold the counter reset for a period determined by the values of C1 and R4. The circuit now ignores all switch presses until C1 has discharged, thus providing a simple keyboard lock-out feature if an invalid key is pressed. Only pressing S1, S2 and S3 in that order will cause output Q3 to go high and switch on the transistor TR1 via buffer resistor R6 thus energising the relay.

The value chosen for C1 will depend on the time for which the relay is to remain energised. With R4 equal to 1MΩ, the delay will be about one second for each microfarad.

Code Sequence

Although the keys are labelled S1, S2, S3 etc. in the circuit diagram, they may of course be numbered in any sequence on the keyboard itself. For example, S1 could be key number five while S2 and S3 are numbers seven and three respectively. The open sequence in this case would be 573 and pressing any other sequence will not open the lock. The circuit board has been designed to make it possible to pre-wire any sequence into the circuit.

This simple circuit does have a number of limitations however. One is that each valid number must be different so that sequences such as 444 or 767 cannot be used. Assuming a 3-digit code, this

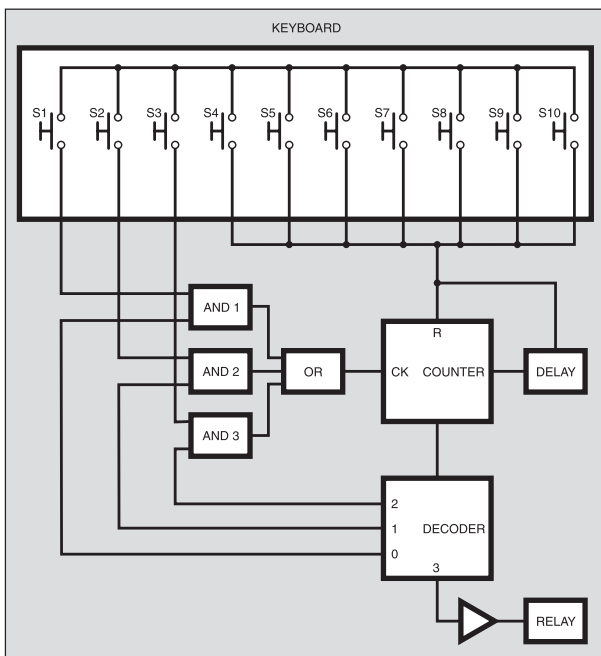


Fig.3.3. Block diagram for the Digital Lock

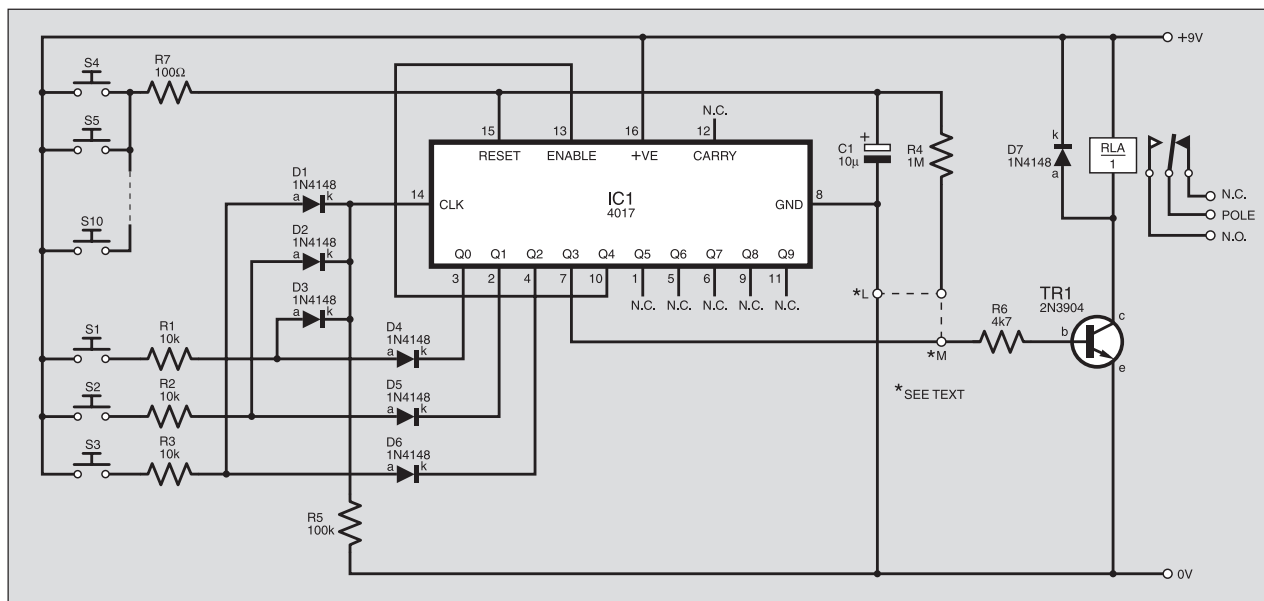


Fig.3.4. Complete circuit diagram for the Digital Lock

therefore provides only 719 possible combinations instead of 999. However, the probability of someone opening the lock, even if they were aware of this fact but did not know the sequence, would still be very low.

A 4-digit sequence could easily be implemented by adding another two diodes and a resistor, and connecting R6 to output Q4 instead of Q3. Alternatively, matters could be made even more complicated for the would-be intruder by adding more keys

(connected to the reset input) thus increasing the chances of pressing an incorrect key.

More sophisticated circuits often include an automatic reset if a valid key is

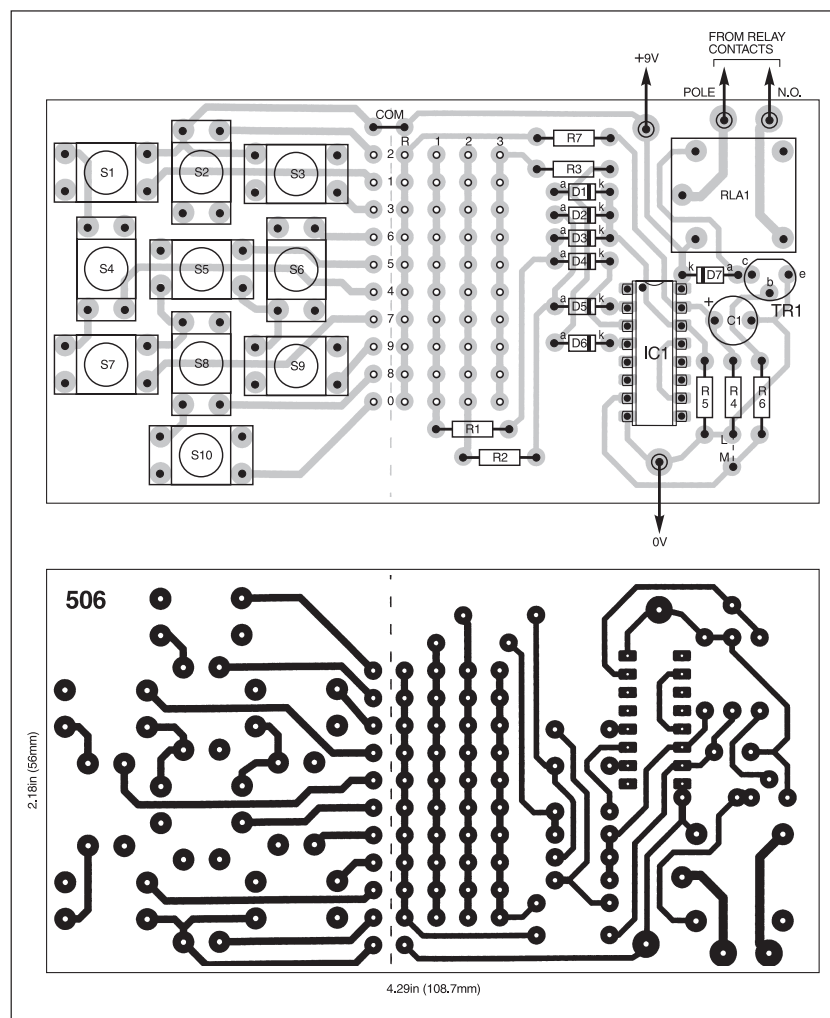


Fig.3.5. Component and track layout details for the Digital Lock printed circuit board

COMPONENTS

Digital Lock

Resistors

R1 to R3	10k (3 off)
R4	1M
R5	100k
R6	4k7
R7	100Ω

See
SHOP
TALK
page

Capacitors

C1	10µ radial elect. 16V (see text)
----	-------------------------------------

Semiconductors

D1 to D7	1N4148 signal diode (7 off)
IC1	4017 decade counter
TR1	2N3904 npn transistor

Miscellaneous

RLA	min. s.p.s.t. relay, 12V, contact rating to suit load, p.c.b. mounting (see text)
S1 to S10	push-to-make switch, p.c.b. mounting (10 off)

Printed circuit board, available from the EPE PCB Service, code 506; case to suit (see text); 16-pin d.i.l. socket; 9V (PP3 type) battery and clip; connecting wire; solder etc.

Approx. Cost
Guidance Only

£9

excl. batt &
hardware

pressed out of sequence, as well as a time limit on entering the correct sequence, or an anti-tamper alarm and a timed keyboard lockout if a preset number of incorrect entries are made.

All of these features could be added, but the circuit complexity and cost would inevitably increase. In the end, it boils down to what the circuit will be used to protect and even with a six or seven digit sequence and numerous alarms fitted, the thief could still make a lucky guess. After all, people have sometimes guessed the correct numbers in the national lottery!

The circuit draws virtually no power except when the relay is energised so that it is ideal for battery operation, provided a suitable relay is chosen and the circuit is not left in the "open" state for long periods.

Alternatively, connecting R4 to output Q3 (point M) instead of 0V (point L) will reset the circuit a short period after the lock is opened, thus limiting the length of time for which the relay will remain energised. This (momentary) mode of operation is most suitable for use with doors where the lock remains open for a period sufficient to allow authorised persons to enter and then locks automatically behind them.


Construction

Printed circuit board component and track layouts are shown in Fig.3.5. This board is available from the *EPE PCB Service*, code 506. It has been designed to hold all of the components, including the relay and the keys for the keyboard.

Depending on the application, a standard keyboard or one built from individual keys may be used, and this may be separated from the main circuit by cutting the board along the dotted line. The two parts may then be connected by an 11-way (ribbon) cable.

The advantage of doing this is that only the keyboard needs to be mounted outside the protected area, so that only its connections will be accessible if the front cover is removed. The rest of the circuit may then be housed within the protected area so that the intruder cannot simply short out the transistor and energise the relay without using the keyboard.

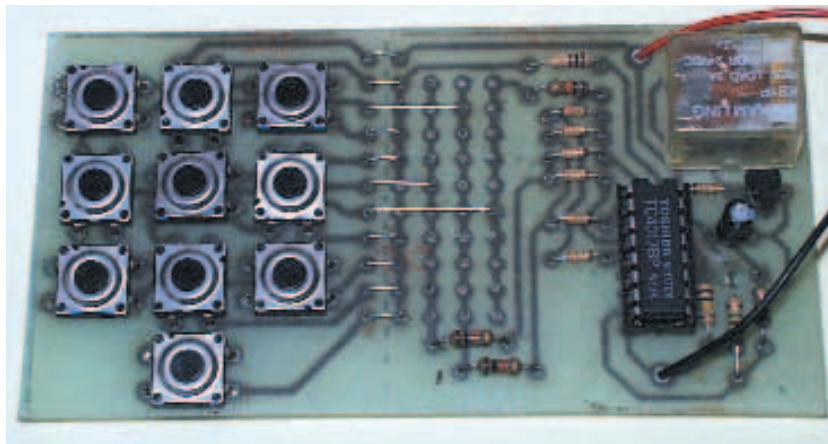Most of the wires from the keyboard will terminate on the first row of connection holes (marked R) but three should be



connected to holes in the rows marked 1, 2 and 3 to define the open sequence. The choice of sequence is up to you. The keyboard common wire should be connected to the pad marked COM (topmost link).

Assemble the board in ascending order of size, starting with the link wires. Use a socket for IC1, but do not insert the i.c. until the circuit has been completed and fully checked, and then observe the anti-static handling precautions mentioned earlier. Ensure all semiconductors are connected the right way around.

The position of resistor R4 depends on whether the relay is to remain energised following the correct entry sequence (Latched) or switch off automatically (Momentary). In the latter case it should be connected to the position marked M. If latched operation is required, the L position should be used.

Power Aspects

The circuit will operate from a range of d.c. voltages from 5V to 15V so that a 9V supply is ideal. The relay should be chosen to suit the supply used, although in practice a 12V relay with a coil resistance of 400Ω will work satisfactorily from a 9V supply.

The relay used in the prototype has changeover contacts and its normally-open contacts are brought out to the pins on the p.c.b. The contacts of any relay chosen should of course be rated for the intended load.

Note that the p.c.b. design is suited only for use with a low voltage load. It

must not be used to control an a.c. mains powered load.

In cases where the load is a d.c. powered door lock solenoid, the relay could be dispensed with altogether and the solenoid connected directly in its place. Alternatively, if only a logic level output is required, a pull-up resistor from TR1 collector (c) to the logic supply would replace the relay. In this case, diode D7 need not be fitted.

Basically, the choice of case in which to house this design is not too important and any plastic or metal enclosure of a suitable size may be used. However, this is also dictated by the keypad and will depend on how and where it is to be mounted.

In most applications, a simple plastic or metal panel drilled or punched out to accept the keypad will suffice. Electrical wiring boxes are probably most convenient as suitable blank panels are available, and they offer the possibility of flush or surface mounting.

If the keypad is mounted remotely from the circuit, removing the front panel would not compromise security so that the keypad enclosure does not need to be particularly robust, unless wanton vandalism is expected. The keypad switches and their enclosure should, of course, be suitable for outdoor use if such is to be the intended application.

Next Month

In Part 4 next month we present a Doorchime and Electronic Dice. □

Obtaining EPE

An initiative in the UK is designed to help you obtain your favourite magazines from newsagents. Called Just Ask! its aim is to raise awareness that newsagents can stock, order and often home deliver magazines.

To raise awareness we will be including the Just Ask! logo in the pages of this and future issues and have included a newsagent order form to help you to obtain copies.

So keep a look out for the logo and next time you visit your newsagent remember to Just Ask! about obtaining copies of your chosen magazines.



NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of *Everyday Practical Electronics* for me each month

Name and Address

..... Post Code Tel

Everyday Practical Electronics is published on the second Thursday of each month and distributed S.O.R. by COMAG

Make sure of your copy of EPE each month – cut out or photostat this form, fill it in and hand it to your newsagent.

Net Work

The Internet Page

Alan Winstanley



WHENEVER I access a web site searching for software or an upgrade, my heart sinks when I realise that a file download is needed that will take forever to fetch. For example, my Iomega REV backup system required a big driver download before it could work at all in Windows XP Pro, and trying to download and run Musicmatch (the PC music and download site now owned by Yahoo!) became such a frustratingly hair-tearing experience that I nearly threw the system box out of the window onto the pavement below. Many evenings and weekends have been wasted trying to coax various software products into operation that depend on large downloads, but Musicmatch nears the top of my list for causing an early onset of alopecia. It was literally quicker to ask a friend to fetch the files over broadband and mail me a CD.

Because the Internet and personal computers are increasingly co-dependent, these sorts of hassles can turn computer ownership into a challenge without reward, especially if dialup access is the only Internet access available. To meet demands for more bandwidth, BT has over the years variously pushed the rental of second phone lines for dialup modem users, then "Home Highway" ISDN, before turning the spotlight onto ADSL broadband.

The writer gave up any prospect of receiving ADSL broadband when BT emphatically ruled out the conversion of the local exchange, instead promising us wireless or satellite broadband some time in the distant future. However, politics suddenly intervened and 99% of Britain was promised the tantalising prospect of broadband by Summer 2005. Well readers, after waiting many years, Broadband Day, the date that broadband will finally be activated, is almost upon the writer. The wheels are spinning and the tyres are smoking, but the handbrake is jammed firmly on.

In anticipation of Broadband Day, underneath my desk I have a Linksys ADSL2 gateway hooked to a matching Linksys gigabit Ethernet switch, and my recently-rebuilt TCP/IP network fair hums along, but like running a Ferrari on lamp oil, it is still shackled to a POTS telephone line via a 3Com modem. A microfilter hangs forlornly off the gateway in anticipation of the grand switch-on. The Linksys gateway is supplied with simple setup instructions written specially for the UK market, but additional security, fire-wall and anti-virus aspects will also have to be considered before I am willing to let it all loose on broadband.

A Broad Choice

It is fair to say that the slow expansion of a broadband network across Britain has retarded the growth of communications and affected end-users in many ways. Resentment of the slow pace is double-edged, because some urban-based Internet users are now complaining that 512kbps (kilobits per second) or 1Mbps (megabits per second) ADSL is inadequate for their needs. That BT has been forced to devote resources to wiring up the rest of the nation for broadband has, in some eyes, discriminated against heavier broadband users who demand ever more bandwidth for themselves.

Like many users, the writer now faces a choice of new broadband provider. Users are not compelled to buy their broadband service from BT (www.bt.com) and it pays to shop around and compare packages. Tiscali (www.tiscali.co.uk) offers entry-level 512kbps ADSL, which is usage-capped at 30 gigabytes (GB) per month of traffic for £15.99 per month, or for the same price 1Mbps is available with 2GB per month usage, plus £1.50 per GB excess.

For £19.99 their new 2Mbps service provides 15GB usage also with £1.50 per GB excess. A useful competitor comparison chart is shown on Tiscali's web site.

Also worth considering is UK Online (www.ukonline.net) which is the UK's first £9.99 broadband provider, available in certain areas only. AOL (www.aol.co.uk) offers unlimited downloads and a free support line for broadband users, and is ideal for all round family-friendly consumer access.

Other considerations on your checklist should include:

- free modem offers
- the minimum lengths of contract
- the cost (if any) of telephone support
- the ability (where desired) to send your own domain-name email (i.e. mail sent FROM:you@your-domain.co.uk, or mail relaying: not possible with AOL, and difficult with BT)
- any connection charges
- Always on, or any timeouts after a period of usage
- is a mailbox included? Do you need one?
- static IP address, important for virtual private networks. Any extra cost.

Be aware that the lowest cost "bareback" broadband services will not include an associated email box, and will only offer a raw broadband connection (which is all that some users want), so check this carefully.

Remember too that you can run a phone or fax machine in parallel once your line is activated for ADSL, so can you save some line rental somewhere else?

What Are We Waiting For?

Connection rates of 1Mbps to 2Mbps sound like dizzying speeds when compared with narrow-band dialup. Over a year ago in Japan, though, 12Mbps ADSL services were available as standard, and one westerner working out there expressed disappointment that "only" 12Mbps was all that he could receive, due to the distance from his exchange. Japanese consumers can today sign up for ADSL supplied under the Yahoo! BB brand at a speed of up to 50Mbps download and 3Mbps upload, with Yahoo's IP phone service thrown in.

Japan's extraordinary adoption of high speed fibre internet means that typical rates of up to 30Mbps will be available, shared with 32 users on a 1Gbps feed. Telephone calls will cost next to nothing. British domestic users are already complaining that 512kbps is almost as slow as dialup at times, and 1Mbps to 2Mbps isn't enough either.

Having thrown away a whole series of dialup modems in the name of progress, at least my ADSL2 gateway will cope with up to 25Mbps if ever they can squeeze it up the telegraph pole outside the door. Meantime, roll on Broadband Day at the end of May 2005. It can't come quickly enough: a bit like my Internet traffic really.

I'll be offering more practical tips about Internet and web usage in future *Net Work* articles. You can email feedback to me at alan@epemag.demon.co.uk.

By the time you read this, the new *EPE Chat Zone* should be in full swing. The new access address to bookmark is www.chatzones.co.uk.

PIC N' MIX

JOHN BECKER

Our periodic column for your PIC programming enlightenment

Data Tables and the DE directive, and a "D"ebatable problem with VB

READER John Waller of Plainville USA recently emailed the author, saying, "my first PIC18F452s arrived and I ran your PIC18F demo program OK, having changed the PIC type to 452. One question about your program: Malcolm Wiles in his follow-up article explains what **DB** is used for, but not the **DE** you use against the last table in the program. Can you explain?"

The articles to which John refers are my *PIC Toolkit TK3 Simulator and PIC18F Upgrade* (Mar '05), and Malc's *PIC18F Microcontroller Family* (Apr '05).

Malc explained that the **DB** statements can be used to set up arrays of data bytes in program memory, e.g.:

```
TABLCD
DB B'00110011', B'00110011'
DB B'00110010', B'00101100'
```

DB tables can be placed anywhere convenient in the program, and the table is accessed via an indexed call to its label, **TABLCD** in this instance.

The **DE** statement, however, is the prefix that allocates a value to the PIC's data EEPROM. Although **DB** does not need locations to be specified, **DE** does, as in the following 18F example:

```
ORG H'F00000' ; 18F
DE 'A'
DE 'B'
DE 'C'
DE 'D'
```

The **ORG H'F00000'** sets the location at which the programming software places the first data byte. Ignore the fact that the address value appears to be higher than would really exist in a PIC – it's the prefix **H'F0'** which is the code for EEPROM use, and then **0000** is the first address (in HEX) within that dedicated block. Each data value is placed at consecutive addresses from that first location. All **DE** values are placed at the end of the program.

DE has been widely used in many published 16F designs as well, the following is an example of its use:

```
ORG H'2100' ; 16F
DE 1
DE 2
DE 3
DE 4
```

The start location is now specified as **ORG H'2100'**, the first 16F data EEPROM location available.

Formatting for 18F DE

It is important to note that in 18F, MPASM treats the format of data values in single **DE** statements (as above) and multiple **DE** statements (e.g. **DE 5,6,7,8**) differently. The following **DE** statements produce the HEX code shown in Table 1a, illustrating the difference between the two formats:

```
ORG H'F00000' ; data EEPROM 18F
                    assembly address
```

```
DE 1,2,3,4,5,6,7,8,9,10,11,12,13,14,15
DE 1
DE 2
DE 3
DE 4
DE 5
DE 6
DE 7
DE 8
```

In the HEX code shown in Table 1a, the **DE** values are held in the eight central sections, between the EEPROM address data at the left and the checksum at the right (separated out for clarity).

In the first line, representing the multiple statements, the **DE** values have been converted to HEX as expected, but note that the **DE** table line has an uneven number of values and MPASM gives an extra "00" at the end of the line to make the quantity even.

In the second line, representing the single statements, note now how *each* value also has an extra "00" allocated.

It is important to take these differences in representation into account when writing code to make calls to and from an 18F program's **DE** tables.

As an example of 16F **DE** tables, the hex lines in Table 1b were produced by MPASM from the same table above (but

prefixed by **ORG H'2100'**). It will be seen that all values, whether expressed singly or in multiples on the same line, all have an extra "00" added.

DE and TK3

TK3 handles 16F **DE** tables in the same way as does MPASM, (Table 1b). However, at the present time, **TK3** does not follow MPASM for multiple 18F **DE** statements, but uses the same principle as for 16F. Table 1c illustrates the point, again assembled from the same table data given above.

Eventually, **TK3** will be modified in a future version to comply with MPASM's multiple statement format. In the meantime, it is recommended that if you are writing for 18F through **TK3**, you always use multiple **DE** statements with an even number of values on any line. If you do this, then **DE** statements that you assemble and program with the current version of **TK3** will have the same effect when **TK3** is modified.

It is also recommended that if you are using an assembler other than MPASM or **TK3** that you check how it handles **DE** statements.

D-Numbered Labels

Reader Peter Hardy emailed me about what turned out to be a really intriguing problem which he'd come across when using **TK3's** Simulator and his test code shown in Table 2.

Peter could only get the program to run if he "commented out" the three statements **GOTO D10x**. With the lines left in, the Simulator crashed. Running Peter's code on my system showed that the statement **GOTO D10B** caused Visual Basic to crash, quoting an "Overflow Error".

Further investigation showed that **VB** does not like statements such as **D10B**

Table 1

1a.	18F MPASM :10000000 0102 0304 0506 0708 090A 0B0C 0D0E 0F00 78 :10001000 0100 0200 0300 0400 0500 0600 0700 0800 BC
1b.	16F MPASM and TK3 :10420000 0100 0200 0300 0400 0500 0600 0700 0800 8A :10421000 0900 0A00 0B00 0C00 0D00 0E00 0F00 0100 49 :0E422000 0200 0300 0400 0500 0600 0700 0800 6D
1c.	18F TK3 :10000000 0100 0200 0300 0400 0500 0600 0700 0800 CC :10001000 0900 0A00 0B00 0C00 0D00 0E00 0F00 0100 8B :0E002000 0200 0300 0400 0500 0600 0700 0800 AF

and **D10C**. The Sim program imports each code line (as variable **TempA\$**) as in the following example format:

```
14 D10C GOTO D10D ; 2 cycles 28 0F
```

It is prefixed by the line count number, 14 in this case. Following the line number, the code line as in the original ASM statement is given, followed by the twin-byte HEX value of the command as would be sent to the PIC (28 0F here).

The Sim program asks itself what value the statement has at its start to extract the line number. Unfortunately, VB not only sees the 14, but also the D and the value beyond it, 10 here. In the case of **14 D10C**, the value it finds is actually 140000000000 (it ignores the C), D having a specific mathematical meaning.

VB does not like such large numbers unless it has been told to expect them, which it hasn't in the Sim. Consequently it crashes, giving the system message of "Overflow".

Sometime I'll recode this section of the Sim, but in the meantime, the situation can be avoided by prefixing the D with

DELAY10US	GOTO D10B	; 2 cycles
D10B	GOTO D10C	; 2 cycles
D10C	GOTO D10D	; 2 cycles
D10D	NOP	; 1 cycle
	DECFSZ CLCK,F	; 1 cycle
	GOTO DELAY10US	; 2 cycles
	RETURN	

another letter that does not have maths significance. But beware that the letter E might also cause problems, though I have not checked this. You could also follow the D by another letter so that a value beyond D is not seen (in this case "10").

In Peter's full example listing I also found that the Sim does not like labels associated with NOP, e.g.:

```
LABEL1 NOP
```

I'll fix this sometime. Until I do,

though, if you simply want a Sim delay of one cycle to occur at a label, instead of using NOP, use a non-invasive 1-cycle statement like **MOVF CLCK,F**, which does not affect W, but only affects the Z flag.

PICing Mixed Queries

Do you have any PIC-related questions you'd maybe like us to consider for answering via *PIC n' Mix*? If so, email them to john.becker@wimborne.co.uk.



PIC Ultrasonic Scanner

The first point to make concerning component parts for the *PIC Ultrasonic Scanner* project concerns the motor driver chip. It is most important that when ordering the L293DN 16-pin half-H driver chip (also known as a stepper motor driver i.c.) that you emphasize you require one with the DN suffix. The D denotes it is a 16-pin device and has diode protection. Do not use other L293 device types as they may not have the same characteristics and could be 20-pin versions. The one used in the prototype was purchased from **Rapid Electronics** (☎ 01206 751166 or www.rapidelectronics.co.uk), code 82-0192.

The rest of the semiconductor devices should be readily available. It's doubtful, but if a local source for the MAX232 RS232 serial interface driver proves to be elusive, it can be ordered direct (credit card only) from **RS** (☎ 01536 444079 or rswww.com), code 655-290.

Ultrasonic transducers are usually sold in pairs, transmitter and receiver, so it might be an idea to adopt the dual sensor approach. The author obtained his from Rapid (see above) and can be purchased as individual items. You have a choice of sealed (outdoor use) and unsealed devices, codes:Tx 35-0182, Rx 35-0184; and Tx 35-0175, Rx 35-0180 respectively.

For those readers unable to program their own PICs, fully programmed PIC16F877 microcontrollers can be purchased from **Magenta Electronics** (☎ 02083 565435 or www.magenta2000.co.uk) for the inclusive price of £10 each (overseas add £1 for p&p). The software, including source code files, is available on a 3.5in. PC-compatible disk (Disk 8) from the *EPE Editorial Office* for a sum of £3 each (UK), to cover admin costs (for overseas charges see page 445). The software is also available for free download via the Downloads link on our UK website at www.epemag.co.uk.

The printed circuit board is available from the *EPE PCB Service*, code 503 (see page 445). The 2-line 16-character (per line) alphanumeric display is a standard I.c.d. module and most of our components advertisers should be able to offer a suitable device.

Super-Ear Audio Telescope

No real component problems should arise when shopping for components for the *Super-Ear Audio Telescope* project. Most component advertisers will probably list the low value miniature electrolytic capacitor (C5) as 0.22µF rather than 220nF. You can, if you wish, use a ceramic disc type which seems to be a more widely stocked item.

With IC1's output impedance being 64 ohms, the author suggests that "walkman-type" earphones are ideal for this project and are recommended over miniature loudspeakers. Of course, the size and type of jack socket you select will depend on the headphones/earphones used. The one in the model is a 3.5mm mono enclosed type and

came from **Rapid Electronics** (☎ 01206 751166 or www.rapidelectronics.co.uk), code 20-0135.

Most of our component advertisers should be able to offer a suitable omni-directional sub-miniature microphone insert. However, many seem to only stock ones with solder pad connections and not p.c.b. mounting pins. Obviously, the pad type will need extra care when soldering to the board interconnecting leads.

The BC109C transistor and the LM386N audio i.c. should be "off the shelf" items. You may not find an aluminium two piece U-shaped box to the exact dimensions specified but one slightly larger should be selected, not smaller. Before you purchase a length of copper pipe from your local DIY supplier, check the diameter of your microphone insert and don't forget to allow for the thickness of the wrap-around insulating tape.

Back to Basics – Part 3 Scarecrow/Digital Lock

The piezoelectric horn specified for the *Scarecrow*, one of this month's *Back to Basics* projects, was purchased from **Rapid Electronics** (☎ 01206 751166 or www.rapidelectronics.co.uk), code 35-1460. Some readers may experience problems locating the MOSFET transistors locally. You could try **ESR Components** (☎ 0191 257 4363 or www.esr.co.uk).

The miniature "tactile" switches used in the *Digital Lock*, the second project, should be generally available. Note that although they have four connecting pins, each switch contact is connected to two pins so they have to be inserted on the p.c.b. as shown in the article to complete the "common" line.

As most readers will purchase a relay with contacts rated to suit their own intended application, the chances are that it will not fit directly on the p.c.b. The answer is to "hard wire" it to the board.

The two printed circuit boards are available from the *EPE PCB Service*, codes 505 (Scarecrow) and 506 (Lock).

Radio Control Model Switcher

For those readers unable to program their own PIC16F84A chip for the *Radio Control Model Switcher* project, fully programmed microcontrollers can be purchased from **Magenta Electronics** (☎ 02083 565435 or www.magenta2000.co.uk) for the inclusive price of £5.90 each (overseas add £1 for p&p). The software, including source code files, is available on a 3.5in. PC-compatible disk (Disk 8) from the *EPE Editorial Office* for a sum of £3 each (UK), to cover admin costs (for overseas charges see page 445). The software is also available for Free download via the Downloads link on our UK website at www.epemag.co.uk.

The rest of the components should be readily available from our component advertisers. You must use a TO220 insulating kit to mount the transistor on the circuit board as its metal tab is also connected to one of the leadout pins.

The Switcher printed circuit board is available from the *EPE PCB Service*, code 504 (see page 445).

Circuit Surgery – Compact Flash Card

Those readers wanting to experiment with *CompactFlash Cards*, a small interface p.c.b. is available from the *EPE PCB Service*, code 507 (see page 445).

INTERFACE

Robert Penfold



COMPUTER-CONTROLLED PWM POWER SUPPLY

THE previous *Interface* article (April '05) covered a PC Controlled Power Supply that used a digital-to-analogue converter (DAC) based on the AD557JN 8-bit converter chip. Many applications of digital-to-analogue converters require a normal d.c. output, and a bench power supply unit clearly fits into this category. However, there are many applications where it is better to use a pulsed signal. The big advantage of using pulsed control is that it greatly reduces the power wasted in the control circuit, and the amount of heat produced by this wasted energy.

A series regulator, as used in the power supply, is effectively a variable resistor in series with the load. At some output voltages there is a large voltage drop through the series resistor and a high current flow.

This combination of high current and large voltage drop results in a substantial amount of power being dissipated in the output device. Although the output voltages and currents provided by the PC Controlled Power Supply are fairly modest, the output transistor still requires a substantial heatsink in order to avoid overheating.

Switched On

With a pulsed controller the output transistor operates as a switch, and it provides either the full output potential or no output voltage at all. With a theoretically perfect switch there is no power wasted in the control circuit. The switch passes a high current when it is closed, but the voltage drop is zero, giving zero power loss. No output current at all flows when the switch is open, and the output power is therefore zero.

Of course, real-world electronic switches do not achieve anything approximating to theoretical perfection. There is normally a negligible current flow when a switching transistor is turned off, but there is a significant voltage drop when a semiconductor is switched on and passing a high current. Even so, pulsed control is usually much more efficient than using some form of variable resistance.

Pulse control varies the average output voltage rather than providing a continuous voltage. For example, in order to set the output voltage at half the maximum supply potential, an output signal with a 1:1 mark-space ratio is used. The output voltage is at maximum for 50 percent of the time while the output is switched on, and at zero for the other 50 percent of the time. This gives an average output potential of half the maximum level.

Any required output potential from zero to maximum can be obtained by using the appropriate mark-space ratio. For (say) an output potential equal to 70 percent of the maximum potential, the output would be switched on for 70 percent of the time, and off for 30 percent of the time.

Basic pulse control is not usable in all applications, while in others due care has to be taken when selecting the pulse frequency. A very low frequency is unlikely to work properly with any type of load. Light emitting diodes (l.e.d.s) and filament bulbs would flash rather than dim, and a d.c. electric motor would have a very jerky action. A high pulse frequency could give problems with some types of load, and would tend to generate strong radio frequency interference (r.f.i.). A frequency in the region of 100Hz to 500Hz is suitable for most practical applications of pulse control.

Pulse Width Modulation

It is possible to generate the pulse signal using a single digital output and some simple software routines. This method has been covered more than once in previous *Interface* articles, and it has the obvious advantage of requiring little hardware. It simply requires a buffer/amplifier to provide the required maximum output voltage and current.

The drawback of this method is that generating the pulse signal can take up a fair amount of the processor's time. There is an alternative method that requires more hardware but is less demanding on the processor.

The basic setup used in the Pulse Controller featured here is shown in Fig.1, and it uses a DAC plus simple pulse width modulation (PWM). The converter provides an output voltage range of 0V to 2.55V, which is inadequate to drive the pulse width modulator properly. A d.c. amplifier is therefore used to boost the maximum output voltage to about 5-6 volts.

The voltage comparator and triangular oscillator form a conventional pulse width modulator. The output of the comparator goes high if the output potential from the converter is higher than the voltage from the oscillator. At low output voltages from the converter the oscillator always provides the higher potential, and the output of the comparator is permanently low.

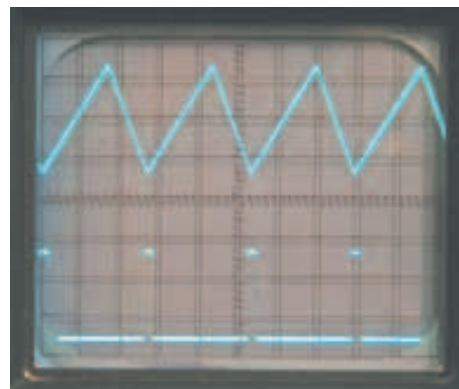


Fig.2. The oscillator (top) and comparator output signals at a low output voltage

Setting the output voltage from the converter a little higher results in it providing the higher potential during the troughs of the oscillator's signal. This results in the output of the comparator pulsing high during these periods – see screen shot Fig.2.

Taking the output voltage of the converter even higher results in it providing the higher potential for a greater proportion of the time. With its output set at roughly the middle output voltage from the oscillator, the output from the comparator has a mark-space ratio of about 1:1 (see screen display Fig.3). If the converter's output voltage is taken still higher, the oscillator will only provide the higher voltage during signal peaks. The output of the comparator is therefore high for most of the time, and it only goes low during the signal peaks from the oscillator (see Fig.4).

By using an even higher output potential from the converter, the oscillator always provides the lower voltage, even during signal peaks. The output from the comparator then goes high continuously.

A buffer amplifier at the output of the comparator enables the circuit to provide sufficient output current to drive filament bulbs, a d.c. electric motor, a bank of l.e.d.s, or whatever. Voltage amplification could be

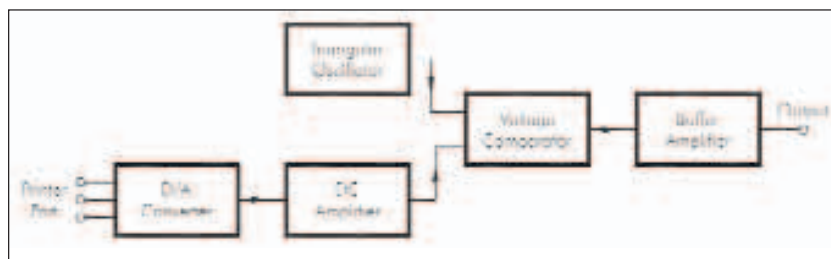


Fig.1. The block diagram for the pulse controller. The oscillator and comparator form a conventional pulse width modulator

included here as well, but a simple buffer stage is all that is used in the present design.

Pulse Circuit

The full circuit diagram for the Pulse Controller is shown in Fig.5. The converter is an 8-bit type based on an AD557JN chip (IC1). It is provided with a stabilised 5V supply by voltage regulator IC2. This part of the circuit is the same as the equivalent section of the computer controlled power supply unit featured previously, and it will not be considered further here.

Note that the bias voltage provided by resistors R3 and R4 has deliberately been made much lower than the normal mid-supply level. This is necessary because the output voltage range of IC3 is not centred on the mid-supply level, but at a much lower potential.

Even with the aid of this lop-sided biasing, there will be a small range of low converter values that give zero output, and a small range of high values that give maximum output. Where necessary, the software can be written to take this into account. The circuit should

of 12V is available, with the “missing” three volts being dropped through the output stage. This voltage drop means that transistor TR1 has to dissipate up to about 6W at maximum output voltage and current. The power dissipated by TR1 drops in proportion to the average output voltage, so it never has to dissipate more than about 6W. A heatsink having a rating of about 10 degrees Celsius per watt or better is required.

Be aware that the AD557JN used for IC1, the CA3140E used for IC3 and IC5,

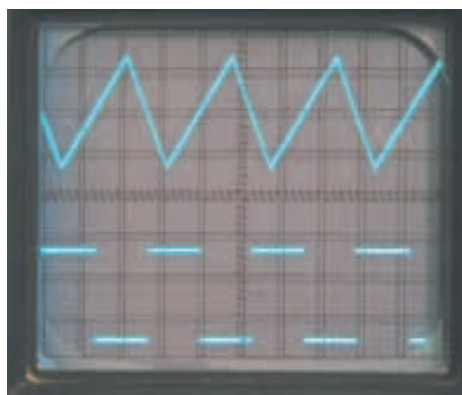


Fig.3. The oscillator and comparator outputs at a middle output potential

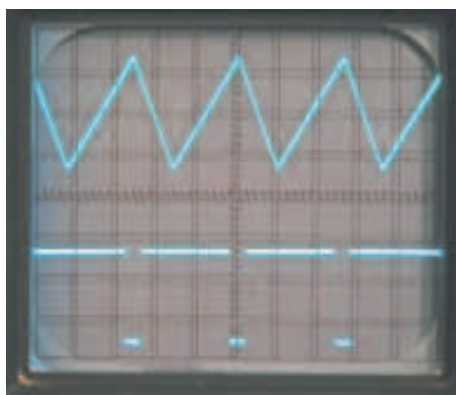


Fig.4. The oscillator and comparator output signals with almost maximum output voltage

A simple non-inverting amplifier, IC3, has its voltage gain set at just over two times by the negative feedback network made up of resistors R1 and R2. This gives the required 0V to 5.6V output range at pin 6 of IC3.

A dual operational amplifier (op. amp), IC4, is used to provide the triangular signal. It uses a conventional configuration that has IC4a as an integrator and IC4b as a trigger circuit. Triangular and square-wave signals are produced at the outputs of IC4a and IC4b respectively, but in this case it is only the triangular signal at pin 1 of IC4a that is required.

This is fed to the inverting input (pin2) of comparator IC5, and the output of IC3 is fed to the non-inverting input (pin3). The output frequency of the oscillator is about 200Hz, but it is easily changed by altering the value of capacitor C3. The output frequency is inversely proportional to the value of this component.

still provide well over 200 different output levels, which should be more than adequate for normal applications.

Transistor TR1 is used as an emitter follower buffer stage at the output of IC5. Although the maximum drive current available from IC5 is only a few milliamps, the TIP121 used for TR1 is a power Darlington device that has a very high current gain. Consequently, the circuit can provide output currents of up to about 2A.

There is no built-in current limiting, so the power supply should include this feature. Resistor R8 ensures that TR1 always has a significant load. Diode D1 suppresses any high voltage spikes that occur if the circuit is used to drive an inductive load such as an electric motor.

Finally

The circuit requires a reasonably stable 15V supply. A maximum output voltage

and the CA3240E used for IC4 are all MOS devices that require the standard anti-static handling precautions.

The CA3140E and CA3240E are operational amplifiers that can be used in d.c. circuits without the aid of a negative supply. Few other types will work properly in this circuit, and the use of substitutes is not recommended. A TIP121 is specified for TR1, but a TIP122 will also work in this circuit.

The software for the Computer Controlled Power supply (April '05 *Interface*) can also be used for testing this circuit. Bear in mind though, that this circuit is only designed to provide a range of output potentials for *simple* d.c. power control applications. It does not provide anything approaching the precision available from the Computer Controlled Power Supply project.

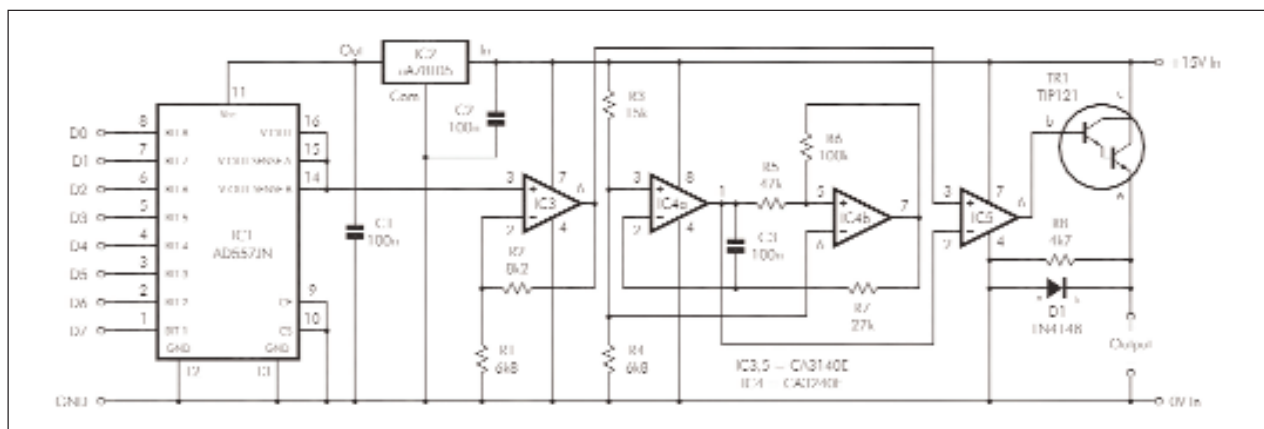


Fig.5. The full circuit diagram for the Pulse Controller. A maximum output potential of 12V can be provided, and the maximum output current is 2A

DIRECT BOOK SERVICE

NOTE: ALL PRICES INCLUDE UK POSTAGE

FREE *Electronics Hobbyist Compendium*
book with Teach-In 2000 CD-ROM



EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* interactive software (Win 95, 98, ME and above) covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

Teach-In 2000 covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface (Win 95, 98, ME only) which allows a PC to be used as a basic oscilloscope.

ONLY **£12.45** including VAT and p&p

Order code Teach-In CD-ROM

Circuits and Design

PREAMPLIFIER AND FILTER CIRCUITS

R. A. Penfold

Provides circuits and background information for a range of preamplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and a specialist high performance audio preamplifier i.c. results in circuits that have excellent performance, but which are still quite simple. All the circuits featured can be built at quite low cost. The preamplifier circuits featured include: Microphone preamplifiers (low impedance, high impedance, and crystal). Magnetic cartridge pick-up preamplifiers with R.I.A.A. equalisation. Crystal/ceramic pick-up preamplifier. Guitar pick-up preamplifier. Tape head preamplifier.

Other circuits include: Audio limiter. Passive tone controls. Active tone controls. PA filters (highpass and low-pass). Scratch and rumble filters. Loudness filter. Mixers. Volume and balance controls.

92 pages

Temporarily out of print

MICROCONTROLLER COOKBOOK

Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages

Order code NE26

£23.99

A BEGINNER'S GUIDE TO TTL DIGITAL ICs

R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the "real world".

142 pages

Order code BP332

£5.45

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias – tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages

Order code BP53

£5.49

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER
SELECTION OF BOOKS
SEE THE NEXT TWO
ISSUES OF EPE

All prices include UK
postage

WINDOWS XP EXPLAINED

N. Kantaris and P. R. M. Oliver

If you want to know what to do next when confronted with Microsoft's Windows XP screen, then this book is for you. It applies to both the Professional and Home editions. The book was written with the non-expert, busy person in mind. It explains what hardware requirements you need in order to run Windows XP successfully, and gives an overview of the Windows XP environment.

The book explains: How to manipulate Windows, and how to use the Control Panel to add or change your printer, and control your display; How to control information using WordPad, Notepad and Paint, and how to use the Clipboard facility to transfer information between Windows applications; How to be in control of your filing system using Windows Explorer and My Computer; How to control printers, fonts, characters, multimedia and images, and how to add hardware and software to your system; How to configure your system to communicate with the outside world; and use Outlook Express for all your email requirements; How to use the Windows Media Player 8 to play your CDs, burn CDs with your favourite tracks, use the Radio Tuner, transfer your videos to your PC, and how to use the Sound Recorder and Movie Maker; How to use the System Tools to restore your system to a previously working state, using Microsoft's Website to update your Windows set-up, how to clean up, defragment and scan your hard disk, and how to backup and restore your data; How to successfully transfer text from those old but cherished MS-DOS programs.

268 pages

Order code BP514

£7.99

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages – large format

Order code BP901

£14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS – Robert Penfold

Covers the Vision Command System

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on

the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages

Order code BP902

£14.99

PIC YOUR PERSONAL INTRODUCTORY COURSE

SECOND EDITION John Morton

Discover the potential of the PIC microcontroller through graded projects – this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PICs capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too: this is not a reference book – you start work with the PIC straight away.

The revised second edition covers the popular reprogrammable EEPROM PICs: P16C84/16F84 as well as the P54 and P71 families.

270 pages

Order code NE36

£15.99

INTRODUCTION TO MICROPROCESSORS

John Crisp

If you are, or soon will be, involved in the use of microprocessors, this practical introduction is essential reading. This book provides a thoroughly readable introduction to microprocessors, assuming no previous knowledge of the subject, nor a technical or mathematical background. It is suitable for students, technicians, engineers and hobbyists, and covers the full range of modern microprocessors.

After a thorough introduction to the subject, ideas are developed progressively in a well-structured format. All technical terms are carefully introduced and subjects which have proved difficult, for example 2's complement, are clearly explained. John Crisp covers the complete range of microprocessors from the popular 4-bit and 8-bit designs to today's super-fast 32-bit and 64-bit versions that power PCs and engine management systems etc.

222 pages

Order code NE31

£21.99

NEWNES PC TROUBLESHOOTING POCKET BOOK – THIRD EDITION

Howard Anderson, Mike Tooley

All the essential data for PC fault-finding and upgrading. This book provides a concise and compact reference that describes, in a clear and straightforward manner, the principles and practice of fault-finding and upgrading PCs and peripherals. The book is aimed at anyone who is involved with the installation, configuration, maintenance, upgrading, repair or support of PC systems. It also provides non-technical users with sufficient background information, charts and checklists to enable the diagnosis of faults and help to carry out simple modifications and repairs. In order to reflect rapid changes in computer technology (both hardware and software) this new edition has been completely revised and rewritten.

256 pages

Order code NE41

£19.99

NEWNES INTERFACING COMPANION

Tony Fischer-Cripps

A uniquely concise and practical guide to the hardware, applications and design issues involved in computer interfacing and the use of transducers and instrumentation.

Newnes Interfacing Companion presents the essential information needed to design a PC-based interfacing system from the selection of suitable transducers, to collection of data, and the appropriate signal processing and conditioning.

Contents: Part 1 – Transducers; Measurement systems; Temperature; Light; Position and motion; Force, pressure and flow. Part 2 – Interfacing; Number systems; Computer architecture; Assembly language; Interfacing; A to D and D to A conversions; Data communications; Programmable logic controllers; Data acquisition project. Part 3 – Signal processing; Transfer function; Active filters; Instrumentation amplifier; Noise; Digital signal processing.

320 pages

Order code NE38

£26.99

Testing, Theory and Reference

THE AMATEUR SCIENTIST CD-ROM

The complete collection of The Amateur Scientist articles from *Scientific American* magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards. Plus over 1,000 pages of helpful science techniques that never appeared in *Scientific American*. Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather . . . and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems. Includes extensive Science Software Library with even more science tools. Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher. Over 1,000 projects



CD-ROM

Order code AS1 CD-ROM £19.95

BEBOP BYTES BACK (and the Beboputer Computer Simulator) CD-ROM

Clive (Max) Maxfield and Alvin Brown This follow-on to *Bebop to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design . . . and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this! Over 800 pages in Adobe Acrobat format



CD-ROM

Order code BEB2 CD-ROM £21.95

DIGITAL ELECTRONICS – A PRACTICAL APPROACH With FREE Software: Number One Systems – EASY-PC Professional XM and Pulsar (Limited Functionality) Richard Monk

Covers binary arithmetic, Boolean algebra and logic gates, combination logic, sequential logic including the design and construction of asynchronous and synchronous circuits and register circuits. Together with a considerable practical content plus the additional attraction of its close association with computer-aided design including the FREE software.

There is a 'blow-by-blow' guide to the use of EASY-PC Professional XM (a schematic drawing and printed circuit board design computer package). The guide also conducts the reader through logic circuit simulation using Pulsar software. Chapters on p.c.b. physics and p.c.b. production techniques make the book unique, and with its host of project ideas make it an ideal companion for the integrative assignment and common skills components required by BTEC and the key skills demanded by GNVQ. The principal aim of the book is to provide a straightforward approach to the understanding of digital electronics.

Those who prefer the 'Teach-In' approach or would rather experiment with some simple circuits should find the book's final chapters on printed circuit board production and project ideas especially useful. 250 pages

FREE SOFTWARE

Temporarily out of print

OSCILLOSCOPES – FIFTH EDITION Ian Hickman

Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models are available.

This handy guide to oscilloscopes is essential reading for anyone who has to use a 'scope for their work or hobby; electronics designers, technicians, anyone in industry involved in test and measurement, electronics enthusiasts . . . Ian Hickman's review of all the latest types of 'scope currently available will prove especially useful for anyone planning to buy – or even build – an oscilloscope.

The contents include a description of the basic oscilloscope; Advanced real-time oscilloscopes; Accessories; Using oscilloscopes; Sampling oscilloscopes; Digital storage oscilloscopes; Oscilloscopes for special purposes; How oscilloscopes work (1): the CRT; How oscilloscopes work (2): circuitry; How oscilloscopes work (3): storage CRTs; plus a listing of Oscilloscope manufacturers and suppliers. 288 pages

Order code NE37 £22.99

SCROGGIE'S FOUNDATIONS OF WIRELESS AND ELECTRONICS – ELEVENTH EDITION S. W. Amos and Roger Amos

Scroggie's Foundations is a classic text for anyone working with electronics, who needs to know the art and craft of the subject. It covers both the theory and practical aspects of a huge range of topics from valve and tube technology, and the application of cathode ray tubes to radar, to digital tape systems and optical recording techniques.

Since *Foundations of Wireless* was first published over 60 years ago, it has helped many thousands of readers to become familiar with the principles of radio and electronics. The original author Sowerby was succeeded by Scroggie in the 1940s, whose name became synonymous with this classic primer for practitioners and students alike. Stan Amos, one of the fathers of modern electronics and the author of many well-known books in the area, took over the revision of this book in the 1980s and it is he, with his son, who have produced this latest version. 400 pages

Temporarily out of print

PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING Robin Pain

To be a real fault finder, you must be able to get a feel for what is going on in the circuit you are examining. In this book Robin Pain explains the basic techniques needed to be a fault finder.

Simple circuit examples are used to illustrate principles and concepts fundamental to the process of fault finding. This is not a book of theory, it is a book of practical tips, hints and rules of thumb, all of which will equip the reader to tackle any job. You may be an engineer or technician in search of information and guidance, a college student, a hobbyist building a project from a magazine, or simply a keen self-taught amateur who is interested in electronic fault finding but finds books on the subject too mathematical or specialised.

The fundamental principles of analogue and digital fault finding are described (although, of course, there is no such thing as a "digital fault" – all faults are by nature analogue). This book is written entirely for a fault finder using only the basic fault-finding equipment: a digital multimeter and an oscilloscope. The treatment is non-mathematical (apart from Ohm's law) and all jargon is strictly avoided. 274 pages

Order code NE22 £25.99

ELECTRONIC TEST EQUIPMENT HANDBOOK Steve Money

In most applications of electronics, test instruments are essential for checking the performance of a system or for diagnosing faults in operation, and so it is important for engineers, technicians, students and hobbyists to understand how the basic test instruments work and how they can be used.

The principles of operation of the various types of test instrument are explained in simple terms with a minimum of mathematical analysis. The book covers analogue and digital meters, bridges, oscilloscopes, signal generators, counters, timers and frequency measurement. The practical uses of these instruments are also examined. 206 pages

Order code PC109 £9.95

DIGITAL GATES AND FLIP-FLOPS Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic. 200 pages

Order code PC106 £9.95

UNDERSTANDING ELECTRONIC CONTROL SYSTEMS Owen Bishop

Owen Bishop has produced a concise, readable text to introduce a wide range of students, technicians and professionals to an important area of electronics. Control is a highly mathematical subject, but here maths is kept to a minimum, with flow charts to illustrate principles and techniques instead of equations.

Cutting edge topics such as microcontrollers, neural networks and fuzzy control are all here, making this an ideal refresher course for those working in industry. Basic principles, control algorithms and hardware control systems are also fully covered so the resulting book is a comprehensive text and well suited to college courses or background reading for university students.

The text is supported by questions under the headings Keeping Up and Test Your Knowledge so that the reader can develop a sound understanding and the ability to apply the techniques they are learning. 228 pages

Order code NE35 £20.99

HOW ELECTRONIC THINGS WORK – AND WHAT TO DO WHEN THEY DON'T Robert Goodman

You never again have to be flummoxed, flustered or taken for a ride by a piece of electronics equipment. With this fully illustrated, simple-to-use guide, you will get a grasp on the workings of the electronic world that surrounds you – and even learn to make your own repairs.

You don't need any technical experience. This book gives you: Clear explanations of how things work, written in everyday language. Easy-to-follow, illustrated instructions on using test equipment to diagnose problems. Guidelines to help you decide for or against professional repair. Tips on protecting your expensive equipment from lightning and other electrical damage. Lubrication and maintenance suggestions.

Covers: colour TVs, VCRs, radios, PCs, CD players, printers, telephones, monitors, camcorders, satellite dishes, and much more!

394 pages

Order code MGH3 £21.99

VINTAGE RADIOS – COLLECTING • SERVICING • RESTORING Tony Thompson

The essential guide to collecting, repairing and restoring vintage valve radios. These receivers are becoming ever more popular as collectibles, this is a good thing because it means that a very large piece of technological history is being reclaimed when at one time many thought it lost forever. If you look around, you will find plenty of valve radio sets just waiting for a loving restoration. They may not yet be the most highly prized, and they are unlikely to be in top condition, but they can be yours and, if you develop the skills outlined in this book, you will possess radio receivers to be proud of.

The book covers radio history, styling, faultfinding, chassis and cabinet restoration, types of set. 124 pages spiral bound

Order code TT1 £13.50



All prices include UK P&P



Project Building

ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages

Temporarily out of print

BUILDING VALVE AMPLIFIERS

Morgan Jones

The practical guide to building, modifying, fault-finding and repairing valve amplifiers. A hands-on approach to valve electronics – classic and modern – with a minimum of theory. Planning, fault-finding, and testing are each illustrated by step-by-step examples.

A unique hands-on guide for anyone working with valve (tube in USA) audio equipment – as an electronics experimenter, audiophile or audio engineer.

Particular attention has been paid to answering questions commonly asked by newcomers to the world of the vacuum tube, whether audio enthusiasts tackling their first build, or more experienced amplifier designers seeking to learn the ropes of working with valves. The practical side of this book is reinforced by numerous clear illustrations throughout.

368 pages

Order code NE40

£21.99

Theory and Reference

NEWNES DICTIONARY OF ELECTRONICS

S.W. Amos, R.S. Amos

A concise glossary for electronics, TV, radio and computing, including a handy appendix of acronyms. The Newnes Dictionary of Electronics has become an essential item on the bookshelves of electronics engineers, managers, technicians, students and enthusiasts. The book is in a convenient compact format that makes it an ideal working dictionary. The definitions are clear and concise, supported by numerous illustrations and circuit diagrams.

389 pages

Order code NE42

£13.99

GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages

Order code BP239

£5.49

PRACTICAL ELECTRONIC FILTERS

Owen Bishop

This book deals with the subject in a non-mathematical way. It reviews the main types of filter, explaining in simple terms how each type works and how it is used.

The book also presents a dozen filter-based projects with applications in and around the home or in the constructor's workshop. These include a number of audio projects such as a rhythm sequencer and a multi-voiced electronic organ.

Concluding the book is a practical step-by-step guide to designing simple filters for a wide range of purposes, with circuit diagrams and worked examples.

188 pages

Order code BP299

£5.49

ELECTRONIC PROJECTS FOR EXPERIMENTERS

R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded "seen it all before" syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different.

The subjects covered include:- Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red "torch", Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

138 pages

Order code BP371

£5.45

PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374

£5.45

ELECTRONIC MUSIC AND MIDI PROJECTS

R. A. Penfold

Whether you wish to save money, boldly go where no musician has gone before, rekindle the pioneering spirit,

or simply have fun building some electronic music gadgets, the designs featured in this book should suit your needs. The projects are all easy to build, and some are so simple that even complete beginners at electronic project construction can tackle them with ease. Stripboard layouts are provided for every project, together with a wiring diagram. The mechanical side of construction has largely been left to the individual constructors to sort out, simply because the vast majority of project builders prefer to do their own thing.

None of the designs requires the use of any test equipment in order to get them set up properly. Where any setting up is required, the procedures are very straightforward, and they are described in detail.

Projects covered: Simple MIDI tester, Message grabber, Byte grabber, THRU box, MIDI auto switcher, Auto/manual switcher, Manual switcher, MIDI patchbay, MIDI controlled switcher, MIDI lead tester, Program change pedal, Improved program change pedal, Basic mixer, Stereo mixer, Electronic swell pedal, Metronome, Analogue echo unit.

138 pages

Order code PC116

£5.45

VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages

Order code PC115

£5.45

BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £2 per book. For the rest of the world airmail add £3 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, Amex, Diners Club or Maestro to:

**DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LTD.,
408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. *Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.*

For a further selection of books see the next two issues of EPE.

Tel 01202 873872 Fax 01202 874562. Email: dbs@wimborne.co.uk

Order from our online shop at: www.epemag.co.uk

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

☐ Please charge my card £ Card expiry date.....

Card Number Switch/Maestro Issue No.....

Card Security Code (the last three digits on or just under the signature strip)


Please send book order codes:

.....



Please continue on separate sheet of paper if necessary
If you do not wish to cut your magazine, send a letter or copy of this form

ELECTRONICS MANUALS ON CD-ROM £29.95 EACH

ELECTRONICS SERVICE MANUAL

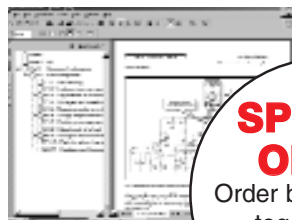

THE MODERN ELECTRONICS MANUAL

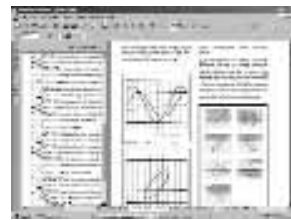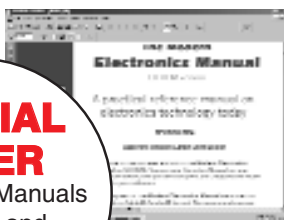

SPECIAL OFFER

Order both Manuals together and
SAVE £10

Everything you need to know to get started in repairing electronic equipment

- Around 900 pages • Fundamental principles • Troubleshooting techniques • Servicing techniques • Choosing and using test equipment • Reference data • Manufacturers' web links
- Easy-to-use Adobe Acrobat format • Clear and simple layout
- Vital safety precautions • Professionally written • Supplements

SAFETY: Safety Regulations, Electrical Safety and First Aid.

UNDERPINNING KNOWLEDGE: Electrical and Electronic Principles, Active and Passive Components, Circuit Diagrams, Circuit Measurements, Radio, Computers, Valves and Manufacturers' Data, etc. **PRACTICAL SKILLS:** Learn how to identify Electronic Components, Avoid Static Hazards, Carry Out Soldering and Wiring, Remove and Replace Components. **TEST EQUIPMENT:** How to Choose and Use Test Equipment, Assemble a Toolkit, Set Up a Workshop, and Get the Most from Your Multimeter and Oscilloscope, etc. **SERVICING TECHNIQUES:** The Manual includes vital guidelines on how to Service Audio Amplifiers. The Supplements include similar guidelines for Radio Receivers, TV Receivers, Cassette Recorders, Video Recorders, Personal Computers, etc. **TECHNICAL NOTES:** Commencing with the IBM PC, this section and the Supplements deal with a very wide range of specific types of equipment – radios, TVs, cassette recorders, amplifiers, video recorders etc. **REFERENCE DATA:** Diodes, Small-Signal Transistors, Power Transistors, Thyristors, Triacs and Field Effect Transistors. Supplements include Operational Amplifiers, Logic Circuits, Optoelectronic Devices, etc.

The essential reference work for everyone studying electronics

- Over 800 pages • In-depth theory • Projects to build • Detailed assembly instructions • Full components checklists • Extensive data tables • Manufacturers' web links • Easy-to-use Adobe Acrobat format • Clear and simple layout • Comprehensive subject range • Professionally written • Supplements

BASIC PRINCIPLES: Electronic Components and their Characteristics; Circuits Using Passive Components; Power Supplies; The Amateur Electronics Workshop; The Uses of Semiconductors; Digital Electronics; Operational Amplifiers; Introduction to Physics, including practical experiments; Semiconductors and Digital Instruments.

CIRCUITS TO BUILD: The Base Manual describes 12 projects including a Therman and a Simple TENS Unit.

ESSENTIAL DATA: Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s.

EXTENSIVE GLOSSARY: Should you come across a technical word, phrase or abbreviation you're not familiar with, simply look up the glossary and you'll find a comprehensive definition in plain English.

The Manual also covers **Safety** and provides web links to component and equipment **Manufacturers and Suppliers**.

Full contents list available online at: www.epemag.wimborne.co.uk

Supplements: Additional CD-ROMs each containing approximately 500 pages of additional information on specific areas of electronics are available for £19.95 each. Information on the availability and content of each Supplement CD-ROM will be sent to you.

Presentation: CD-ROM suitable for any modern PC. Requires Adobe Acrobat Reader which is included on the CD-ROM.

Wimborne Publishing Ltd., Dept Y06, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.

PLEASE

send me



☐ THE MODERN ELECTRONICS MANUAL CD-ROM

☐ ELECTRONICS SERVICE MANUAL CD-ROM

I enclose payment of £29.95 (for one Manual) or £49.90 for both Manuals (saving £10 by ordering both together).

FULL NAME
(PLEASE PRINT)

ADDRESS

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

ORDER FORM

Simply complete and return the order form with your payment to the following address:

Wimborne Publishing Ltd,
Dept. Y06,
408 Wimborne Road East, Ferndown,
Dorset BH22 9ND

Price includes postage to anywhere in the World

We will happily exchange any faulty CD-ROMs but since the content can be printed out we do not offer a refund on these items.

Your CD-ROM(s) will be posted to you by first class mail or airmail, normally within four working days of receipt of your order

EPE PIC PROJECTS VOLUME 1 MINI CD-ROM

A plethora of 20 "hand-PICked" PIC Projects from selected past issues of EPE

Together with the PIC programming software for each project plus bonus articles

The projects are:

PIC-Based Ultrasonic Tape Measure

You've got it taped if you PIC this ultrasonic distance measuring calculator

EPE Mind PICKler

Want seven ways to relax? Try our PIC-controlled mind machine!

PIC MIDI Sustain Pedal

Add sustain and glissando to your MIDI line-up with this inexpensive PIC-controlled effects unit

PIC-based MIDI Handbells

Ring out thy bells with merry tolling – plus a MIDI PIC-up, of course!

EPE Mood PICKer

Oh for a good night's sleep! Insomniacs rejoice – your wakeful nights could soon be over with this mini-micro under the pillow!

PIC Micro-Probe

A hardware tool to help debug your PIC software

PIC Video Cleaner

Improving video viewing on poorly maintained TVs and VCRs

PIC Graphics LCD Scope

A PIC and graphics LCD signal monitor for your workshop

PIC to Printer Interface

How to use dot-matrix printers as data loggers with PIC microcontrollers

PIC Polywhatsit

A novel compendium of musical effects to delight the creative musician

PIC Magick Musick

Conjure music from thin air at the mere untouching gesture of a fingertip

PIC Mini-Enigma

Share encrypted messages with your friends — true spymaster entertainment

PIC Virus Zapper

Can disease be cured electronically? Investigate this controversial subject for yourself

PIC Controlled Intruder Alarm

A sophisticated multi-zone intruder detection system that offers a variety of monitoring facilities

PIC Big-Digit Display

Control the giant ex-British Rail platform clock 7-segment digits that are now available on the surplus market

PIC Freezer Alarm

How to prevent your food from defrosting unexpectedly

PIC World Clock

Graphically displays world map, calendar, clock and global time-zone data

PICAXE Projects

A 3-part series using PICAXE devices – PIC microcontrollers that do not need specialist knowledge or programming equipment

PIC-based Tuning Fork and Metronome

Thrill everyone by at long last getting your instrument properly tuned!

Versatile PIC Flasher

An attractive display to enhance your Christmas decorations or your child's ceiling



**ONLY
£14.45**

**INCLUDING
VAT and P&P**

Order on-line from

www.epemag.wimborne.co.uk/shopdoor.htm

or www.epemag.com (USA \$ prices)

or by Phone, Fax, Email or Post.

NOTE: The PDF files on this CD-ROM are suitable to use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader.

EPE PIC PROJECTS CD-ROM ORDER FORM

Please send me (quantity) EPE PIC PROJECTS VOL 1 CD-ROM

Price £14.45 each – includes postage to anywhere in the world.

Name

Address

.....

.....

..... Post Code

☐ I enclose cheque/P.O./bank draft to the value of £

☐ Please charge my Visa/Mastercard/Amex/Diners Club/Switch

£

Card No.

Card Security Code (The last 3 digits on or just under the signature strip)

Start Date Expiry Date Switch Issue No.

**SEND TO: Everyday Practical Electronics,
Wimborne Publishing Ltd.,**

408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax: 01202 874562.

Email: orders@epemag.wimborne.co.uk

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

BECOME A PIC PROJECT BUILDER WITH THE HELP OF EPE!

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for *airmail* outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.

Back numbers or photostats of articles are available if required – see the *Back Issues* page for details. We do not supply kits or components for our projects.

Please check price and availability in the latest issue. A large number of older boards are listed on our website. Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
Bedside Nightlight (Top Tenner) JAN '04		
Sound Trigger	417	£4.44
Timing/Lamp	418	£4.60
Radio Circuits–8 Dual Conversion SW Rec. – I.F. Amp	428	£5.71
– Signal-Strength Meter	429	£4.45
– B.F.O./Prod. Detector	430	£4.75
★ Car Computer (double-sided)	431	£7.61
★ PIC Watering Timer – Software only	–	–
★ GPS to PIC and PC Interface – Software only	–	–
Jazzy Necklace FEB '04	432 pair	£5.40
Sonic Ice Warning	433	£5.39
★ LCF Meter	434	£5.00
★ PIC Tug-of-War	435	£5.00
Bat-Band Convertor MAR '04	436	£4.76
★ MIDI Health Check – Transmitter/Receiver	437 pair	£7.61
Emergency Stand-by Light	438	£5.55
★ PIC Mixer for RC Planes – Software only	–	–
★ Teach-In '04 Part 5 – Software only	–	–
Infra-Guard APR '04	439	£5.07
★ Moon Clock	442	£5.71
★ Teach-In '04 Part 6 – Software only	–	–
★ EPE Seismograph Logger		
Control Board	440	pair £6.50
Sensor Amp. Board	441	
In-Car Lap-Top PSU MAY '04	443	£4.60
Beat Balance Metal Detector	444	£4.60
Teach-In '04 Part 7 – Transmitter	445	£4.91
Receiver	446	£4.75
Moisture	447	£4.44
★ PIC Quickstep	448	£5.71
Body Detector MkII	449	£4.91
★ Teach-In '04 Part 8 – Software only	–	–
★ MIDI Synchromer – Software only	–	–
Hard Drive Warbler JULY '04	450	£4.60
★ Bongo Box	451	£6.02
Portable Mini Alarm – Sensor	452	£5.23
– Counter	453	£5.07
★ Teach-In '04 Part 9		
PIC Combination Lock Alarm Monitor	454	£5.07
★ EPE Magnetometry Logger	455	£5.71
Keyring L.E.D. Torch AUG '04	456	£4.12
★ Teach-In '04 Part 10 – PIC Curtain or Blind Winder	457	£5.39
Simple F.M. Radio – F.M. Tuner	458	£5.07
– Tone Control	459	£4.75
– Audio Power Amp (TDA2003)	347	£4.60
– Power Supply	460	£5.39
★ EPE Scorer	461	£6.66
– Control Board	462	£7.93
– Display Board	463	£5.55
– Slave Board	–	–
★ PIC to Mouse/Keyboard – Software only	–	–
EPE Wart Zapper SEPT '04	464	£4.60
★ Radio Control Failsafe	465	£4.76
★ AlphaMouse Game	466	£4.60
★ Rainbow Lighting Controller – Software only	–	–
★ Moon and Tide Clock Calendar	467	£5.55
Volts Checker	468	£4.20
★ Smart Karts – Software only	–	–
Logic Probe NOV '04	469	£4.76
Thunderstorm Monitor	470	£5.39
MW Amplitude Modulator		
– V.F.O./Buffer	471	£4.76
– Modulator/PA	472	£5.07
– Power Supply	473	£4.76
Super Vibration Switch DEC '04	474	£4.75
Wind Direction Indicator	475	£6.18
★ PIC Flasher Mk2		
– Control Board	476	£4.75
– Transmitter	477	£4.44
– Multipurpose Board	478	£4.75
– Simple Cyclor	479	£4.44
– Luxeon V Controller	480	£4.44
– Power Supply	473	£4.76

PROJECT TITLE	Order Code	Cost
Light Detector JAN '05	481	£4.44
★ Camera Watch	482	£6.03
Gate Alarm – Oscillator	483	£4.92
– Delay/Timer	484	£4.92
★ Sneaky – Transmitter	485	£4.60
– Receiver	486	£4.91
★ PIC Electric Mk2 – Control	487	£5.87
– Sensor	488	£5.71
Sound Card Mixer	489	£7.29
Headphone Monitor MAR '05	490	£5.71
EPE Cat Flap	491	£6.02
★ Bingo Box – Main	492	£9.04
– Big Digit Display	493	£10.31
Spontaflex Radio– Tuner APR '05	494	£5.55
– Coil Pack	495	£5.71
– Audio Amplifier	496	£5.55
– Tuning Capacitor Board	406	£4.28
★ Safety Interface	497	£6.18
Back-To-Basics 1– Fridge/Freezer Door Alarm	498	£5.39
★ Crossword Solver	499	£6.66
20W Amplifier Module	500	£5.14
Back-To-Logic Basics 2		
Water Level Alarm	501	£5.39
Burglar Alarm	502	£5.87
★ PIC Ultrasonic Scanner	503	£6.66
★ Radio Control Model Switcher	504	£5.87
Back-To-Basics 3		
Scarecrow	505	£5.55
Digital Lock	506	£6.66
CompactFlash Interface Board	507	£6.66

EPE SOFTWARE

Software programs for *EPE* projects marked with a single asterisk ★ are available on 3.5 inch PC-compatible disks or *free* from our Internet site. The following disks are available: **PIC Tutorial V2** (Apr-June '03); **EPE Disk 3** (2000); **EPE Disk 4** (2001 – excl. PIC Toolkit TK3); **EPE Disk 5** (2002); **EPE Disk 6** (2003 – excl. Earth Resistivity and Met Office); **EPE Disk 7** (2004); **EPE Disk 8** (Jan 2005 to current cover date); **EPE Earth Resistivity Logger** (Apr-May '03); **EPE PIC Met Office** (Aug-Sept '03); **EPE Seismograph** (Apr-May '04); **EPE Magnetometry Logger** (July-Aug '04); **EPE Teach-In 2000**; **EPE Spectrum**; **EPE Interface Disk 1** (October '00 issue to current cover date). **EPE Toolkit TK3** software is available on the *EPE* PIC Resources CD-ROM, £14.45. Its p.c.b. is order code 319, £8.24. ★ The software for these projects is on its own CD-ROM. The 3.5 inch disks are £3.00 each (UK), the CD-ROMs are £6.95 (UK). Add 50p each for overseas surface mail, and £1 each for airmail. All are available from the *EPE PCB Service*. All files can be downloaded *free* from our Internet FTP site, accessible via our home page at: www.epemag.co.uk.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
Name			
Address			
Tel. No.			
I enclose payment of £..... (cheque/PO in £ sterling only) to:			
		Everyday Practical Electronics 	
		MasterCard, Amex, Diners Club, Visa or Switch/Maestro  	
Card No.			
Valid From		Expiry Date	
Card Security Code Switch/Maestro Issue No			
(The last 3 digits on or just under the signature strip)			
Signature			
NOTE: You can also order p.c.b.s by phone, Fax, Email or via our Internet site on a secure server: http://www.epemag.wimborne.co.uk/shopdoor.htm			

Everyday Practical Electronics reaches twice as many UK readers as any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £10 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Phone: 01202 873872. Fax: 01202 874562. Email: epreads@wimborne.co.uk

For rates and information on display and classified advertising please contact us as above.

TOTALROBOTS

ROBOTICS, CONTROL & ELECTRONICS TECHNOLOGY

High quality robot kits and components
UK distributor of the OOPic microcontroller

Secure on-line ordering

Rapid delivery

Highly competitive prices

Visit www.totalrobots.com

Tel: 0208 823 9220

X-10® Home Automation We put you in control™

Why tolerate when you can automate?

An extensive range of 230V X-10 products and starter kits available. Uses proven Power Line Carrier technology, no wires required.

Products Catalogue available Online.

Worldwide delivery.

Laser Business Systems Ltd.

E-Mail: info@laser.com

<http://www.laser.com>

Tel: (020) 8441 9788

Fax: (020) 8449 0430

VV TRANSFORMERS

Transformers and Chokes for all types of circuits including specialist valve units
Custom design or standard range
High and low voltage

Variable Voltage Technology Ltd

Unit 8, Sheat Manor Farm, Chiltonton,
Newport, Isle of Wight, PO30 3HP
Tel: 0070 243 0414 Fax: 01983 721572
email: sales@vv-transformers.co.uk

www.vvtransformers.co.uk

SURVEILLANCE, SECURITY AND WIRELESS LINK TECHNOLOGY

Professional 2 channel audio, video & audio links
(1394MHz, 2.4GHz & 10GHz).

Professional 2.4GHz fully synthesized tuning video and audio receivers. High gain directional antennas (dramatically increase range).

Covert video and audio surveillance equipment. Concealed covert equipment (briefcases, calculators, soft toys etc.). Electronic design and custom made equipment. Coming soon: Latest technology, high quality digital spread spectrum surveillance equipment.

Special battery power supplies & chargers (to increase run time).

Contact: QTRONIX Tel: 0115 9522646
Email: info.qtronix@ntlworld.com

The Versatile, Programmable On Screen Display System

www.STV5730A.co.uk



Component Kits!

<p>£4.99</p> <p>CAP-001 2500pF Electrolytic Capacitor Kit (1-2500uF 16-50V)</p>	<p>£9.99</p> <p>RES-001 10000pF Metal Film Resistor Kit (100-50M 0.25W 1%)</p>
<p>£4.99</p> <p>CAP-002 1000pF Polyester Capacitor Kit (1-1000pF 50V)</p>	<p>£4.99</p> <p>CAP-003 3300pF Electrolytic Capacitor Kit (1-3300uF 16-50V)</p>

Mail order P&P: £2.50 (Free P&P orders over £20)

www.fastcomponents.co.uk

Tel: 0870 750 4466 Fax: 0870 137 6005
Winchester House, Winchester Rd,
Wallington-Thames, Surrey, KT12 2RH

PROSCHEMATIC

A shareware schematic drawing tool.
Draw in different styles, print, publish, netlist and generate a Bill of Materials.

Visit: www.hobbyace.co.uk

Free plugin modules available from SATURNSoft LTD

BTEC ELECTRONICS TECHNICIAN TRAINING

VCE ADVANCED ENGINEERING
ELECTRONICS AND ICT
HNC AND HND ELECTRONICS
NVQ ENGINEERING AND IT
**PLEASE APPLY TO COLLEGE FOR
NEXT COURSE DATE
FULL PROSPECTUS FROM**

LONDON ELECTRONICS COLLEGE
(Dept EPE) 20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721

ByVac

29 Springwood View, Penistone
S36 6SX

Microcontroller, no development tools needed, runs BASIC will run stand alone
KIT £14.95 + £1.81 P & P

www.byvac.com



BOWOOD ELECTRONICS LTD

Suppliers of Electronic Components

Place a secure order on our website or call our sales line
All major credit cards accepted

Web: www.bowood-electronics.co.uk

Unit 1, McGregor's Way, Turnoaks Business Park,
Chesterfield, S40 2WB. Sales: 01246 200222

Send 60p stamp for catalogue

Miscellaneous

MICRO CHIP DEVICES for home and business. Projects and Products on Microchip and 1-wire technologies. Visit our WEB site at: www.microchipdevices.com

VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

FREE! PROTOTYPE PRINTED CIRCUIT BOARDS! Free prototype p.c.b. with quantity orders. Call Patrick on 028 9073 8897 for details. Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast BT5 4GX.

PRINTED CIRCUIT BOARDS - QUICK SERVICE. Prototype and production artwork raised from magazines or draft designs at low cost. PCBs designed from schematics. Production assembly, wiring and software programming. For details contact Patrick at Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast BT5 4GX. Phone 028 9073 8897, Fax 028 9073 1802, Email agar@argonet.co.uk

KITS, TOOLS, COMPONENTS. S.a.e. catalogue: Sir-Kit Electronics, 52 Severn Road, Clacton, CO15 3RB.
www.geocities.com/sirkituk

Computer Software

FREE DOWNLOADABLE SOFTWARE: Electronics, Electrical and Computing V8.2. Computer Science V8.2 and GCSE Maths V8.2. Still selling at £120 each on CDROM is now available to download and fully install to your hard drive COMPLETELY FREE OF CHARGE. Latest update includes the new Web Links feature. Visit www.eptsoft.com for details.

N. R. BARDWELL LTD (Est. 1948)

100	Signal Diodes 1N4148	£1.00	80	Asstd. capacitors 1nF to 1µF	£1.00
75	Rectifier Diodes 1N4001	£1.00	200	Asstd. disc ceramic capacitors	£1.00
50	Rectifier Diodes 1N4007	£1.00	50	Asstd. SMD Presets (sm, stand, ceramic)	£1.00
10	W01 Bridge Rectifiers	£1.00	50	Asstd. RF chokes (inductors)	£1.00
10	555 Timer I.C.s	£1.00	25	Asstd. grommets	£0.60
4	741 Op Amps	£1.00	8	Asstd. di. switches	£1.00
50	Assorted Zener Diodes 400mW	£1.00	8	Asstd. push-button switches, multi-bank, multi-pole	£1.00
12	Assorted 7-segment Displays	£1.00	30	Asstd. di. sockets up to 40 way	£1.00
35	Assorted I.e.d.s, var. shapes, colours & sizes	£1.00	10	TV coax plugs, plastic	£1.00
25	5mm I.e.d.s, red or green or yellow	£1.00		metres very thin connecting wire, red	£1.00
25	3mm I.e.d.s, red or green or yellow	£1.00	40	Tin. glass reed switches	£1.00
75	5mm I.e.d.s, green, 8-5mm legs	£1.00	20	Any one value 1/4W 5% of resistors range 1R to 10M	£0.45
50	Axial I.e.d.s, 2mcd red Diode Package	£1.00	10	7812 Voltage Regulators	£1.00
25	Asstd. High Brightness I.e.d.s, var. cols	£1.00	300	Asstd. resistors, 1/4W 1/2W, mostly on tapes	£1.00
20	BC182L Transistors	£1.00			
25	BC212L Transistors	£1.00			
30	BC237 Transistors	£1.00			
20	BC327 Transistors	£1.00			
30	BC328 Transistors	£1.00			
30	BC547 Transistors	£1.00			
20	BC547B Transistor	£1.00			
30	BC548 Transistors	£1.00			
30	BC549 Transistors	£1.00			
25	BC557 Transistors	£1.00			
30	BC558 Transistors	£1.00			
25	BC559 Transistors	£1.00			
20	2N3904 Transistors	£1.00			
100	1nF 50V wkg Axial Capacitors	£1.00			
80	Asstd capacitors electrolytic	£1.00			

288 Abbeydale Road, Sheffield S7 1FL
Phone (local rate): 0845 166 2329
Fax: 0114 255 5039

e-mail: sales@bardwells.co.uk
web: www.bardwells.co.uk
Prices include VAT. Postage £1.85
44p stamp for lists or disk
POs, Cheques and Credit Cards accepted
SEE OUR WEB PAGES FOR MORE
COMPONENTS AND SPECIAL OFFERS



Get your magazine "instantly" anywhere in the world – buy from the web.

TAKE A LOOK, A FREE ISSUE IS AVAILABLE

A one year subscription (12 issues) costs just \$14.99 (US)
www.epemag.com

Europe's Largest Surplus Store

20,000,000 Items on line NOW !
New items added daily

Established for over 25 years, UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

We Ship Worldwide

Surplus Wanted

www.distel.co.uk

Display Electronics
29 / 35 Osborne Road
Thornton Heath
Surrey UK CR7 8PD

Telephone
[44] 020 8653 3333
Fax [44] 020 8653 8888

EPE BINDERS

KEEP YOUR MAGAZINES SAFE – RING US NOW!

This ring binder uses a special system to allow the issues to be easily removed and re-inserted without any damage. A nylon strip slips over each issue and this passes over the four rings in the binder, thus holding the magazine in place.

The binders are finished in hard-wearing royal blue p.v.c. with the magazine logo in gold on the spine. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £6.95 plus £3.50 post and packing. If you order more than one binder add £1 postage for each binder after the initial £3.50 postage charge (overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each).

Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by card), to **Everyday Practical Electronics, Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.**

E-mail: editorial@epemag.wimborne.co.uk. Web site: <http://www.epemag.co.uk>
Order on-line from www.epemag.co.uk/shopdoor.htm

We also accept card payments. Mastercard, Visa, Amex, Diners Club or Maestro. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), plus Maestro Issue No. with your order.



SQUIRES

MODEL & CRAFT TOOLS

A COMPREHENSIVE RANGE OF MINIATURE HAND AND POWER TOOLS AND AN EXTENSIVE RANGE OF **ELECTRONIC COMPONENTS**

FEATURED IN A FULLY ILLUSTRATED

704 PAGE MAIL ORDER CATALOGUE

2005 ISSUE

**SAME DAY DESPATCH
FREE POST AND PACKAGING**

Catalogues: FREE OF CHARGE to addresses in the UK.
Overseas: CATALOGUE FREE, postage at cost charged to credit card

SHOP EXTENSION NOW OPEN

**Squires, 100 London Road,
Bognor Regis, West Sussex, PO21 1DD**



TEL: 01243 842424
FAX: 01243 842525



Rechargeable Batteries With Solder Tags

NIMH

AA 2000mAh	£2.82
C 4Ah	£4.70
D 9Ah	£7.60
PP3 150mAh	£4.95

NICAD

AA 650mAh	£1.41
C 2.5Ah	£3.60
D 4Ah	£4.95

Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT(=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.



866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = **£8.77**



Please add £1.66 + VAT = £1.95 postage & packing per order

JPG Electronics

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

www.JPGElectronics.com

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

ADVERTISERS INDEX

AUTOTRAX	Cover (iv)
N. R. BARDWELL	447
BITZ TECHNOLOGY	396
BRUNNING SOFTWARE	378
BULL GROUP	Cover (ii)
CRICKLEWOOD ELECTRONICS	393
DISPLAY ELECTRONICS	447
ESR ELECTRONIC COMPONENTS	386
JAYCAR ELECTRONICS	405
JPG ELECTRONICS	448
LABCENTER	Cover (iii)
MAGENTA ELECTRONICS	384/385
MATRIX MULTIMEDIA	420
MILFORD INSTRUMENTS	429
NURVE NETWORKS LLC	425
PICO TECHNOLOGY	397/420
QUASAR ELECTRONICS	380/381
SHERWOOD ELECTRONICS	448
SQUIRES	447
STEWART OF READING	392
SUMA DESIGNS	425

ADVERTISEMENT OFFICES:

408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND

PHONE: 01202 873872

FAX: 01202 874562

EMAIL: epeads@wimborne.co.uk

For Editorial address and phone numbers see page 387

SHERWOOD ELECTRONICS

FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

SP1 15 x 5mm Red LEDs	SP135 6 x Miniature slide switches
SP2 12 x 5mm Green LEDs	SP136 3 x 8F50 transistors
SP3 12 x 5mm Yellow LEDs	SP137 4 x W005 1.5A bridge rectifiers
SP5 25 x 5mm 1 part LED clips	SP138 20 x 2.2/63V radial elect. caps.
SP6 15 x 3mm Red LEDs	SP140 3 x W04 1.5A bridge rectifiers
SP7 12 x 3mm Green LEDs	SP142 2 x CMOS 4017
SP8 10 x 3mm Yellow LEDs	SP143 5 Pairs min. crocodile clips (Red & Black)
SP9 25 x 3mm 1 part LED clips	SP144 5 Pairs min.crocodile clips (assorted colours)
SP10 100 x 1N4148 diodes	SP146 10 x 2N3704 transistors
SP11 30 x 1N4001 diodes	SP147 5 x Stripboard 9 strips x 25 holes
SP12 30 x 1N4002 diodes	SP151 4 x 8mm Red LEDs
SP18 20 x BC182 transistors	SP152 4 x 8mm Green LEDs
SP20 20 x BC184 transistors	SP153 4 x 8mm Yellow LEDs
SP23 20 x BC549 transistors	SP154 15 x BC548 transistors
SP24 4 x CMOS 4001	SP156 3 x Stripboard, 14 strips x 27 holes
SP25 4 x 555 timers	SP160 10 x 2N3904 transistors
SP26 4 x 741 Op.Amps	SP161 10 x 2N3906 transistors
SP28 4 x CMOS 4011	SP162 2 x C106D thyristors
SP29 3 x CMOS 4013	SP165 2 x LF351 Op.Amps
SP33 4 x CMOS 4081	SP166 20 x 1N4003 diodes
SP34 20 x 1N914 diodes	SP167 5 x BC107 transistors
SP36 25 x 10/25V radial elect. caps.	SP168 5 x BC108 transistors
SP37 12 x 100/35V radial elect. caps.	SP171 8 Meters 18SWG solder
SP38 15 x 47/25V radial elect. caps.	SP172 4 x Standard slide switches
SP39 10 x 470/16V radial elect. caps.	SP173 10 x 220/25V radial elect. caps.
SP40 15 x BC237 transistors	SP174 20 x 22/25V radial elect. caps.
SP41 20 x Mixed transistors	SP175 20 x 1/63V radial elect. caps.
SP42 200 x Mixed 0.25W C.F. resistors	SP177 10 x 1A 20mm quick blow fuses
SP47 5 x Min. PB switches	SP178 10 x 2A 20mm quick blow fuses
SP49 4 x 5 metres stranded core wire	SP181 5 x Phone plugs - assid colours
SP101 8 Meters 22SWG solder	SP182 20 x 4.7/63V radial elect. caps.
SP102 20 x 8-pin DIL sockets	SP183 20 x BC547 transistors
SP103 15 x 14-pin DIL sockets	SP187 15 x BC239 transistors
SP104 15 x 16-pin DIL sockets	SP189 4 x 5 metres solid core wire
SP105 4 x 74LS00	SP192 3 x CMOS 4066
SP109 15 x BC557 transistors	SP193 3 x 10mm Yellow LEDs
SP112 4 x CMOS 4093	SP197 6 x 20 pin DIL sockets
SP115 3 x 10mm Red LEDs	SP198 5 x 24 pin DIL sockets
SP116 3 x 10mm Green LEDs	SP199 5 x 2.5mm mono jack plugs
SP118 2 x CMOS 4047	SP200 5 x 2.5mm mono jack sockets
SP124 20 x Assorted ceramic disc caps	
SP126 6 x Battery clips - 3 ea. PP3 + PP9	
SP130 100 x Mixed 0.5W C.F. resistors	
SP131 2 x TL071 Op.Amps	
SP133 20 x 1N4004 diodes	
SP134 15 x 1N4007 diodes	

RESISTOR PACKS - C.Film

RP3 5 each value - total 365 0.25W	£3.30
RP7 10 each value - total 730 0.25W	£4.55
RP10 1000 popular values 0.25W	£6.45
RP4 5 each value-total 345 0.5W	£4.20
RP8 10 each value-total 690 0.5W	£6.85
RP11 1000 popular values 0.5W	£8.70

2005 Catalogue now available £1 inc. P&P or FREE with first order.

P&P £1.50 per order. NO VAT Cheques and Postal Orders to:

Sherwood Electronics,
7 Williamson St., Mansfield,
Notts. NG19 6TD.

EPE SUBSCRIPTIONS

SAVE 51p AN ISSUE OVER UK NEWSTAND PRICES
ON A UK ONE YEAR SUBSCRIPTION

Subscriptions for delivery direct to any address in the UK: 6 months £16.50, 12 months £31, two years £57; Overseas: 6 months £19.50 standard air service or £28.50 express airmail, 12 months £37 standard air service or £55 express airmail, 24 months £69 standard air service or £105 express airmail. Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to *EPE Subs. Dept.*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Switch or Visa. (For past issues see the Back Issues page.)

ONLINE SUBSCRIPTIONS

Online subscriptions, for downloading the magazine via the Internet, \$14.99US (approx. £8) for one year available from www.epemag.com.

USA/CANADA SUBSCRIPTIONS

To subscribe to *EPE* from the USA or Canada please telephone Express Mag toll free on 1877 363-1310 and have your credit card details ready. Or fax (514) 355 3332 or write to Express Mag, PO Box 2769, Plattsburgh, NY 12901-0239 or Express Mag, 8155 Larrey Street, Anjou, Quebec, H1J 2L5.

Email address: expsmag@expressmag.com.

Web site: www.expressmag.com.

USA price \$60(US) per annum, Canada price \$97(Can) per annum - 12 issues per year.

Everyday Practical Electronics, periodicals pending, ISSN 0262 3617 is published twelve times a year by Wimborne Publishing Ltd., USA agent USACAN at 1320 Route 9, Champlain, NY 12919. Subscription price in US \$60(US) per annum. Periodicals postage paid at Champlain NY and at additional mailing offices. POSTMASTER: Send USA and Canada address changes to *Everyday Practical Electronics*, c/o Express Mag., PO Box 2769, Plattsburgh, NY, USA 12901-0239.